

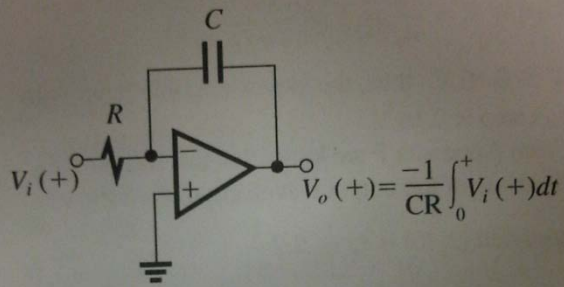


Ex: 2.27

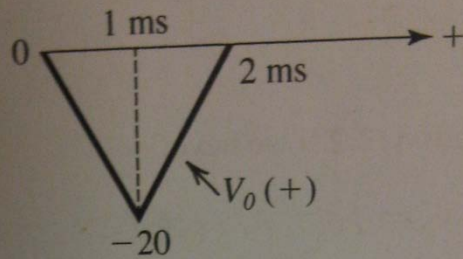

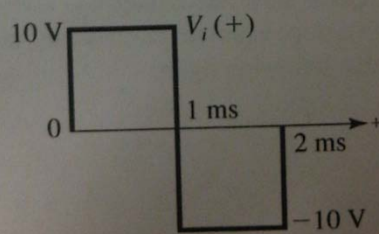The waveforms for one period of the input and the output signals are shown below:



We have

$$-20 = \frac{-1}{CR} \int_0^{1 \text{ ms}} 10 dt$$

$$\Rightarrow -20 = \frac{-1}{CR} \times 10 \times 1 \text{ ms}$$

$$CR = \frac{10}{20} \times 1 \text{ ms} = 0.5 \text{ ms}$$

2.2

Refer to fig P 2.2

$$v_+ = v_i \times \frac{1 \text{ K}}{1 \text{ K} + 1 \text{ M}} = v_i \frac{1}{1001}$$

$$v_o = A v_+ = A v_i \frac{1}{1001}$$

$$A = 1001 \frac{v_o}{v_i}$$

$$= 1001 \times \frac{4}{2}$$

$$A = 2002 \text{ V/V}$$

2.41


$v_o = v_1 + 2v_2 - 3v_3 - 4v_4$: Consider Fig. 2.11.

According to eq. 2.8 For a weighted summer circuit:

$$v_o = v_1 \frac{R_a R_c}{R_1 R_b} + v_2 \frac{R_a R_c}{R_2 R_b} - v_3 \frac{R_c}{R_3} - v_4 \frac{R_c}{R_4}$$

$$\frac{R_a}{R_1} \frac{R_c}{R_b} = 1, \frac{R_a}{R_2} \frac{R_c}{R_b} = 1, \frac{R_c}{R_3} = 3, \frac{R_c}{R_4} = 4$$

assume:

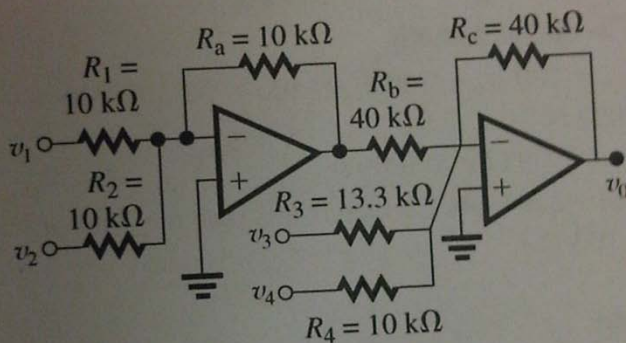

$$R_4 = 10 \text{ k}\Omega \Rightarrow R_c = 40 \text{ k}\Omega \Rightarrow R_3 = \frac{40}{3}$$

$$= 13.3 \text{ k}\Omega$$

$$\frac{R_a}{R_1} \times \frac{40}{R_b} = 1 \quad \frac{R_a}{R_2} \times \frac{40}{R_b} = 1$$

$$R_b = 40 \text{ k}\Omega, \quad R_1 = R_2 = R_a = 10 \text{ k}\Omega$$


2.49

$$v_+ = v_I \frac{R_4}{R_3 + R_4} = v$$

$$\frac{v}{R_1} = \frac{v_o - v_-}{R_2} \Rightarrow v_o = v_- \left(1 + \frac{R_2}{R_1} \right)$$

From the two above equations:
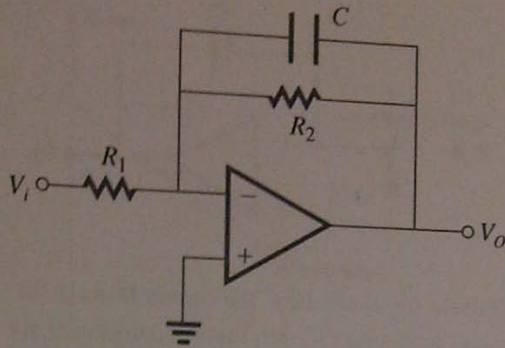
$$\frac{v_o}{v_I} = \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$



Let $Z_2 = R_2 \parallel \frac{1}{sC}$ and $Z_1 = R_1$

$$\begin{aligned} \frac{v_o}{v_i} &= -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{1/R_1}{\frac{1}{R_2} + sC} \\ &= -\frac{(R_2/R_1)}{1 + sCR_2} \end{aligned}$$

This function is of a STC, low pass circuit having


a dc gain of $-\frac{R_2}{R_1}$ and 3-dB frequency

$$\omega_0 = \frac{1}{CR_2}$$

$$R_n = R_1 = 10 \text{ k}\Omega$$

$$\text{dc gain} = 20 \text{ dB} = 10$$
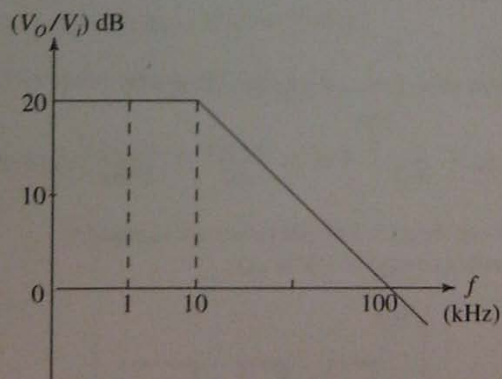
$$\therefore 10 = \frac{R_2}{R_1} \Rightarrow R_2 = 10 R_1 = 100 \text{ k}\Omega$$



3dB frequency at 10 kHz

$$\therefore \omega_0 = 2\pi \times 10 \times 10^3 = \frac{1}{CR_2}$$

$$C = \frac{1}{2\pi \times 10 \times 10^3 \times 100 \text{ K}} = 0.5 \text{ nF}$$

Unity gain frequency at 100 kHz