

Ex: 6.13

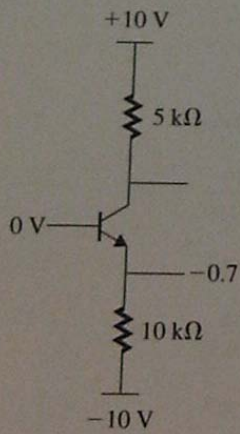


Fig 6.13

$$\beta = 50, V_{BE} = 0.7 \text{ V}$$

$$V_E = V_B - 0.7 \text{ V}$$

$$= 0 - 0.7 = -0.7 \text{ V}$$

$$I_E = \frac{-0.7 + 10}{10 \text{ K}}$$

$$= 0.93 \text{ mA}$$

$$I_C = \frac{50}{51} I_E = 0.91 \text{ mA}$$


$$V_C = 10 - 0.91 \times 5$$

$$= 5.45 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.91}{50}$$

$$= 0.0182 \mu\text{A}$$

**Ex: 6.23**

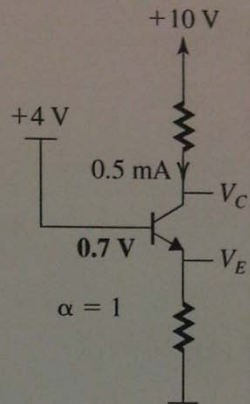

$$V_E = V_B - 0.7$$

$$= 4 - 0.7 = 3.3 \text{ V}$$

$$R_E = \frac{3.3 \text{ V}}{0.5 \text{ mA}} = 6.6 \text{ k}\Omega$$


$$V_C = V_B + 2 \text{ V}$$

$$= 4 + 2 = +6 \text{ V}$$

$$R_C = \frac{V_{CC} - V_C}{I}$$

$$= \frac{10 - 6}{0.5} = 8 \text{ k}\Omega$$

Ex 6.28

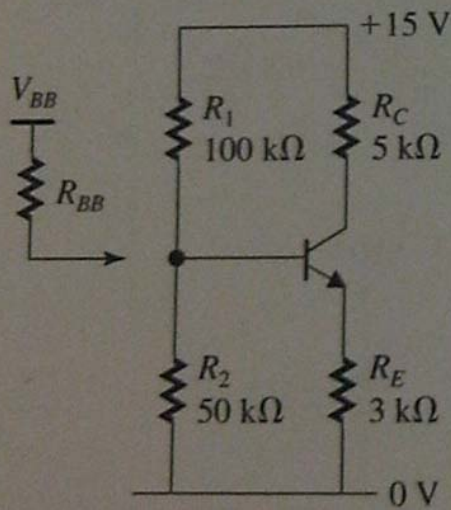

$$\beta = 50$$

$$V_{BB} = \frac{15 \times 50}{150} = 5 \text{ V}$$

$$R_{BB} = 50 \parallel 100 \\ = 100/3 \text{ k}\Omega$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + [R_{BB}/(\beta + 1)]}$$

$$= \frac{4.3}{3 + \frac{100}{3} \cdot \frac{1}{51}}$$


$$= 1.18 \text{ mA}$$

$$I_C = I_E \frac{50}{51} = 1.15 \text{ mA}$$

$$\% \text{ change} = \frac{1.28 - 1.15}{1.28}$$

$$\Rightarrow -9.8\%$$

6.17

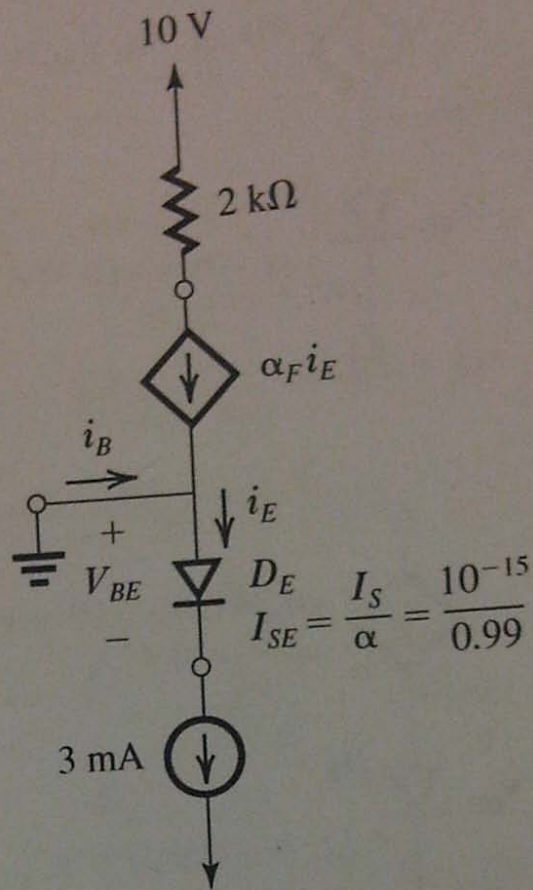

$$\beta = 100, I_S = 10^{-15} \Rightarrow \alpha = \frac{100}{101} = 0.99$$

$$i_E = I_{SE} e^{v_{BE}/V_T}$$

$$3 \times 10^{-3} = \frac{10^{-15}}{0.99} e^{v_{BE}/0.025}$$


$$V_{BE} = 0.718 \text{ V}$$

$$V_E = 0 - 0.718 = -0.718 \text{ V}$$


$$i_C = \alpha i_E = 0.99 \times 3 \text{ mA}$$

$$\begin{aligned}
 V_C &= 10 - 2i_C = 10 - 2 \times 0.99 \times 3 \\
 &= 4.06 \text{ V}
 \end{aligned}$$

6.29

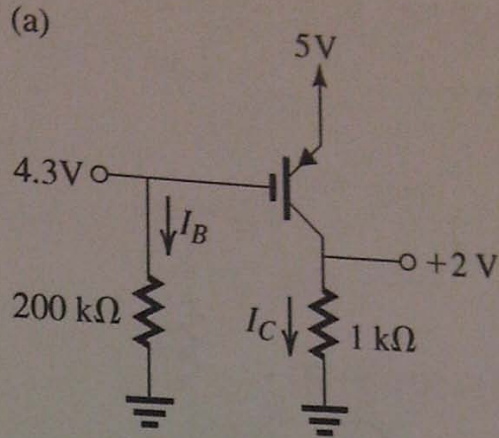
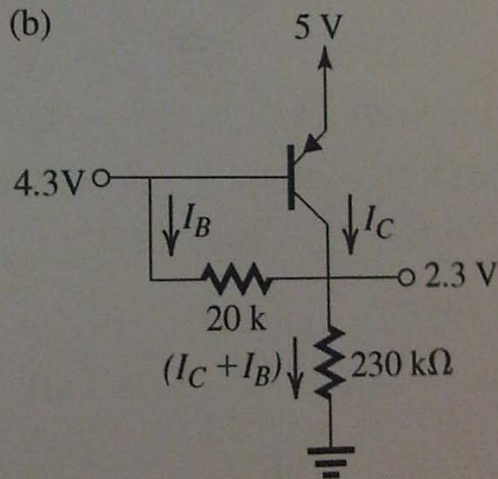
$$\frac{I_c}{I_B} = \beta = \frac{\left(\frac{2}{1 \text{ K}}\right)}{\left(\frac{4.3}{200 \text{ K}}\right)} = \frac{2 \text{ m}}{0.0215 \text{ m}} = 93$$




$$(I_c + I_B) = \frac{2.3}{230} = 10 \text{ mA}$$

$$I_B = \left(\frac{4.3 - 2.3}{20 \text{ K}}\right) = 0.1 \text{ mA}$$

$$\frac{I_c}{I_B} = \left(\frac{10 \text{ m} - 0.1 \text{ m}}{0.1 \text{ m}}\right) = \beta = 99$$



6.32

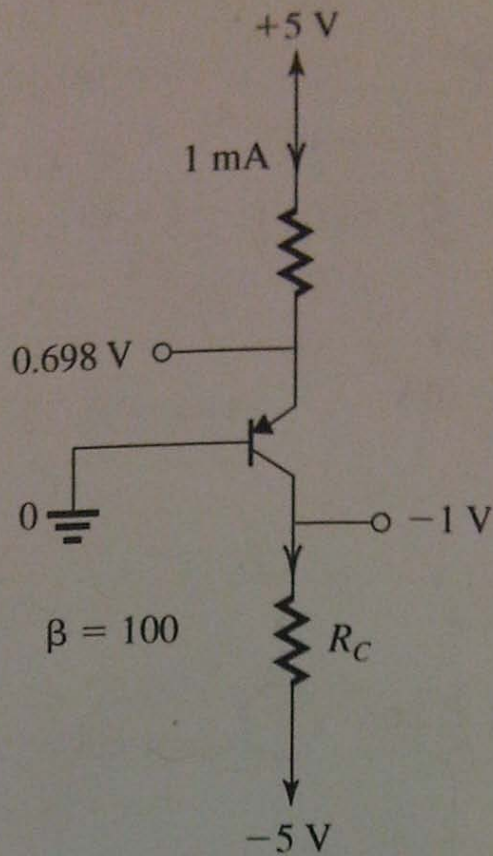

$$V_{BE(1\text{mA})} - V_{BE(0.1\text{mA})}$$

$$= 25 \ln \left[ \frac{1}{0.1} \right]$$

$$\therefore V_{BE(1\text{mA})} = 640 \text{ mV} + 57.9 \text{ mV} \\ = 698 \text{ mV}$$

$$I_C = \frac{100}{101} I_E = 0.99 \text{ mA}$$


$$R_C = \frac{-1 - (-5)}{0.99} = 4.04 \text{ k}\Omega$$

$$R_E = \frac{5 - 0.698}{1} = 4.3 \text{ k}\Omega$$

$V_C$  can be raised until  $\approx +0.4 \text{ V}$

$$R_C = \frac{5 + 0.4}{0.99} = 5.45 \text{ k}\Omega$$

6.34

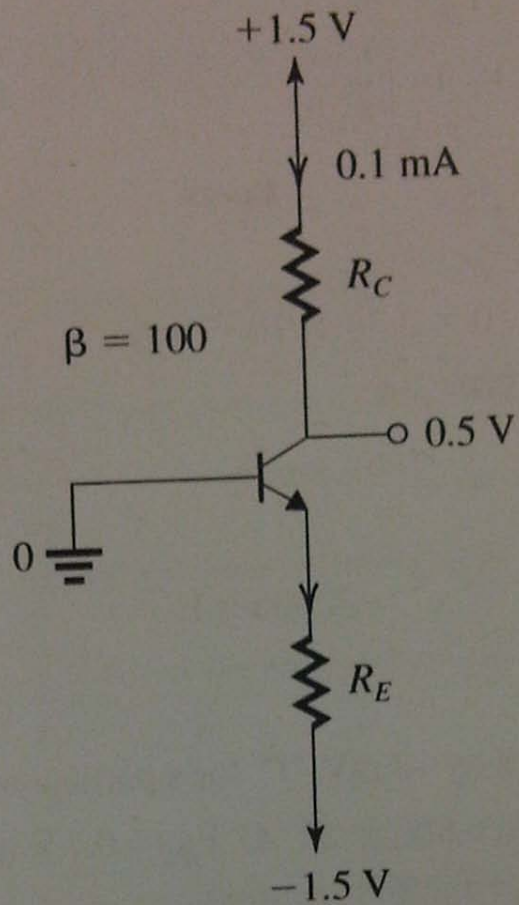

$$\Delta V_{BE} = V_T \ln \left[ \frac{I_{C2}}{I_{C1}} \right]$$

$$= 25 \ln [0.1] = -57.6 \text{ mV}$$

$$V_{BE(0.1)} = 742 \text{ mV}$$

$$R_C = \frac{1.5 - 0.5}{0.1} = 10 \text{ k}\Omega$$

$$V_E = -0.742 \text{ V}$$

$$R_E = \frac{-0.742 + 1.5}{\frac{\beta + 1}{\beta} I_C}$$

$$= \frac{100}{101} \cdot \frac{0.758}{0.1} = 7.5 \text{ k}\Omega$$

(b)  $V_B = 0 \text{ V}$

$$V_E = V_B + 0.8 = 0.8 \text{ V}$$

$$I_E = \frac{0.8 - 1.5}{1 \text{ K}} = 0.7 \text{ mA}$$

$$I_C = \alpha I_E = \frac{50}{51}(0.7 \text{ m}) = 0.69 \text{ mA}$$

$$V_C = I_C(1 \text{ K}) - 1.5 = -0.81 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = 0.69 \text{ m} / 50 = 14 \text{ } \mu\text{A} \text{ and}$$

$$V_C < V_B < V_E \text{ so Active}$$

(c)  $V_B = 1 \text{ V}$

$$V_E = V_B + 0.8 = 1.8 \text{ V}$$

$$I_E = \frac{3 - 1.8}{1.1 \text{ K}} = 1 \text{ mA}$$

$$I_C = \alpha I_E = \frac{50}{51} \times 1 \text{ m} = 0.98 \text{ mA}$$

$$V_C = I_C(560) = 0.55 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.98 \text{ m}}{50} = 20 \text{ } \mu\text{A} \quad \text{and}$$

$$V_C < V_B < V_E \text{ so Active}$$

(d)  $V_B = 1.5 \text{ V}$

$$V_E = 1.5 - 0.8 = 0.7 \text{ V}$$

$$I_E = \frac{0.7}{470} = 1.5 \text{ mA}$$

$$I_C = \alpha I_E = \frac{50}{51}(1.5 \text{ m}) = 1.47 \text{ mA}$$

$$V_C = 3 - (1.47 \text{ m})(1 \text{ K}) = 1.52 \text{ V}$$


$$I_B = \frac{I_C}{\beta} = \frac{1.47 \text{ m}}{50} = 29 \text{ } \mu\text{A} \text{ and}$$

$$V_C > V_B > V_E \text{ so Active}$$

6.35 (B & D)



6.49

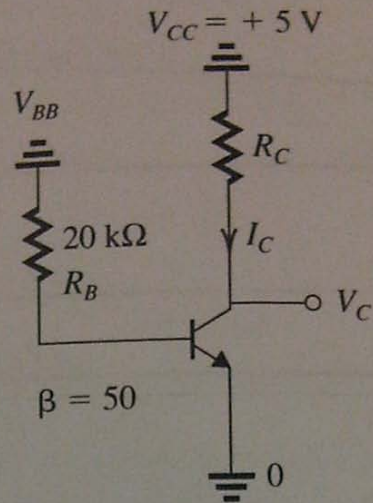

(a) active region

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$= \frac{5 - 1}{1 \text{ K}} = 4 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{4}{50} = 0.08 \text{ mA}$$

$$V_{BB} = 0.7 + \frac{20 \times 4}{50}$$

$$= +2.3 \text{ V}$$

(b) edge of saturation  $v_C = 0.3 \text{ V}$ 

$$I_C = \frac{5 - 0.3}{1} = 4.7 \text{ mA}$$

$$I_B = I_C / \beta = 4.7 / 50 = 0.094 \text{ mA}$$

$$V_{BB} = 0.094 \times 20 + 0.7 = 2.58 \text{ V}$$


(c) deep saturation  $v_C = 0.2 \text{ V}$   $\beta_F = 10$ 

$$I_C = (5 - 0.2) / 1 = 4.8 \text{ mA}$$

$$I_B = I_C / \beta_{\text{forced}} = 4.8 / 10 = 0.48 \text{ mA}$$

$$V_{BB} = 0.48 \times 20 + 0.7 = +10.3 \text{ V}$$

6.59

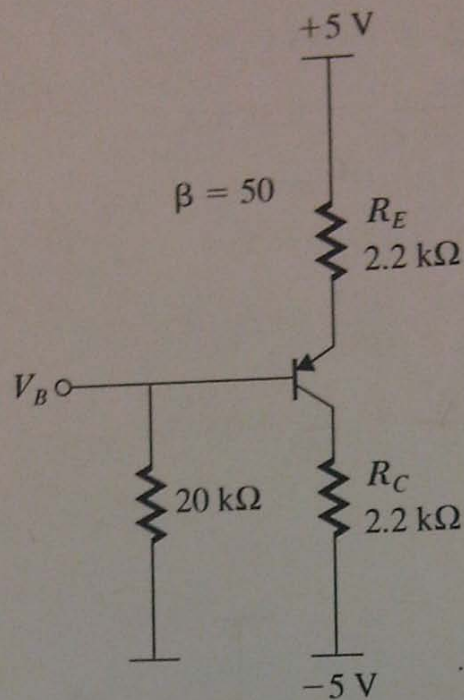For  $R_B = 20 \text{ k}\Omega$ 

$$I_E = \frac{5 - 0.7}{2.2 + 20/51} = 1.66 \text{ mA}$$

$$I_C = I_E \frac{50}{51} = 1.63 \text{ mA}$$

$$V_C = -5 + 2.2 \times 1.63 = -1.42 \text{ V}$$

$$V_E = +5 - 2.2 \times 1.66 = +1.35 \text{ V}$$

$$V_B = V_E - 0.7 = -0.65 \text{ V}$$

For  $R_B = 100 \text{ k}\Omega$ 

$$I_E = \frac{5 - 0.7}{2.2 + 100/51} = 1.03 \text{ mA}$$

$$V_E = 5 - 1.03 \times 2.2 = +2.73 \text{ V}$$

$$V_B = 0 + \frac{1.03}{51} \times 100 = +2.03 \text{ V}$$

$$V_C = -5 + 1.03 \times \frac{50}{51} \times 2.2 = -2.78 \text{ V}$$

$$\text{For same } I_B: \beta = 51 \times \frac{100}{20} - 1 = 255$$

6.62(d)(e)

