
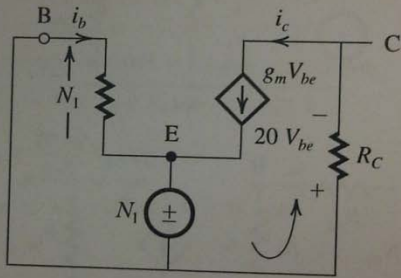


6.95

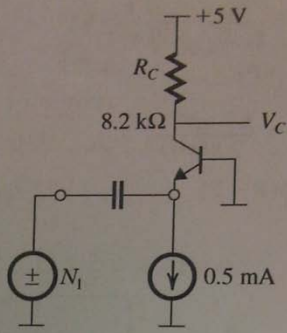

For β very high

$$I_C \approx I_E = 0.5 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.5}{0.025} = 20 \text{ mA/V}$$

$$V_C = 5 - 8.2 \times 0.5 = 0.9 \text{ V}$$



Note: $V_\pi = -V_1$

$$\text{Then } V_C = -g_m R_C V_{be}$$

$$V_C = -20(-)V_1 \times 8.2$$

$$\therefore \frac{V_C}{V_1} = +164 \text{ V/V}$$

6.97


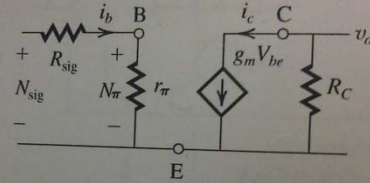
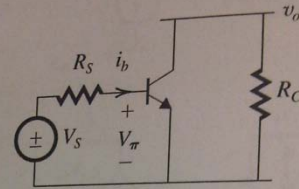


$$\frac{v_O}{v_{sig}} = \frac{v_1}{v_1} = \frac{r_\pi (-) g_m R_C}{r_\pi + R_{sig}}$$

$$= \frac{-r_\pi g_m R_C}{r_\pi + R_{sig}}$$

$$= \frac{-\beta R_C}{r_\pi + R_{sig}}$$

6.100

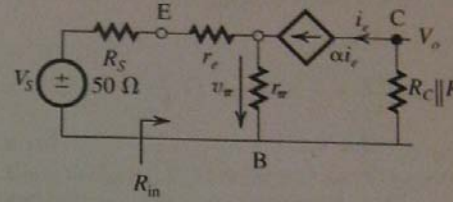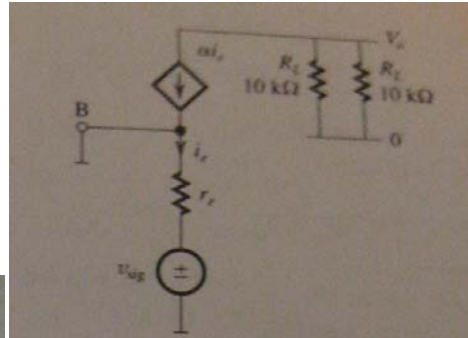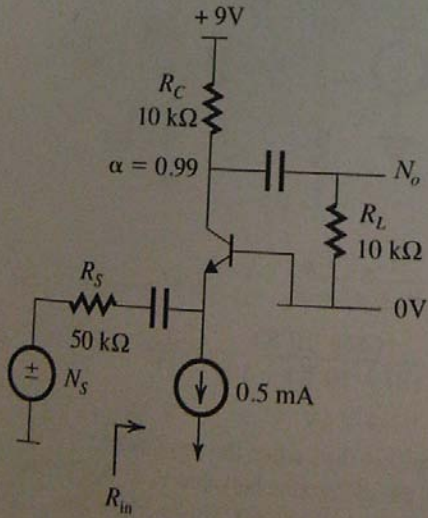

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$

$$R_{IN} = r_e = 50 \Omega$$

$$v_o = -0.99 i_e (R_C \parallel R_L)$$

$$= -0.99 \frac{(-v_s)}{R_{IN}} 5 \text{ k}\Omega$$

$$\frac{v_o}{v_s} = + \frac{0.99 \times 5}{0.050} = + 99 \text{ V/V}$$

6.101

Refer to Fig P5.1166

$$\beta = 200 \rightarrow \alpha = 0.995$$

$$I_C - \alpha I_E = 0.995 \times 10 \text{ mA} = 9.95 \text{ mA}$$

$$V_C = 9.95 \text{ mA} \times 100 = 0.995 \text{ V}$$


$$I_B \cong \frac{10 \text{ mA}}{200} = 0.05 \text{ mA}$$

$$V_B = 1.5 - 10 \text{ k}\Omega \times 0.05 \text{ mA}$$

$$= 1 \text{ V}$$

$$\Rightarrow V_{BC} = +0.005$$

→ Active region

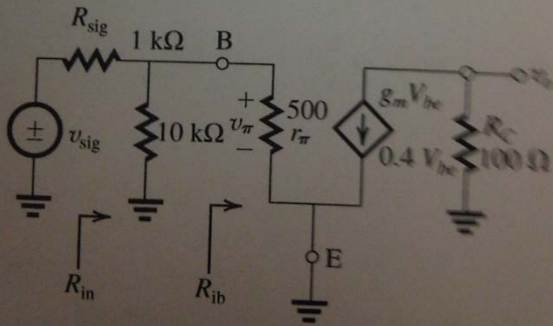

$$g_m = \frac{I_C}{V_T} = \frac{9.95}{25 \text{ m}} = 0.4 \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{200}{0.4} = 500 \Omega$$

$$R_{i6} = r_\pi = 500 \Omega$$

$$R_{in} = 10 \text{ k}\Omega \parallel r_\pi = 476 \Omega$$

$$v_{be} = v_{sig} \times \frac{R_{in}}{R_{sig} + R_{in}} = v_{sig} \times 0.32$$

also :

$$v_o = -g_m v_{be} \cdot R_C$$

$$= -g_m R_C \times 0.32 v_{sig}$$

$$= -0.4 \times 100 \times 0.32 v_{sig}$$

$$= -12.8 v_{sig}$$


$$\Rightarrow \text{gain } \frac{v_o}{v_s} = -12.8 \approx -13 \frac{\text{V}}{\text{V}}$$

$$\text{If } v_o = \pm 0.4 \text{ V}$$

$$\hat{v}_s = \frac{\hat{v}_o}{13} = 30 \text{ mV}$$

$$\hat{v}_{be} = 0.32 \times 30 \text{ m} = 9.8 \text{ mA}$$

6.16]

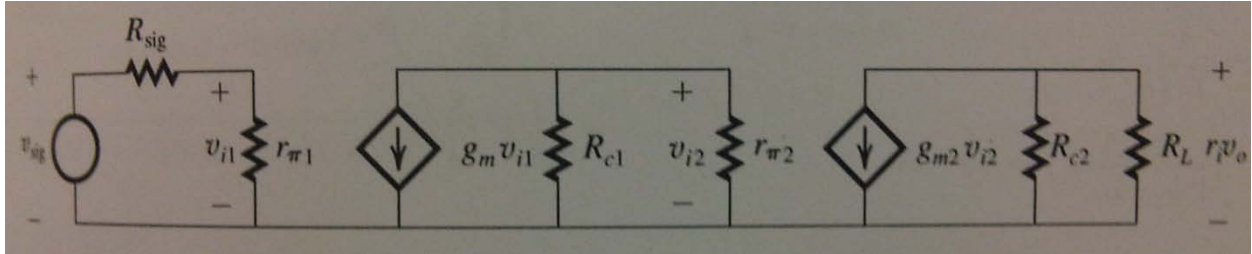

b) Voltage transfer from sig to first stage input

$$v_{i1} / v_{sig} = \frac{r_{\pi 1}}{r_{\pi 1} + R_{sig}}$$

Given $I_C = 0.25 \text{ mA}$; $\beta = 100$; $V_A \rightarrow \infty$;

$R_C = 10 \text{ k}\Omega$; $R_{sig} = 10 \text{ k}\Omega$

$$g_m = \frac{I_C}{V_T}, \quad r_{\pi} = \frac{\beta}{g_m} = \frac{\beta}{I_C} V_T$$

$$r_{\pi} = \frac{100}{0.25 \times 10^{-3}} (0.015) = 10 \text{ k}\Omega$$

$$v_{i1} / v_{sig} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = 1/2$$

c) $A_{V1} = v_{i2} / v_{i1} = -g_m (R_{c1} \parallel r_{\pi 2})$

Since $r_{\pi} = r_{\pi 1} = r_{\pi 2}$ & $R_C = R_{c1} = R_{c2} = 10 \text{ k}\Omega$

$$A_{V1} = -\frac{I_C}{V_T} (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$= -\frac{0.25 \times 10^{-3}}{0.025} (5 \text{ k}\Omega) = -50$$

d) $A_{V2} = v_o / v_{i2} = -g_m \times (R_{c2} \parallel R_L)$


$$= -\frac{I_C}{V_T} (R_{c2} \parallel R_L) = \frac{0.25 \times 10^{-3}}{0.025} (5 \text{ k}\Omega)$$

$$= -50$$

e) $G_V = v_o / v_{sig} = \frac{v_{i1}}{v_{sig}} \times \frac{v_{i2}}{v_{i1}} \times \frac{v_o}{v_{i2}}$

$$= (0.5)(-50)(-50) = G_V = -1250$$

6.142

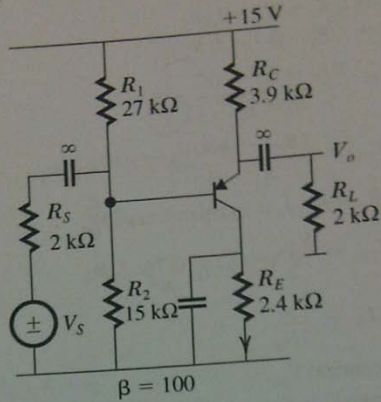

$$R_1 \parallel R_2 = 9.64 \text{ k}\Omega$$

$$V_{BB} = \frac{15 \times R_2}{R_1 + R_2} = 5.36 \text{ V}$$

$$I_E = \frac{V_{BB} - 0.7}{2.4 + \frac{9.64}{101}} = 1.87 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.99 I_E}{V_T} = 74 \text{ V/V}$$

$$r_o = \frac{V_A}{I_C} = 54 \text{ k}\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{74} = 1.35 \text{ k}\Omega$$

$$R_C \parallel R_L = \frac{3.9 \times 2}{5.9} = 1.32 \text{ k}\Omega \ll r_o$$

Thus we can neglect r_o

$$I_C = 0.99 \times I = 1.68 \text{ mA}$$

$$R_{in} = (R_1 \parallel R_2) \parallel r_\pi = 1.18 \text{ k}\Omega$$


$$R_O = r_o \parallel R_C \approx 1.32 \text{ k}\Omega$$

$$\frac{v_O}{v_1} = -\frac{R_{IN}}{R_{IN} + R_s} \times g_m (r_o \parallel R_C \parallel R_L)$$

$$R_s = -\frac{1.18}{3.18} \times 74 \times 1.29$$

$$= -35.4 \text{ V/V}$$

6.147

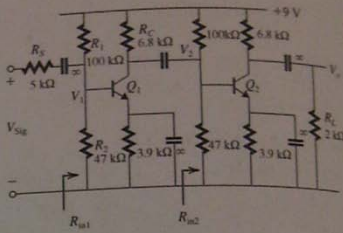

$$I_E = \frac{V_{BB} - 0.7}{R_E + (R_1 \parallel R_2) / (\beta + 1)}$$

$$= \frac{2.88 - 0.7}{3.9 + 32 / 101} \approx 0.5 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.99 \times 0.5}{0.025} = 19.8 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{19.8} \approx 5.05 \text{ k}\Omega$$

$$(c) R_{IN} = [(R_1 \parallel R_2) \parallel r_\pi]$$

$$= 32 \parallel 5 = 4.3 \text{ k}\Omega$$

Stage 2 is identical

$$(d) \frac{v_o}{v_{sig}} = \frac{v_1}{v_{sig}} \cdot \frac{v_2}{v_1}$$

$$= \frac{R_{IN}}{R_S + R_{IN}} \times [(-g_m(R_C \parallel R_{IN}))]$$


$$= \frac{4.3}{9.3} \times (-) 9.8 \times 2.6$$

$$= -23.8$$

$$(e) \frac{v_o}{v_2} = -g_m(R_C R_L) = -30.6 \text{ V/V}$$

$$(f) \frac{v_o}{v_{sig}} = -23.8(-30.6) = +728 \text{ V/V}$$

(b) Equivalent circuit

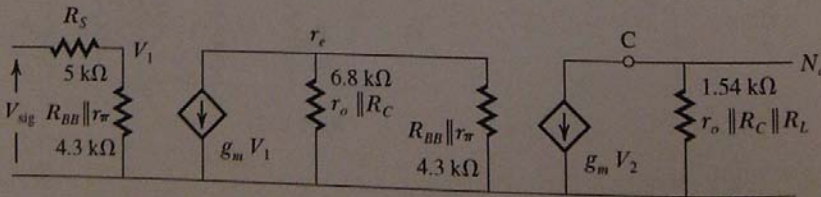



$$\left(r_o = \frac{100}{0.5} = 200 \text{ k}\Omega \text{ ignore} \right)$$

$$g_m = 19.8 \text{ mA/V}$$

(R_E 's are assumed by-passed)

$$G_V = \frac{v_1}{v_{sig}} \cdot \frac{v_2}{v_1} \cdot \frac{v_o}{v_2}$$

6.152

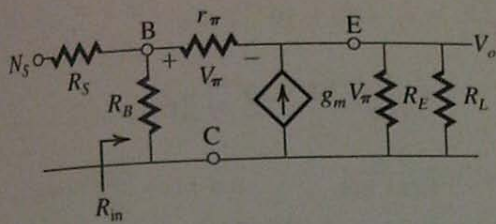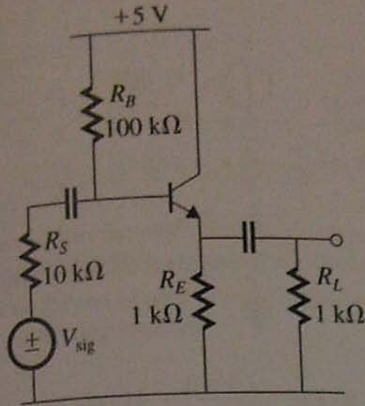 $A_+ E_+$

$$\frac{v_b - v_o}{r_\pi} + g_m r_\pi = \frac{V_O}{R}$$

where $v_\pi = v_b - v_o$ and $R = r_o \parallel R_E \parallel R_L$

$$\begin{aligned} \therefore \frac{v_o}{v_b} &= \frac{1/r_\pi + g_m}{1/r_\pi + g_m + 1/R} \\ &= \frac{R}{R + \frac{r_\pi}{1 + g_m r_\pi}} \\ &= \frac{R}{R + r_e} \end{aligned}$$

Now $R_{IN} = R_B \parallel \left(\frac{v_b}{i_b}\right)$

$$\begin{aligned} \therefore R_{IN} &= R_B \parallel \left[v_b \times \frac{r_\pi}{v_b - v_o} \right] \\ &= R_B \parallel \left[\frac{r_\pi}{1 - v_o/v_b} \right] \\ &= R_B \parallel \left[\frac{r_\pi}{1 - A} \right] \end{aligned}$$

$$I_E(\beta) = \frac{5 - 0.7}{R_B/(\beta + 1) + R_E}$$

$$I_E(50) = \frac{4.3}{100/51 + 1} = 1.45 \text{ mA}$$

$$V_E(50) = 1.45 \text{ V}, \quad V_B(50) = 2.15 \text{ V}$$

$$I_E(200) = \frac{4.3}{100/201 + 1} = 2.87 \text{ mA}$$

$$V_E(200) = 2.8 \text{ mA}, \quad V_B(200) = 3.57 \text{ V}$$

$$\frac{v_o}{v_s} = \frac{v_b}{v_s} \times \frac{v_o}{v_b} = \frac{R_{IN}}{R + R_{IN}} \times \frac{R}{R + r_e}$$

	$\beta = 50$	$\beta = 200$
I_E	1.45 mA	2.87 mA
V_E	1.45 V	2.87 V
V_B	2.15 V	3.57 V
g_m	$56.9 \frac{\text{mA}}{\text{V}}$	$114 \frac{\text{mA}}{\text{V}}$
r_e	17 Ω	8.7 Ω
R_{IN}	20.8 k Ω	49.3 k Ω
$A_v = \frac{v_o}{v_b}$	0.967 V/V	0.982 V/V
$\frac{v_o}{v_{sig}}$	0.653 V/V	0.816 V/V