

**Ex: 5.1**

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{34.5 \text{ pF/m}}{4 \text{ nm}} = 8.625 \text{ fF}/(\mu\text{m})^2$$

$$\mu_n = 450 \text{ cm}^2/\text{VS}$$

$$k'_n = \mu_n C_{ox} = 388 \mu\text{A}/\text{V}^2$$

$$V_{OV} = (v_{GS} - V_t) = 0.5 \text{ V}$$

$$g_{DS} = \frac{1}{1 \text{ k}\Omega} = k'_n \frac{W}{L} V_{OV} \Rightarrow \frac{W}{L} = 5.15$$

$$L = 0.18 \mu\text{m}, \text{ so } W = 0.93 \mu\text{m}$$

$$\text{Ex: 5.3 } I_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2 \text{ in saturation}$$

Change in  $I_D$  is:

(a) double  $L$ , 0.5

(b) double  $W$ , 2

(c) double  $V_{OV}$ ,  $2^2 = 4$

(d) double  $V_{DS}$ , no change (ignoring length modulation)

(e) changes (a) - (d), 4

case (c) would cause leaving saturation if

$$V_{DS} < 2V_{OV}$$

Ex: 5.5  $V_{OV} = 0.5 \text{ V}$

$$g_{DS} = k'_n \frac{W}{L} V_{OV} = \frac{1}{1 \text{ k}\Omega}$$


$$\therefore k_n = k'_n \frac{W}{L} = 2 \text{ mA/V}^2$$

For  $v_{DS} = 0.5 \text{ V} = V_{OV}$

$$I_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2 = 0.25 \text{ mA}$$

for all  $v_{DS} \geq V_{OV} = 0.5 \text{ V}$ .

Ex: 5.9

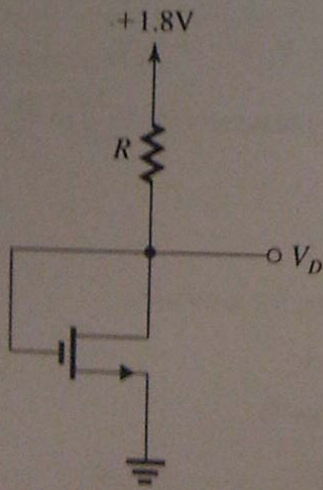

$$\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}} = 4.0$$

$$\lambda = 0$$

saturation mode ( $v_{GD} = 0 < V_{tn}$ )


$$V_D = 0.8 \text{ V} = 1.8 - I_D R_D$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_D - V_{tn})^2 = 72 \mu\text{A}$$

$$\therefore R = \frac{1.8 - 0.8}{72 \mu\text{A}} = 13.9 \text{ k}\Omega$$

$$V_t = 0.7 \text{ V.}$$

$$k_n = 1 \text{ mA} / \text{V}^2$$

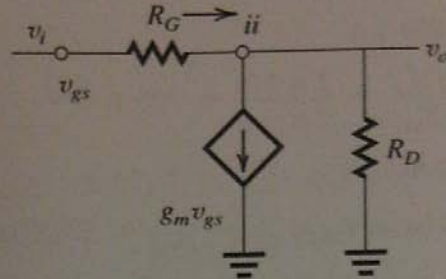

$$\text{Design for } A_v = \frac{v_o}{v_i} = -25, R_{in} = 500 \text{ k}\Omega$$

$$\therefore g_m R_D = 25 = k_n V_{OV} R_D$$

$$R_{in} = \frac{v_i}{i_i} = \frac{v_i}{v_i - v_o} R_G$$

$$\Rightarrow R_G = 26 R_{in} = 13 \text{ M}\Omega$$

$$I_D R_D = \left( \frac{1}{2} k_n V_{OV}^2 \right) R_D$$

$$= \frac{1}{2} g_m R_D V_{OV} = 12.5 V_{OV}$$

and

$$V_{OV} = V_{DD} - V_t - I_D R_D = 4.3 - 12.5 V_{OV}$$

$$\therefore V_{OV} = 0.319 \text{ V.}$$

$$g_m = 319 \mu\text{A} / \text{V}$$

$$R_D = 78.5 \text{ k}\Omega$$

$$V_{DS} = V_{OV} + V_t$$

$$\hat{v}_{GD} = 0 + 26 \hat{v}_i \leq V_t$$

$$\therefore |\hat{v}_i| < \frac{V_t}{26} = 27 \text{ mV.}$$

**Ex: 5.24**

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{SG} - |V_t|)^2$$

$$= \frac{1}{2} \times 60 \times \frac{16}{0.8} \times (1.6 - 1)^2$$


$$I_D = 216 \mu\text{A}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 216}{1.6 - 1} = 720 \mu\text{A/V}$$

$$= 0.72 \text{ mA/V}$$

$$\lambda = 0.04 \Rightarrow V_A' = \frac{1}{\lambda} = \frac{1}{0.04} = 25 \text{ V}/\mu\text{m}$$

$$r_o = \frac{V_A' \times L}{I_D} = \frac{25 \times 0.8}{0.216} = 92.6 \text{ k}\Omega$$

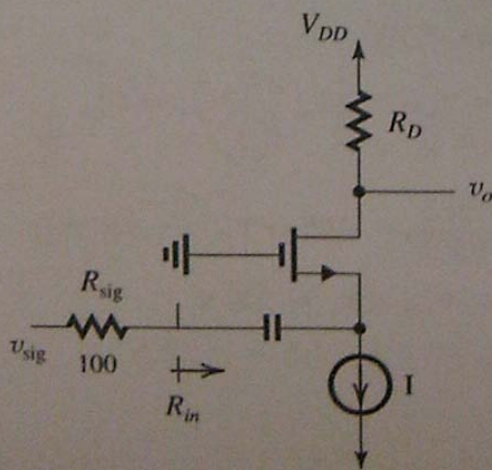**Ex: 5.29**

$$R_{in} = \frac{1}{g_m} = R_{sig} = 100 \Omega$$

$$\Rightarrow g_m = 10 \text{ mA/V}$$


$$g_m = \frac{2I_D}{V_{OV}} = \frac{2I_D}{0.2\text{V}} \Rightarrow I_D = 1 \text{ mA}$$

$$G_V = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} g_m R_D$$

$$= \left(\frac{1}{2}\right) (10 \text{ mA/V}) (2 \text{ k}\Omega)$$

$$= +10$$

Ex: 5.40

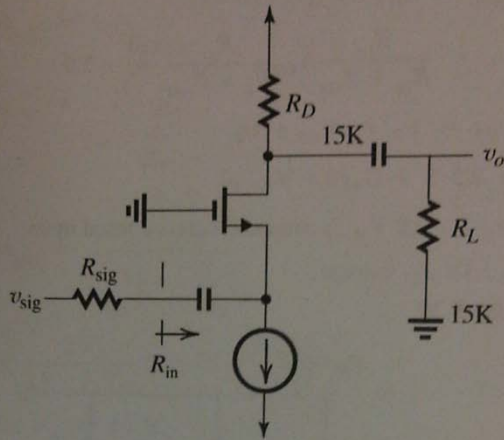

$$g_m = 1 \text{ mA/V}$$

For  $R_{sig} = 50 \Omega$

$$k_{in} = \frac{1}{g_m} = 1 \text{ k}\Omega$$


$$k_{out} = R_D = 15 \text{ k}\Omega$$

$$A_{vO} = +g_m R_D = +15$$

$$A_V = g_m (R_D \parallel R_L) = +7.5$$

$$G_V = \frac{R_{in}}{R_{sig} + R_{in}} A_V = 7.1$$

5.47

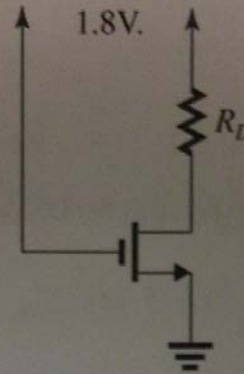

$$k'_n = 0.4 \text{ mA/V}^2$$

$$V_t = 0.5 \text{ V},$$


$$\lambda = 0$$

sat. boundary  $V_{GD} = 0.5 \text{ V}, = I_D R_D$

$$0.5 \text{ V}, = \frac{1}{2} k'_n \frac{W}{L} (1.8 - 0.5)^2 R_D$$

$$\therefore \frac{W}{L} R_D = 1.48 \text{ k}\Omega$$

5.49

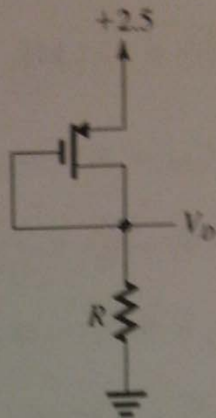

$$V_t = -0.6\text{V}$$

$$k_n' = 100 \mu\text{A}/\text{V}^2$$

$$L = 0.25 \mu\text{m}$$

$$\lambda = 0$$

$$\text{make } i_D = 0.8 \text{ mA}, V_D = 1.5 \text{ V},$$

$$R = \frac{1.5 \text{ V}}{0.8 \text{ mA}} = 1.875 \text{ k}\Omega \quad V_{SO} = +1\text{V}$$

$$0.8\text{mA} = \frac{1}{2} k_n' \frac{W}{L} (1 - 0.6)^2$$


$$\frac{W}{L} = 100$$

$$W = 25 \mu\text{m}$$

5.56 All parts  $k_n' = 0.5 \frac{\text{mA}}{\text{V}^2}$ ,  $V_t = 0.8\text{V}$ ,

$\lambda = 0$

(a)

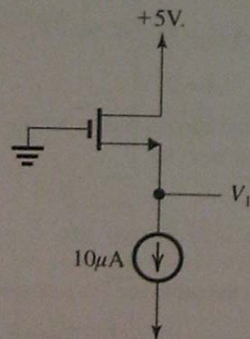

$$V_1 = -V_{GS} = -\sqrt{\frac{(2)(10 \mu\text{A})}{0.5 \text{ mA/V}^2}} - 0.8\text{V}.$$

$$= -1\text{V}.$$


(b) same as (a), except  $i_D = 100 \mu\text{A}$

$$V_2 = -1.432 \text{ V},$$

(c) same as (a), except  $i_D = 1 \text{ mA}$

$$V_3 = -2.80 \text{ V}.$$

h

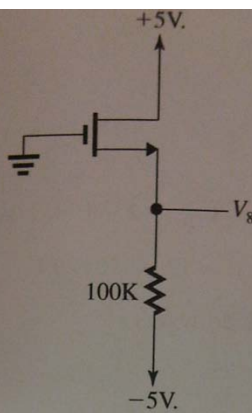

$$V_8 = -V_{GS} = -5 + 100K I_D$$

$$V_{GS} = 5 - (100)\left(\frac{1}{2}\right)(0.5) [V_{GS} - 0.8]^2$$


$$0 = 5 - 25(V_{GS} - 0.8)^2 - V_{GS}$$

see soln, in (f)

$$V_{GS} = +1.19 \text{ V}, \quad I_D = 38.1 \mu\text{A}$$

$$V_8 = -V_{GS} = -1.19 \text{ V}.$$

(b)

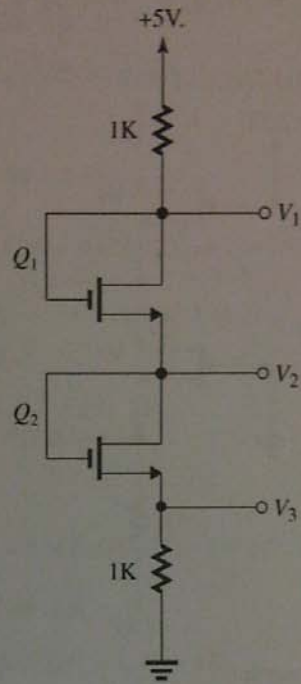

Both  $Q_1$  and  $Q_2$  in sat.

$$(V_{GD1} = V_{GD2} = 0)$$

$\therefore$  both  $Q_1$  and  $Q_2$  have same  $V_{GS}$

$$+5 - 1\text{k}I_D - V_{GS} - V_{GS} - 1\text{k}I_D = 0$$

$$5 - (2)\left(\frac{1}{2}\right)(5)[V_{GS} - 1]^2 - 2V_{GS} = 0$$

$$0 = -5V_{GS}^2 + 8V_{GS}$$

$$V_{GS} = +1.60\text{V}, \text{ (bad root } < V_t \text{)}$$

$$I_D = 0.90\text{mA} = \frac{1}{2}\left(5\frac{\text{mA}}{\text{V}^2}\right)[1.6 - 1]^2$$


$$V_1 = +5 - (1\text{k})I_D = +4.1\text{V}$$

$$V_2 = V_1 - V_{GS} = +2.5\text{V}$$


$$V_3 = V_2 - V_{GS} = (1\text{k})I_D = 0.9\text{V}$$



5.76

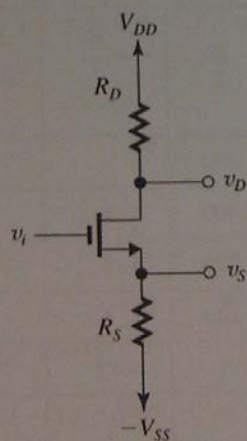

5.76 continues here

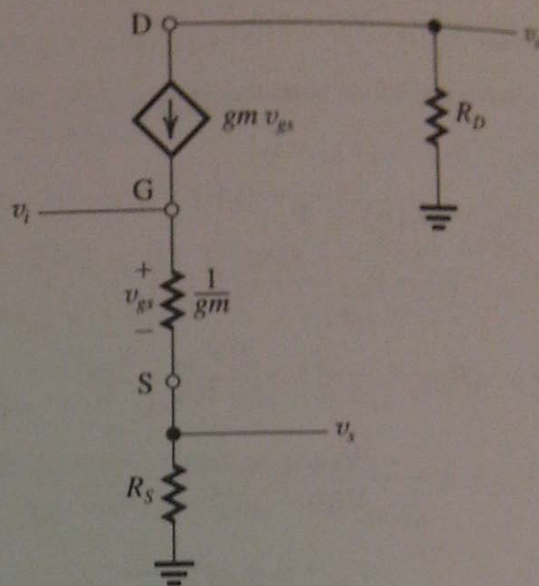

$$v_i = (g_m v_{gs}) \left( \frac{1}{g_m} + R_S \right)$$

$$v_d = -g_m v_{gs} R_D$$

$$v_s = +g_m v_{gs} R_S$$

$$\therefore \frac{v_s}{v_i} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{+g_m R_S}{1 + g_m R_S}$$

$$\frac{v_d}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$

5.79  $V_t = 1V, k'_n = \frac{W}{L} = 2 \text{ mA/V}^2$

(a) dc analysis  $V_G = \frac{5}{15} 15V = 5V$ , assume

$I_D = 1 \text{ mA}$

$V_S = 3V, V_{GS} = 2V, V_{OV} = 1V.$


$I_D = \frac{1}{2} k'_n V_{OV}^2 = 1 \text{ mA (check)}$

$$V_D = V_{DD} - I_D R_D = 7.5V.$$

$$(b) r_o = \frac{V_A}{I_D} = \frac{100V}{1mA} = 100k\Omega$$

$$g_m = \sqrt{2k_n I_D} = 2mS$$

(c)

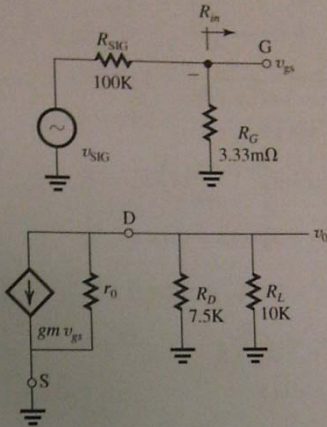


$$(d) R_{in} = R_G = 3.33M\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = 0.97$$

$$\frac{v_o}{v_{gs}} = -g_m(r_o \parallel R_D \parallel R_L) = -8.2$$

$$\frac{v_o}{v_{sig}} = -8.0$$

5.88

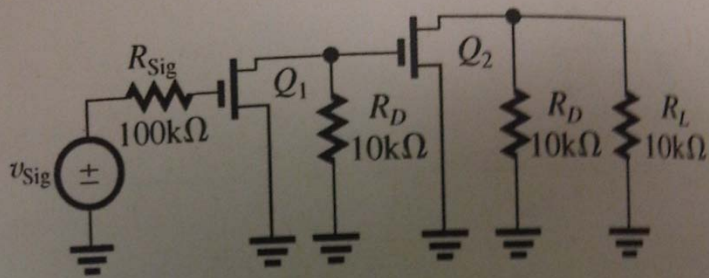

$$\text{For } Q_1 \text{ and } Q_2: I_D = 0.25mA$$


$$V_{OV} = 0.25V \Rightarrow g_{m1,2} = \frac{2 \cdot 0.25mA}{0.25V}$$

$$= \frac{2mA}{V}$$

$$V_A \text{ very large} \Rightarrow r_{o1,2} = \infty$$

This figure belongs to 5.88

a)

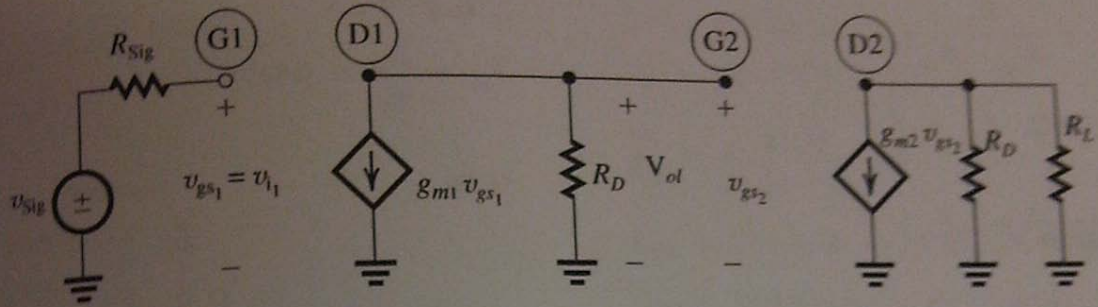

b) Overall  $G_V = G_{V1} \cdot G_{V2}$

$$G_{V1} = -g_{m1} \cdot (\infty \parallel R_D)$$

$$= \frac{-2 \text{ mA}}{\text{V}} \cdot 10 \text{ k}\Omega = -20 \text{ V/V}$$

$$G_{V2} = -g_{m2} \cdot (\infty \parallel R_D \parallel R_L)$$

$$= \frac{-2 \text{ mA}}{\text{V}} \cdot (10 \text{ K} \parallel 10 \text{ K})\Omega = -10 \text{ V/V}$$

$$\Rightarrow G_V = (-20) \cdot (-10) = 200 \text{ V/V}$$


5.90  $g_m = 5 \text{ mS}$

$$i_d = g_m v_{gs} = \frac{g_m}{1 + g_m R_s} v_g$$

$$\frac{g_m}{1 + g_m R_s} = 1 \text{ mS}$$

$$\therefore R_s = \frac{4}{g_m} = 800 \Omega$$

\*D5.113

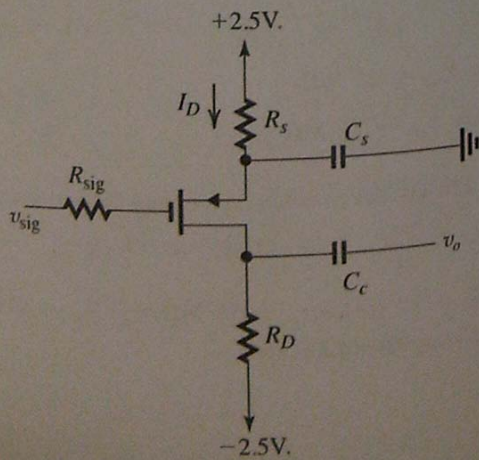

$$V_{tp} = -0.7\text{V}, \quad V_A \rightarrow \infty$$

$$\text{a) for } I_D = 0.3 \text{ mA}, |V_{OV}| = 0.3 \text{ V.}$$

$$V_{SG} = 1.0 \text{ V}, \quad V_G = 0$$

$$V_S = 2.5 - I_D R_S = 1.0 \text{ V.}$$

$$\therefore R_S = 5.0 \text{ k}\Omega$$

$$\text{b) } g_m = \frac{2I_D}{V_{OV}} = 2 \text{ mS}$$

$$G_V = \frac{v_o}{v_{sig}} = -g_m R_D = -10$$

$$\therefore R_D = 5.0 \text{ k}\Omega$$

$$\text{c) } v_{gd} + V_{GD} \geq V_{tp} = -0.7$$

$$-\left| \hat{v}_o + \frac{\hat{v}_o}{10} \right| + 1\text{V} \geq -0.7$$

$$\hat{v}_o \leq 1.55\text{V}_{pk}$$

$$\hat{v}_{sig} \leq \frac{\hat{v}_o, \max}{10} = 0.155\text{V}_{pk}$$

$$\text{d) for } \hat{v}_{sig} = 50 \text{ mV, changed } R_D$$

$$-\left| \hat{v}_o + \frac{\hat{v}_o}{g_m R_D} \right| + (2.5 - I_D R_D) \geq -0.7$$


$$\text{for } g_m = 2 \text{ mS}, I_D = 0.3 \text{ mA}$$

$$-\left| \frac{1 + g_m R_D}{g_m R_D} \right| g_m R_D \hat{v}_{sig} + 2.5 - I_D R_D \geq -0.7$$

$$R_D \leq 7.88 \text{ k}\Omega \quad (\hat{v}_{sig} = 50 \text{ mV})$$

$$G_V = -g_m R_D = -15.8$$

5.115

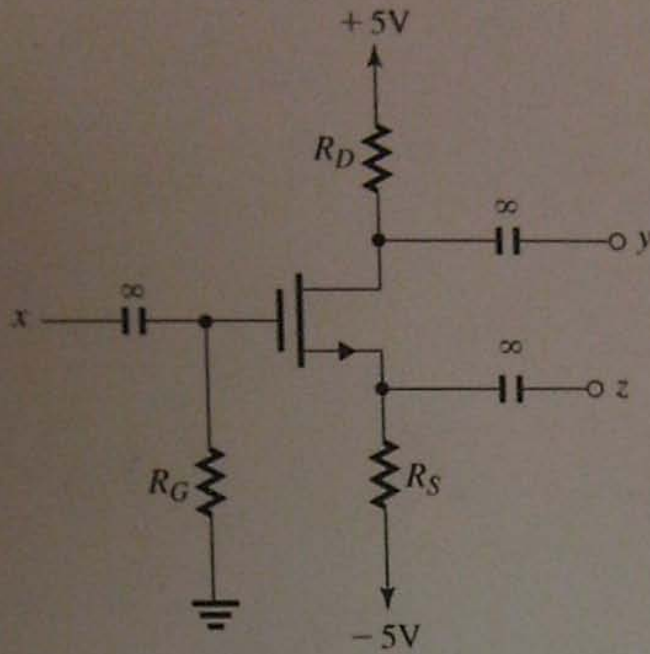

$$V_t = 1\text{V}, \quad k_n = 0.8\text{mA/V}^2$$

$$V_A = 40\text{V}, \quad I_D = 0.1\text{mA}$$

a)  $R_G = 10\text{M}\Omega$

$$V_{OV} = \sqrt{\frac{2I_D}{k_n}} = 0.5\text{V}$$

$$V_{GS} = 1.5\text{V}, \quad R_S = 35\text{k}\Omega$$

$$\text{for } V_D = V_S + V_O + 1\text{V} = 0\text{V},$$

$$R_D = 50\text{k}\Omega$$

b)  $g_m = \frac{2I_D}{V_{OV}} = 0.4\text{mS}$

$$r_o = \frac{V_A}{I_D} = 400\text{k}\Omega$$

c)  $G_V = \frac{v_\phi}{v_{sig}} = -\frac{10\text{M}}{1\text{M} + 10\text{M}} g_m$


$$(r_o \parallel R_D \parallel 40\text{K}) = -7.7$$

$$\frac{v_z}{v_x} = \frac{+g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)} = 0.93$$

$$R_{out} = \frac{1}{g_m} \parallel R_S \parallel r_o$$

$$= 2.32 \text{ k}\Omega$$

e)

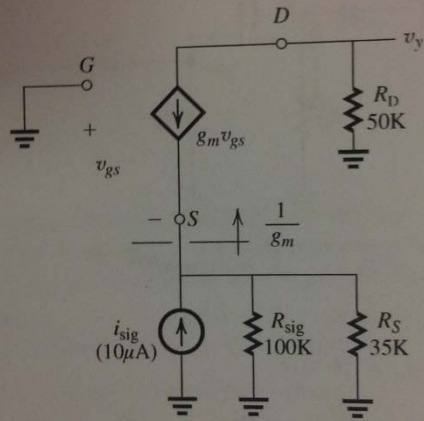

$$v_y = i_{sig} \left[ \frac{1}{g_m} \parallel R_{sig} \parallel R_S \right] g_m R_D$$

$$= (45.6 \text{ k}\Omega) i_{sig}$$

$$= 0.456 \text{ V}$$