

Chapter 5 MOSFETS

Triode Mode

$$I_D = k_n' \left(\frac{W}{L}\right) \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


$n \rightarrow p$ for PMOS

Saturation Mode


$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Typically, we assume $\lambda = 0$ in DC analysis.

$$\lambda = 1/V_A$$

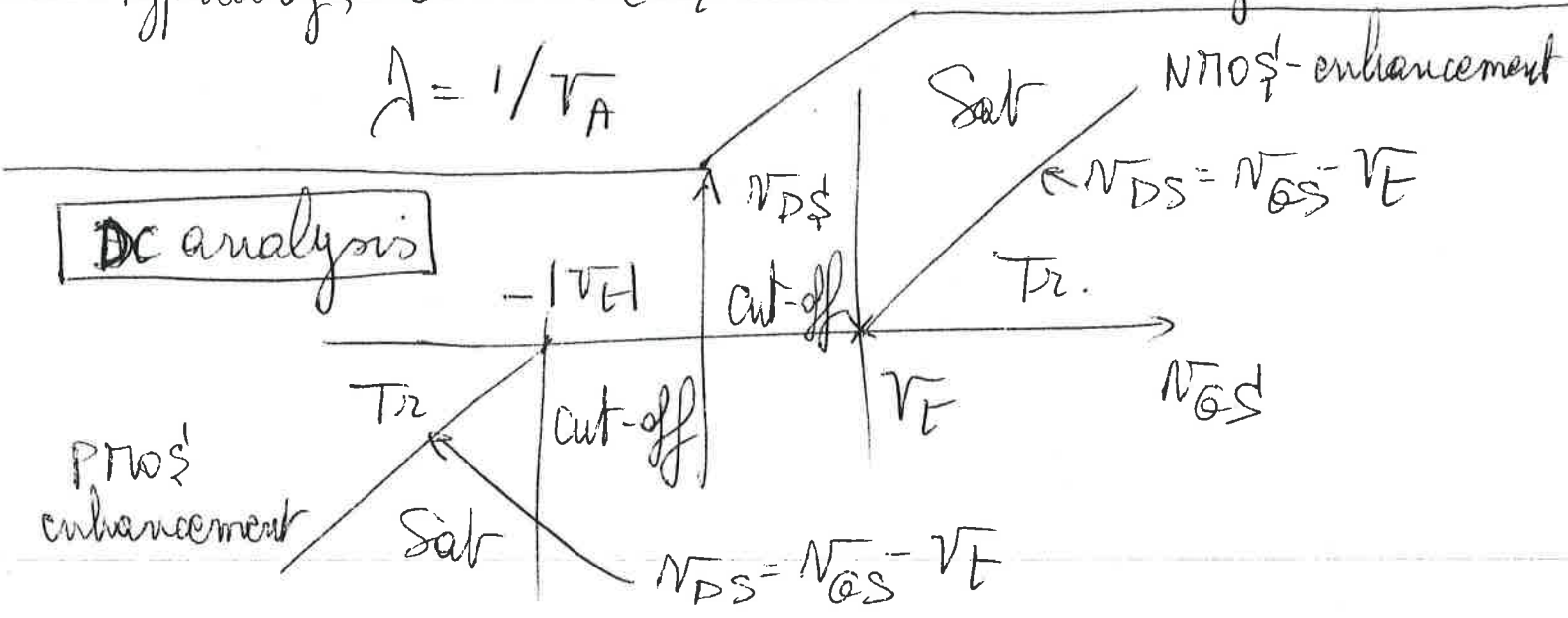


AC analysis

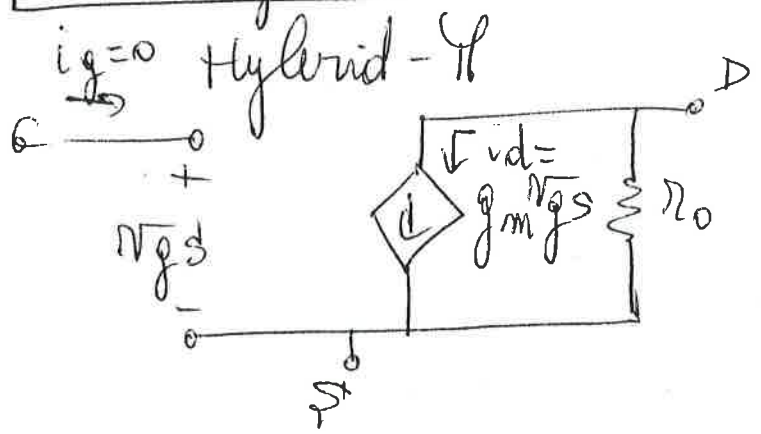

$$g_m = k_n' \frac{W}{L} (V_{GS} - V_T)$$

T-model

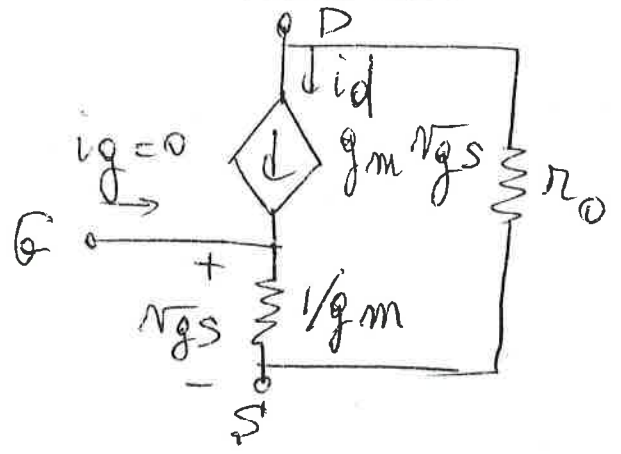

$$r_o = \frac{V_A}{I_D} ; r_o = \infty \text{ if neglected}$$

DC Equations

Chapter 6 BJT

$$|V_{BE}|/V_T$$

$$I_C = I_S e^{V_{BE}/V_T}$$

$$I_B = I_C/\beta$$

$$V_T = 25 \text{ mV at } 300 \text{ K}$$

$$I_C = \alpha I_E$$

$$I_B = I_E/(\beta+1)$$

$$\alpha = \frac{\beta}{\beta+1}$$

$$\beta = \frac{\alpha}{1-\alpha}$$

AC equations

$$v_{be} = v_{\pi} = r_e i_e = r_{\pi} i_b$$

$$r_{\pi} = \frac{V_T}{I_B}$$


$$g_m = \frac{I_C}{V_T}$$

$$i_c = g_m v_{be}$$

$$r_e = \frac{V_T}{I_E}$$

Small signal equivalent circuit

H-model

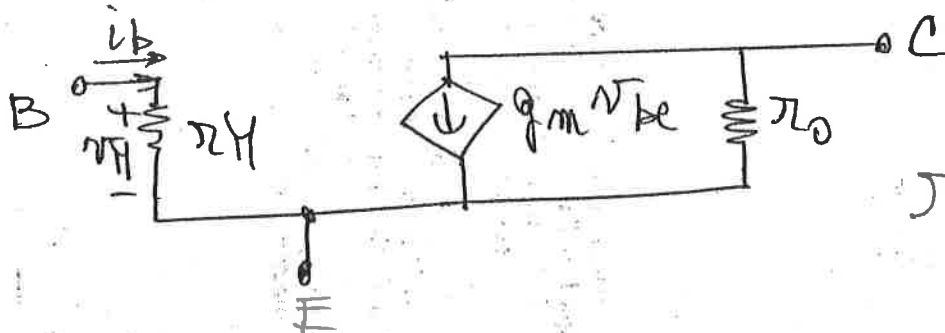

$$r_o = \frac{V_A}{I_C}$$

T-model

