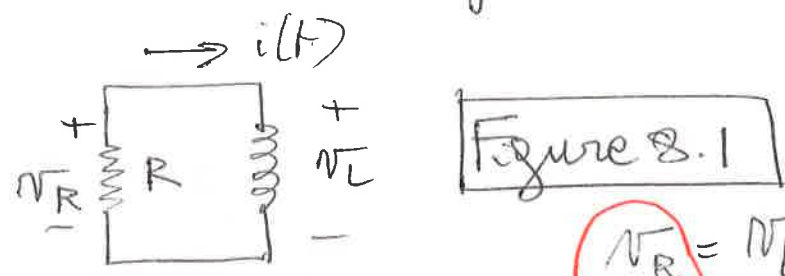


8.1 Source free RL circuit.

→ Homogeneous linear differential equation.
 a diff. eq. in which every term is of the first degree in the dependent variable or one of its derivatives.

Natural response: The response depends on the general "nature" of the circuit.

when we consider independent sources acting on a circuit, part of the response will resemble the nature of the particular solution (This is referred to as the forced response).



Assume $i(t)$ at $t=0$ is $I_0 = i(t=0)$

$$Ri + V_L = Ri + L \frac{di}{dt} = 0$$

$$\begin{aligned} V_R &= V_L \\ -Ri &= L \frac{di}{dt} \end{aligned}$$

or $\frac{di}{dt} + \frac{R}{L} i = 0$

passive sign convention

Direct approach

$$\begin{aligned} \frac{di}{i} &= -\frac{R}{L} dt \\ \int_{I_0}^{i(t)} \frac{di'}{i'} &= \int_0^t -\frac{R}{L} dt' \\ \ln i' \Big|_{I_0}^i &= -\frac{R}{L} (t-0) \end{aligned}$$

$$i(t) = I_0 e^{-\frac{R}{L}t}$$

A more general solution approach (p.258)

Assume $i(t) = A e^{\lambda_1 t}$

where A, λ_1 are constants to be determined.

Substitute $i(t)$ in $\frac{di}{dt} + \frac{R}{L}i = 0$

$$\rightarrow A \lambda_1 e^{\lambda_1 t} + A \frac{R}{L} e^{\lambda_1 t} = 0$$

$$\rightarrow (\lambda_1 + \frac{R}{L}) A e^{\lambda_1 t} = 0$$

This is satisfied if $A=0$, or $\lambda_1 = -\infty$, or $\lambda_1 = -\frac{R}{L}$

\Downarrow
response is zero!

Therefore we must choose $\lambda_1 = -\frac{R}{L}$

$$\rightarrow i(t) = A e^{-\frac{R}{L}t}$$

But $i(0) = I_0 = A$


$$\rightarrow i(t) = I_0 e^{-\frac{R}{L}t}$$

$$\lambda_1 + \frac{R}{L} = 0$$

is called a characteristic equation
It characterizes the natural response of the system

§ 2.2 Properties of the exponential response (p. 262)

128

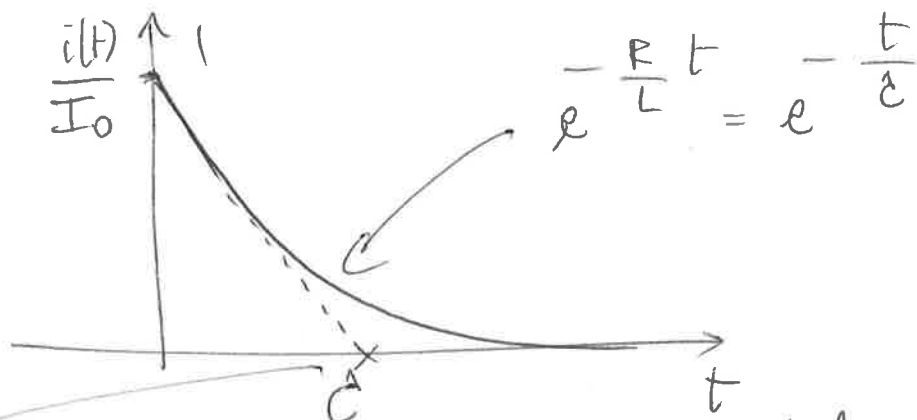

$\tau = \frac{L}{R}$. if $\tau \uparrow$, the exponential takes longer to decay

Initial rate of decay

$$\left. \frac{d}{dt} \left(\frac{i}{I_0} \right) \right|_{t=0} = -\frac{R}{L} e^{-\frac{Rt}{L}} \Big|_{t=0} = -\frac{R}{L}$$

→ can be determined from the display on an oscilloscope!

Other interpretation of τ

$$\frac{i(\tau)}{I_0} = e^{-1} = 0.3679$$

Thus, in one time constant, the response has dropped to $\approx 36.8\%$ of its initial value.


$$\frac{i(t)}{I_0} = 0.1353 \text{ at } t=2\tau$$
$$0.04979 \text{ at } t=3\tau$$
$$0.01832 \text{ at } t=4\tau$$
$$0.006738 \text{ at } t=5\tau$$

If we are asked "How long does it take for the current to decay to zero?" we can answer "about five time constants".

At that point, the current is less than 1% of its original value.

Back to Fig. 8.1

130

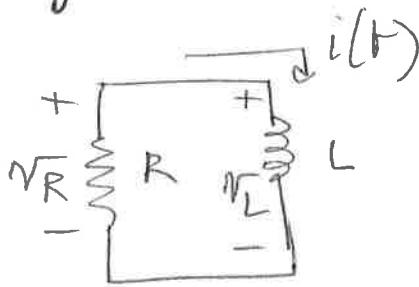

Energy
Instantaneous power; $P_R = R i^2 = I_0^2 R e^{-\frac{2R}{L}t}$

Total energy turned into heat in resistor is



$$W_R = \int_0^{\infty} P_R dt = I_0^2 R \int_0^{\infty} e^{-\frac{2R}{L}t} dt$$

$$W_R = I_0^2 R \left(\frac{-L}{2R} \right) e^{-\frac{2R}{L}t} \Big|_0^{\infty} = \frac{L}{2} I_0^2$$


This is the total energy stored initially in the inductor, at $t=0$; the current through the inductor has dropped to zero at $t=\infty$ and the energy must appear as dissipated in the resistor.

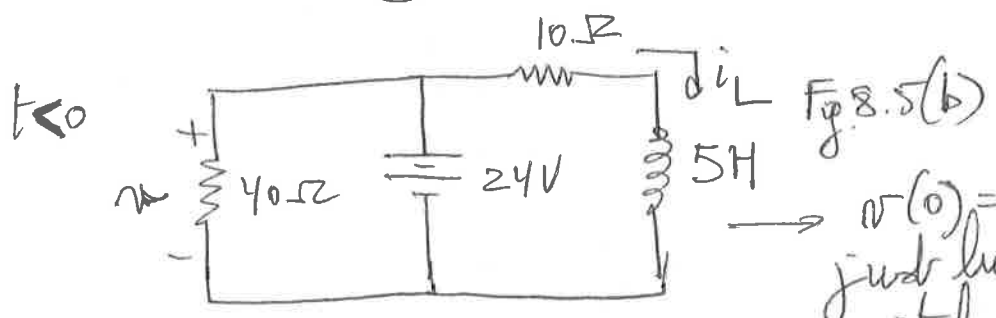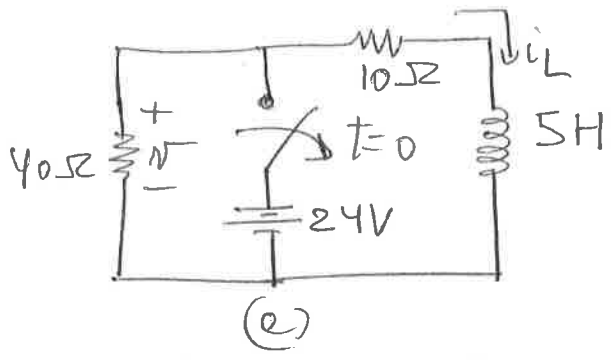Example 8.2 p. 260

For the circuit below, find $v(t=200\mu s)$



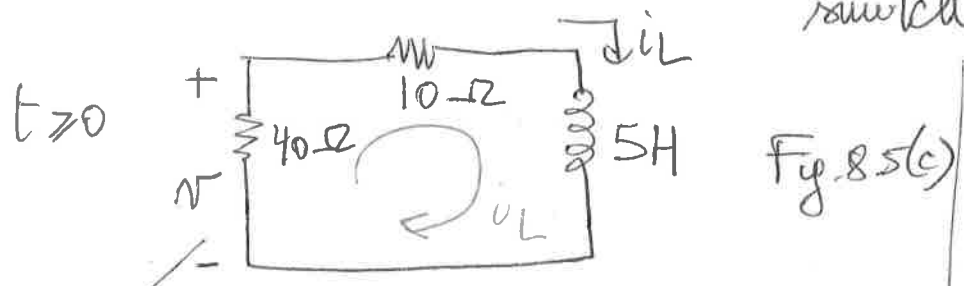$v(0) = 24V$
just before the switch opens.



KVL $\rightarrow -v + 10i_L + 5 \frac{di_L}{dt} = 0$

$$i_L = -v/40$$


$$\frac{5}{40} \frac{dv}{dt} + \left(\frac{10}{40} + 1\right)v = 0$$

$$\frac{dv}{dt} + 10v = 0$$

\hookrightarrow when switch is thrown, only the current through the inductor must remain unchanged.

In Fig 8.5b, $i_L = \frac{24}{10} = 2.4A$
(The inductor acts as a short to a DC current)

From Fig 8.5c)

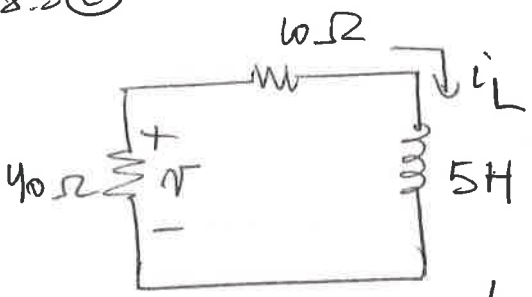

$v(0^+) = 40(-2.4) = -96V!$

$\frac{dv}{dt} + 10v = 0$

$v(t) = A e^{-10t}$

$s + 10 = 0$ is the characteristic equation


$s = -10$


$v(t) = A e^{-10t}$

at $t=0^+$ $v(0^+) = -96V$

$v(t) = -96 e^{-10t}$


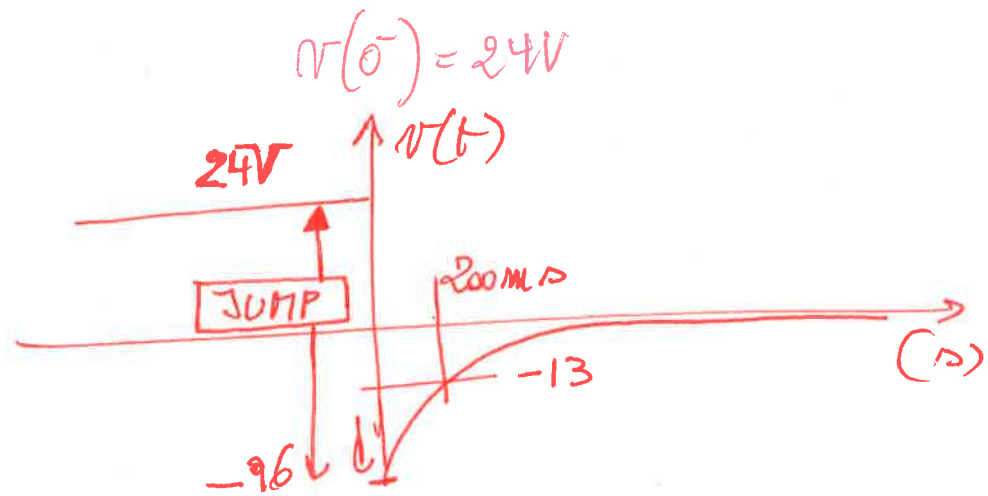
$v(200ms) = -96 e^{-10(0.2)}$
 $= -96 e^{-2} V$
 $= -13V$



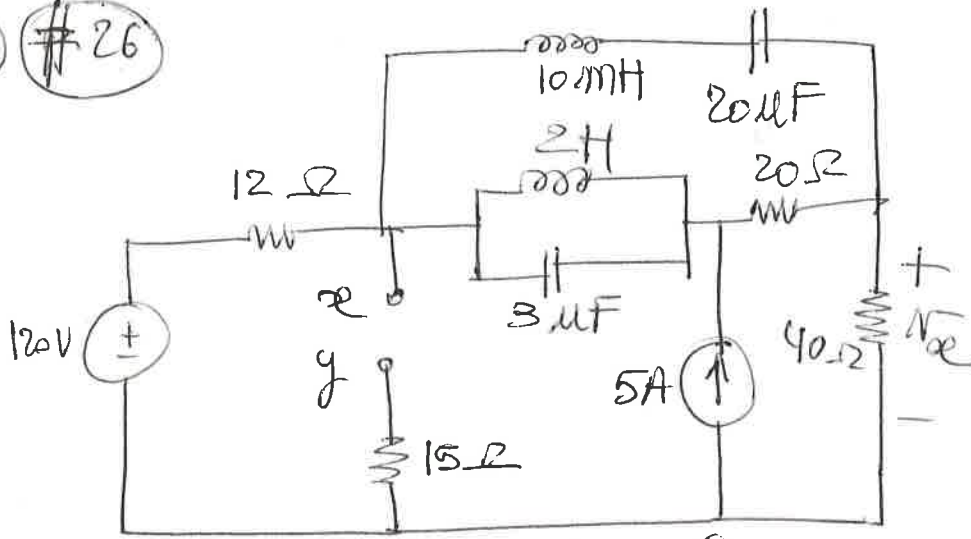

A long time after all connections have been made in the circuit shown above, find V_x if

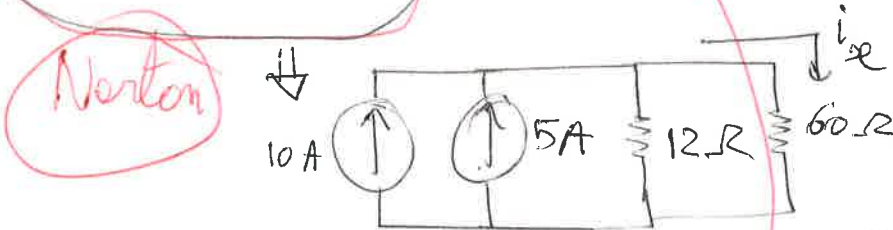
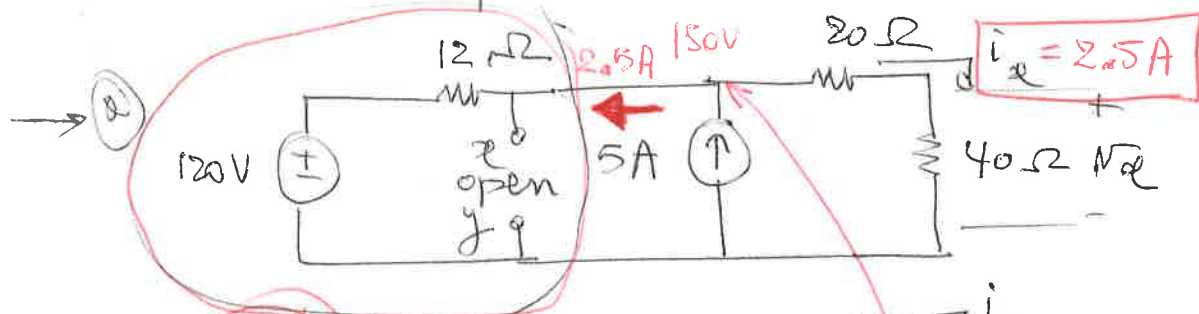
- (a) a capacitor is present between x and y
- (b) an inductor is present between x and y .



$$i_x = \frac{12}{72} \cdot 15A$$

$$i_x = \frac{15A}{6}$$


$$V_x = \frac{40 \cdot 15}{6} = 100V$$

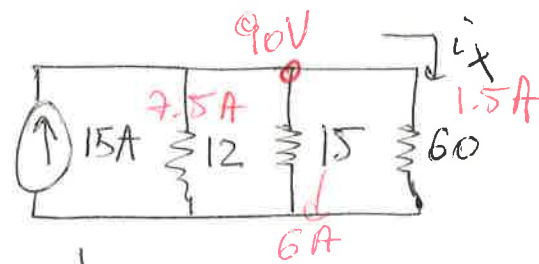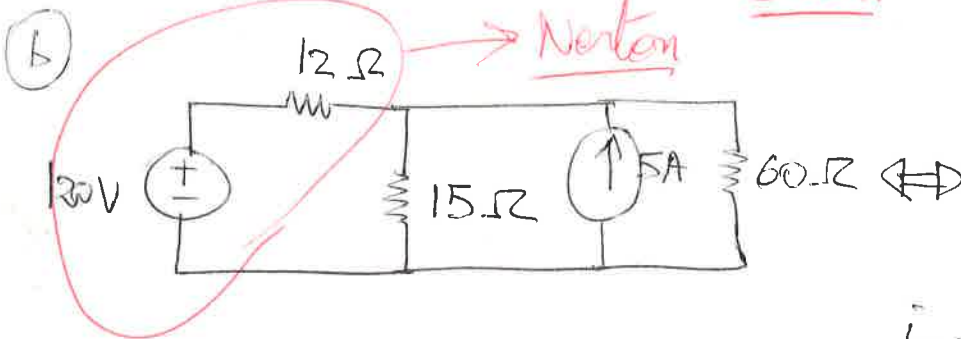

$$i_x = \frac{\frac{1}{60}}{\frac{1}{12} + \frac{1}{15} + \frac{1}{60}} \cdot 15$$




$$i_x = \frac{15}{5+4+1} = 1.5A$$

$$\rightarrow V_x = 60V$$

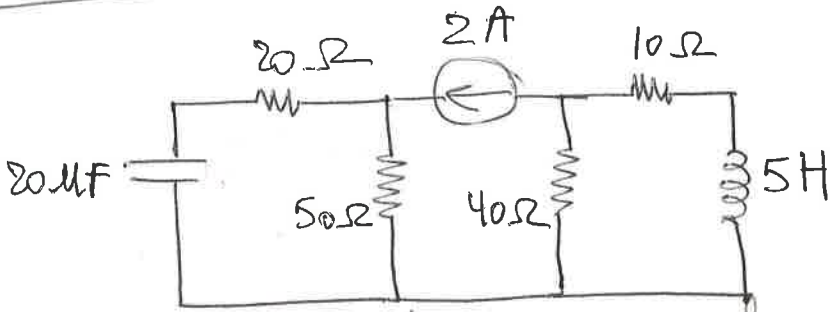

- (a) W_L ?
- (b) W_C ?
- (c) voltage across each circuit element
- (d) current in each circuit element.

Circuit at steady state

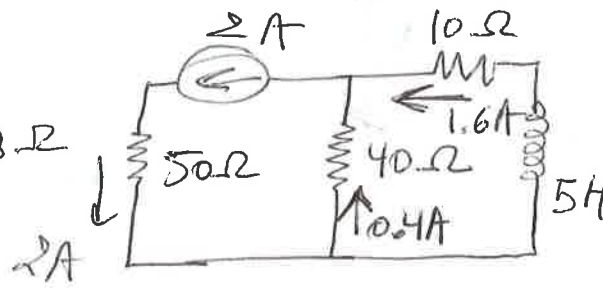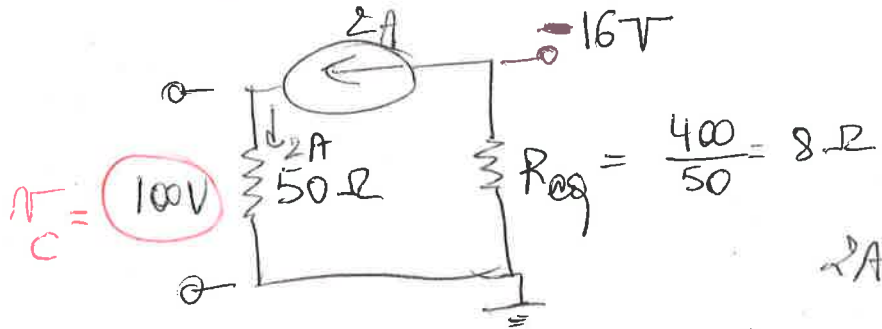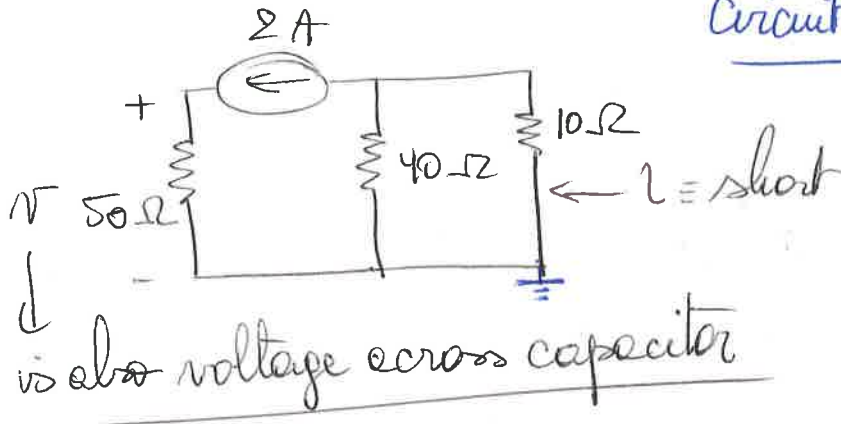

- 16V across 10Ω resistor
 → 1.6A flowing through 10Ω & 5H inductance

$$W_L = \frac{1}{2} L i^2 = \frac{1}{2} \cdot 5 \cdot (1.6)^2 = 6.4 \text{ J}$$

$$W_C = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 20 \cdot 10^{-6} \cdot (10^2)^2 = 10^{-6+4} = 0.1 \text{ J}$$



#28 P 249


135

$$v_s = 400t^2 \text{ V for } t > 0$$

$$i_L(0) = 0.5 \text{ A}$$

at $t = 0.4 \text{ s}$, find values of energy:

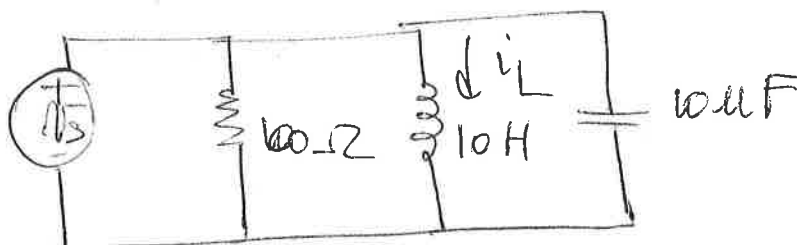- (a) stored in the capacitor
- (b) stored in the inductor
- (c) dissipated by the resistor since $t = 0$.



(c) $P_R = \frac{dW_R}{dt}$

$$W_R(t) - W_R(0) = \int_0^t P_R dt' = \int_0^t dt' R i_R^2(t') = \int_0^t dt' \frac{1}{R} v_s^2(t')$$

(c)

calculate (c) for $t = 0.4 \text{ s}$ $\rightarrow W_R(0.4 \text{ s}) = 3.277 \text{ J}$

(b) $W_C(t) = \frac{1}{2} C v_s^2(t) = \frac{10 \cdot 10^{-6}}{2} [400t^2]^2$ for $t = 0.4 \text{ s}$ (20.48 mJ)

~~(a) $W_L(t) = \frac{1}{2} L i_L^2(t) = \frac{1}{2} L [i_L(t)]^2$~~


$$i_L(t) = i_L(0) + \int_0^t dt' v_s(t')$$

$$W_L(t) = \frac{1}{2} L i_L^2(t) = 9.158 \text{ J}$$

$t = 0.4 \text{ s}$ \uparrow

$\rightarrow i_L(0.4) = 1.3533 \text{ A}$

$i_2(t)$?
 $i_1(t)$? $t > 0$

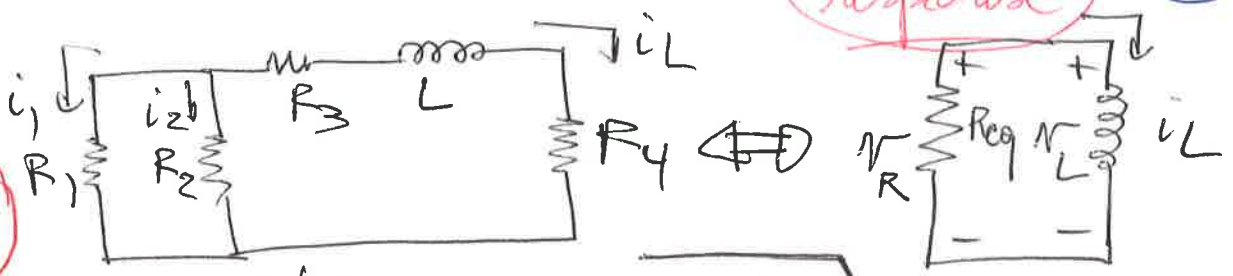

$$R_{eq} = R_3 + R_4 + (R_1 // R_2)$$

Assume at $t = 0_-$, $i_L(0_-)$
 $\rightarrow i_L(t) = i_L(0_-) e^{-\frac{t}{\tau}} = i_L(0_+) e^{-\frac{t}{\tau}}$
 i_2 ? using current divider rule.

$$i_2(t) = \left[\frac{-R_1}{R_1 + R_2} \right] i_L(t) \quad ; \quad i_1(t) = \left[\frac{-R_2}{R_1 + R_2} \right] i_L(t)$$

$$i_2(t) = i_1(t) \frac{R_1}{R_2}$$

$$t > 0 \quad i_2(t) = \left(\frac{-R_1}{R_1 + R_2} \right) i_L(0_+) e^{-t/\tau}$$


$$i_1(t) = \left(\frac{-R_2}{R_1 + R_2} \right) i_L(0_+) e^{-t/\tau}$$

All currents have the same time dependence


Example 8.4 Determine i_1 & i_L for $t > 0$

$i_L(0_-) = 360 \text{ mA}$ ←

137
Show that.

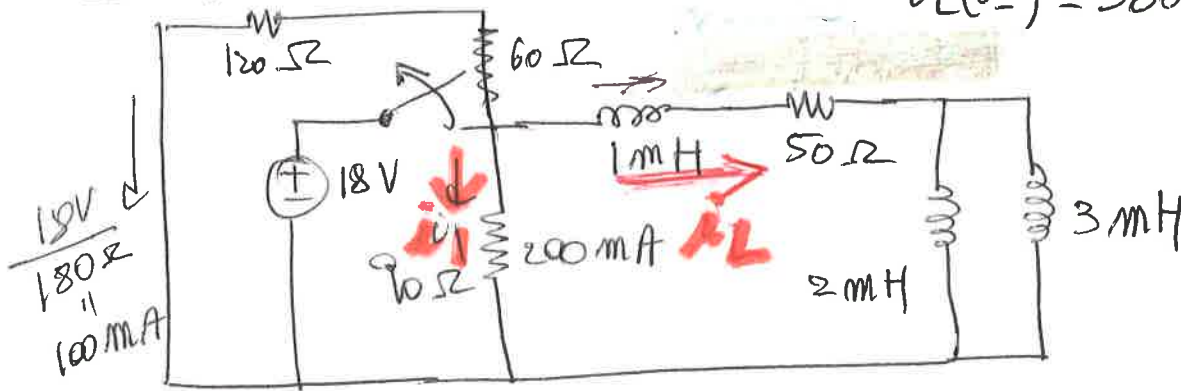

After $t=0$

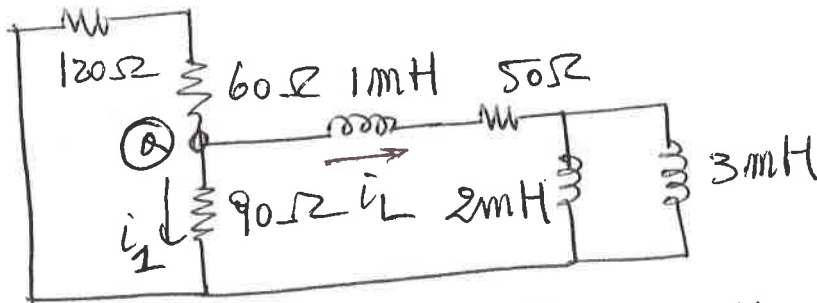

$$l_{eq} = 1 \text{ mH} + \frac{2 \text{ mH} \cdot 3 \text{ mH}}{(2+3) \text{ mH}} = 2.2 \text{ mH}$$

$$R_{eq} = (90 // 180) + 50 = 110 \Omega$$

$$\tau = \frac{l_{eq}}{R_{eq}} = 20 \mu\text{s}$$

natural response is $K e^{-\frac{t}{\tau}}$

Prior to opening switch $i_L = \frac{18 \text{ V}}{50 \Omega} = \frac{18}{50} \text{ A} = 360 \text{ mA}$

$i_L(0_+) = i_L(0_-)$

$\rightarrow i_L(0_-) = 360 \text{ mA} ; i_L(t > 0) = 360 \text{ mA} e^{-\frac{t}{\tau}}$

Current divider rule at node (a)
 $i_1(t=0_+) = \frac{18}{90} = 200 \text{ mA}$
 $i_1(0_+) = \left[\frac{-(120+60)}{120+60+90} \right] i_L(0_+)$


abrupt change in current through resistor

$i_1(0_+) = -240 \text{ mA} ; i_1(t > 0) =$

$e^{-\frac{t}{\tau}}$
 -240 mA

Practice 8.5 p242

At $t = 0.15s$, find i_L, i_1, i_2

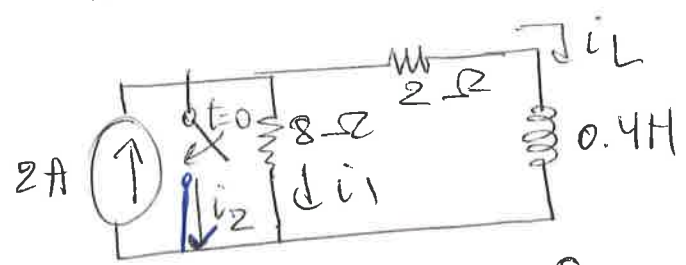


$t < 0 \quad i_L(0^-) = \frac{8}{10} 2A = 1.6A$

$i_1(0^-) = \frac{2}{10} 2A = 0.4A$

$t \geq 0 \quad i_L(0^+) = 1.6A$

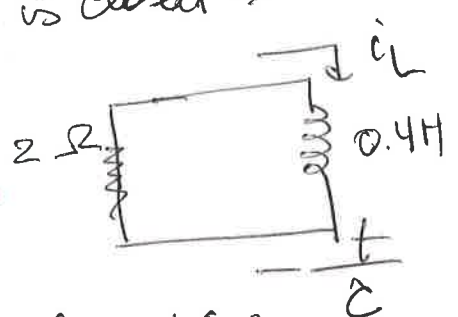$t = 0$ switch is closed $\rightarrow v$ across 8Ω is zero.



Natural response

$i_L(t) = 1.6 e^{-t/\tau}$

$\tau = \frac{L}{R} = \frac{0.4}{2} = 0.2s$

$i_L(0.15s) = 1.6 e^{-\frac{0.15}{0.2}} = 0.756A$

$i_1(0^-) = 0.4A \rightarrow i_1(0^+) = 0$ (8Ω resistor is shorted)

$i_2(0.15s) + i_L(0.15s) = 2A!$
 $i_2(0.15s) = 2 - i_L(0.15s) = 1.244A$

$i_2(0^+) = 0.4A$
 the short takes on all the current which was flowing in 8Ω resistor

$i_L(+\infty) \rightarrow 0$
 $i_2(+\infty) = 2A$

$i_1(t) = 0 \quad \forall t > 0$

$i_2(t) = 2 - i_L(t) = 2 - 1.6 e^{-t/\tau}$