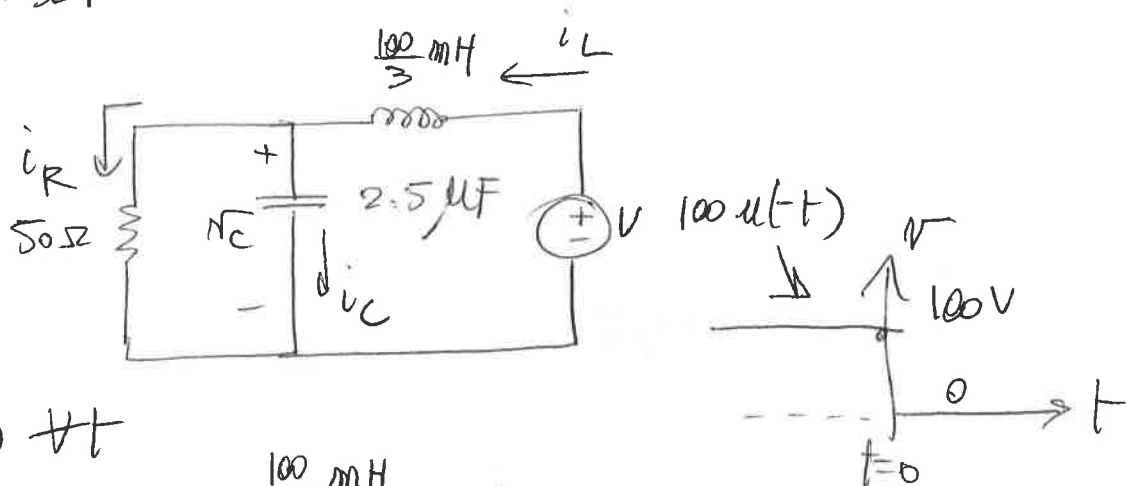


# overdamped parallel RLC circuit


9.21  
179

Problem 16 P. 361



Find  $i_L(t)$  vs  $t$


$t < 0$

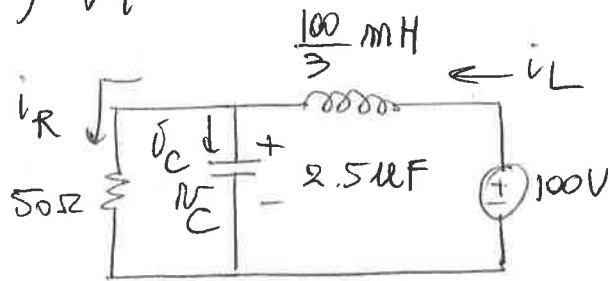

$$\rightarrow v_C(0_-) = 100V \quad i_L(0_-) = i_R(0_-) = \frac{100}{50} = 2A$$

$$v_C(0_-) = v_C(0_+) = 100V$$

$t > 0$

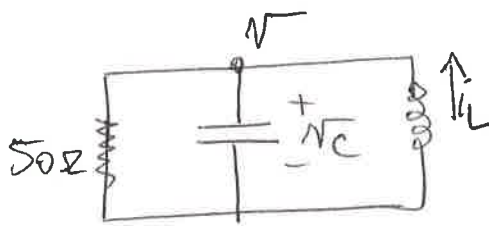

$$i_L(0_+) = 2A = i_L(0_-)$$

$$v_C(0_+) = 100V$$

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0$$

$$v_C(t) = v(t) = ?$$

$$\alpha = \frac{1}{2RC} = 4000 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 3464 \text{ s}^{-1}$$

$\alpha > \omega_0$   
overdamped

(over)

$$v(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$$

$$\lambda_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = \begin{cases} \dots & \lambda^{-1} \\ \dots & \lambda^{-1} \end{cases}$$

$$\lambda_1 - \lambda_2 = 2\sqrt{\alpha^2 - \omega_0^2}$$

$$i_L(t) = i_C(t) + i_R(t)$$

$$i_L(t) = C \frac{dv}{dt} + \frac{v(t)}{R} = C (\lambda_1 A_1 e^{\lambda_1 t} + \lambda_2 A_2 e^{\lambda_2 t}) + \frac{1}{R} (A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t})$$

$$v(t=0_+) = \boxed{A_1 + A_2 = 100}$$

$$\left[ \frac{dv}{dt} \right]_{t=0_+} = \lambda_1 A_1 + \lambda_2 A_2$$

$$i_L(t=0_+) = 2A = 2.5 \cdot 10^{-6} (\lambda_1 A_1 + \lambda_2 A_2) + \frac{1}{50} (A_1 + A_2)$$

$$\cancel{2A} = 2.5 \cdot 10^{-6} (\lambda_1 A_1 + \lambda_2 A_2) + \cancel{2A}$$

$$\rightarrow \boxed{\lambda_1 A_1 + \lambda_2 A_2 = 0}$$

$$A_2 = 100 - A_1$$


$$\lambda_1 A_1 + \lambda_2 (100 - A_1) = 0 \rightarrow (\lambda_1 - \lambda_2) A_1 = -100 \lambda_2$$

$$\Rightarrow \left. \begin{aligned} A_1 &= \frac{-100 (-\alpha - \sqrt{\alpha^2 - \omega_0^2})}{2 \sqrt{\alpha^2 - \omega_0^2}} = 50 \left( \frac{\alpha + \sqrt{\alpha^2 - \omega_0^2}}{\sqrt{\alpha^2 - \omega_0^2}} \right) \\ A_2 &= 100 - A_1 \end{aligned} \right\}$$

# Underdamped Parallel RLC circuit



#32 P. 363

9-23  
181

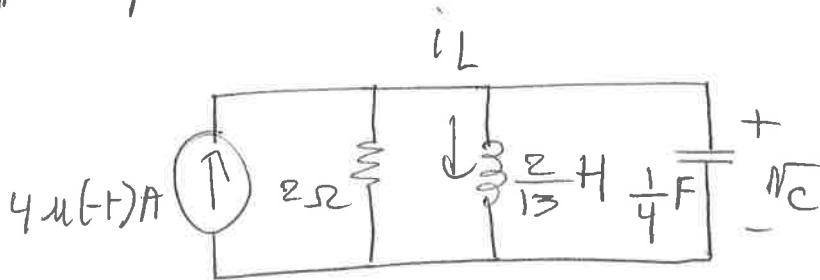

(a)  $i_L(0_+)$ ; (b)  $v_C(0_+)$ ; (c)  $\left. \frac{di_L}{dt} \right|_{t=0_+}$

(d)  $\left. \frac{dv_C}{dt} \right|_{t=0_+}$ ; (e)  $v_C(t)$ ; sketch  $v_C(t)$ ,  $-0.1 < t < 2$ .

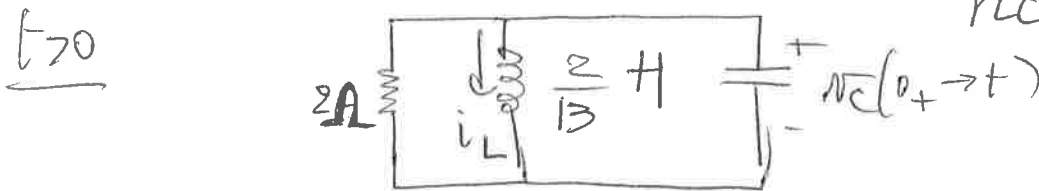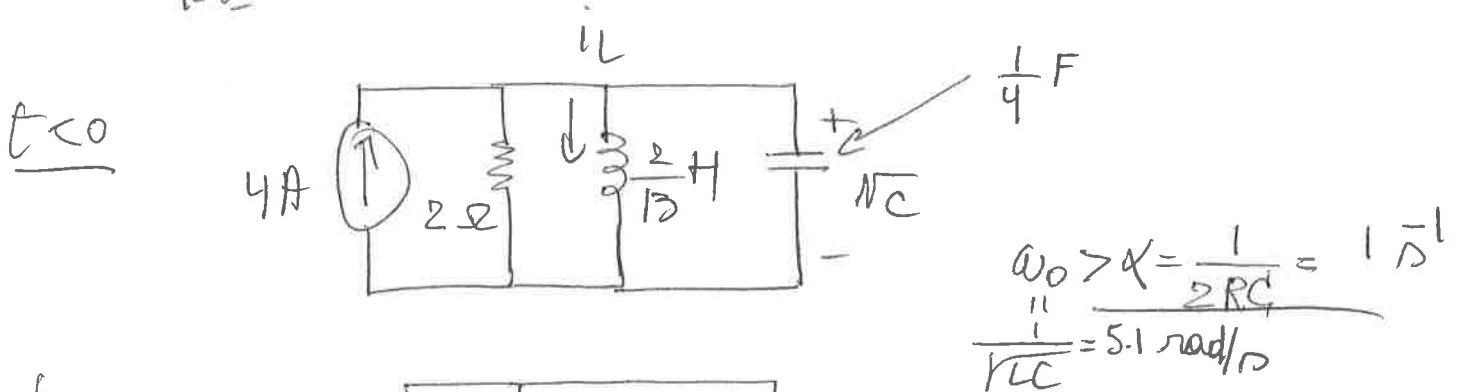

$t < 0$   $i_L(0_-) = 4A$ ,  $i_R(0_-) = 0 = i_C(0_-)$

(a)  $i_L(0_+) = 4A$   $v_C(0_-) = 0 \rightarrow v_C(0_+) = 0$  (b)

$\left. \frac{di_L}{dt} \right|_{t=0_+}$  ?  $i_L(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 5 \text{ rad/s}$   
 $-\alpha t$

$i_L(0_+) = 4A = B_1 \rightarrow i_L(t) = e^{-\alpha t} (4 \cos \omega_d t + B_2 \sin \omega_d t)$

$v_L = v_C = L \frac{di_L}{dt} = L \left( -\alpha e^{-\alpha t} 4 \cos \omega_d t - 4 e^{-\alpha t} \omega_d \sin \omega_d t - \alpha e^{-\alpha t} B_2 \sin \omega_d t + B_2 e^{-\alpha t} \omega_d \cos \omega_d t \right)$

$$v_c(t=0_+) = L(-4\alpha + B_2 \omega_d)$$

$$v_c(t=0_+) = v_c(t=0_-) = 0$$

$$\rightarrow -4\alpha + B_2 \omega_d = 0$$

$$\boxed{B_2 = \frac{4\alpha}{\omega_d}}$$


$$\left. \frac{dv_c}{dt} \right|_{t=0_-} = 0, \quad v_c(t) = L \left( \begin{aligned} & 4\alpha e^{-\alpha t} \cos \omega_d t \\ & - 4\omega_d e^{-\alpha t} \sin \omega_d t \\ & - B_2 \alpha e^{-\alpha t} \sin \omega_d t \\ & + B_2 \omega_d e^{-\alpha t} \cos \omega_d t \end{aligned} \right)$$

$$v_c(t) = L e^{-\alpha t} \left( \begin{aligned} & -4\alpha \cos \omega_d t + B_2 \omega_d \cos \omega_d t \\ & - 4\omega_d \sin \omega_d t - B_2 \alpha \sin \omega_d t \end{aligned} \right)$$

$$v_c(t) = -L e^{-\alpha t} \left( 4\omega_d \sin \omega_d t + B_2 \alpha \sin \omega_d t \right)$$

$$v_c(t) = -L e^{-\alpha t} \sin \omega_d t \left( 4\omega_d + \frac{4\alpha^2}{\omega_d^2} \right)$$

why is it < 0?

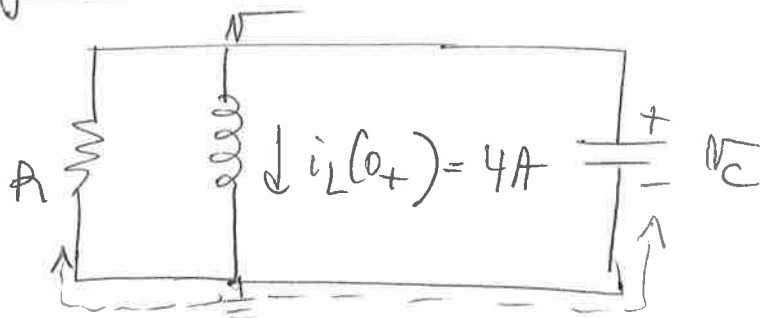


$v$  goes negative

#24

A parallel RLC circuit is constructed using a 1mH inductor and a 12μF capacitor.

Ⓐ Select R such that the circuit response is critically damped. How can this be?

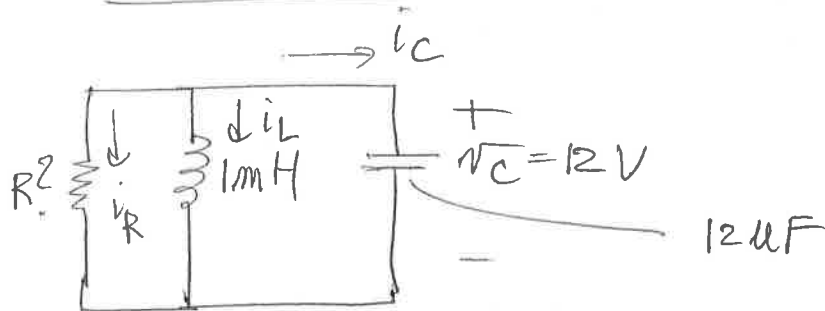Ⓑ If  $v_C(0_-) = 12V$   $i_L(0_-) = 0$ , find  $v_C(t)$  for  $t > 0$ .



$$\text{Ⓐ } \alpha = \omega_0 \rightarrow \frac{1}{2RC} = \frac{1}{\sqrt{LC}} \rightarrow R = \frac{\sqrt{LC}}{2C} = \frac{1}{2} \sqrt{\frac{L}{C}}$$

$$R = \frac{1}{2} \sqrt{\frac{10^{-3}}{12 \cdot 10^{-6}}} = \frac{1}{2} \sqrt{\frac{10^3}{12}}$$

$$\boxed{R_c = 4.56 \Omega}$$

Ⓑ critically damped  $v(t) = e^{-\alpha t} (A_1 t + A_2)$

$$v_C(0_-) = 12V = v_C(0_+) = A_2$$

$$\rightarrow \boxed{A_2 = 12V}$$

$$i_L(0_-) = 0 \Rightarrow i_L(0_+) = 0A \quad i_R(0_-) = \frac{12V}{R_c} \approx 2.63A$$

$$i_R(0+) + i_L(0+) + i_C(0+) = 0$$

$$i_C(0+) = -i_R(0+) = \frac{-12}{R_C} \quad A = -2.63 \text{ A}$$

$$v(t) = e^{-\alpha t} (A_1 t + A_2)$$

$$i_C = C \frac{dv}{dt} = C \left[ -\alpha e^{-\alpha t} (A_1 t + A_2) + e^{-\alpha t} A_1 \right]$$

$$i_C(0+) = C [-\alpha A_2 + A_1]$$


$$\frac{-12}{R_C} = C [-\alpha A_2 + A_1]$$


$$\rightarrow A_1 - 12\alpha = \frac{-12}{R_C}$$

$$A_1 = 12 \left[ \alpha - \frac{1}{R_C} \right] = 12 \left[ \frac{1}{2R_C C} - \frac{1}{R_C} \right]$$

$$A_1 = \frac{-12}{2R_C C} = \frac{-6}{R_C C}$$
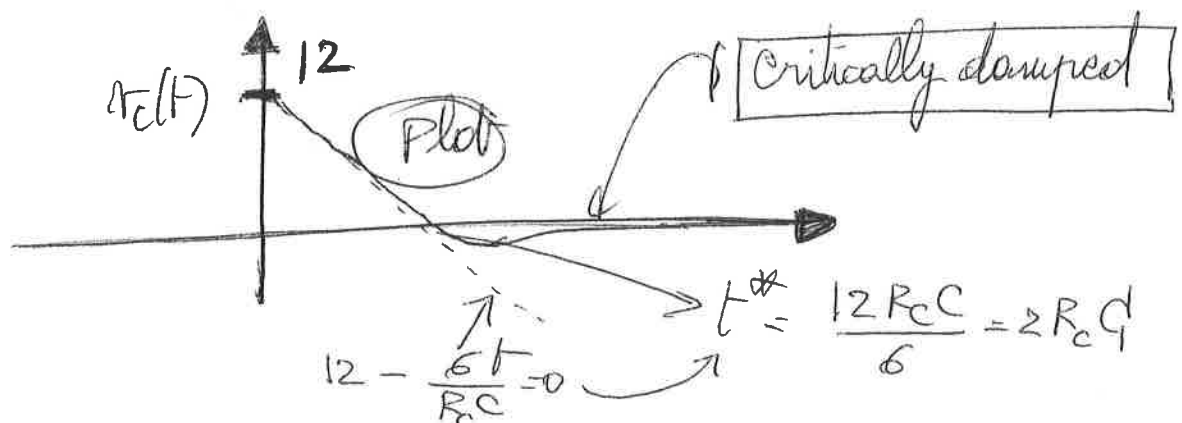
$$v_C(t) = e^{-\alpha t} \left( \frac{-6}{R_C C} t + 12 \right)$$




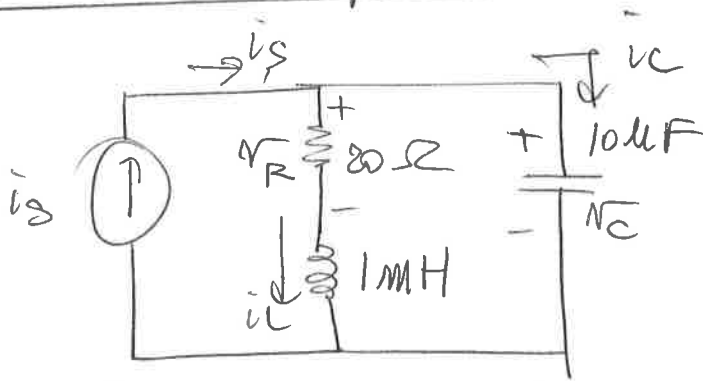

$$i_s = [10 \mu(-t) - 20 \mu(t)] \text{ A}$$

$i_L(t)$

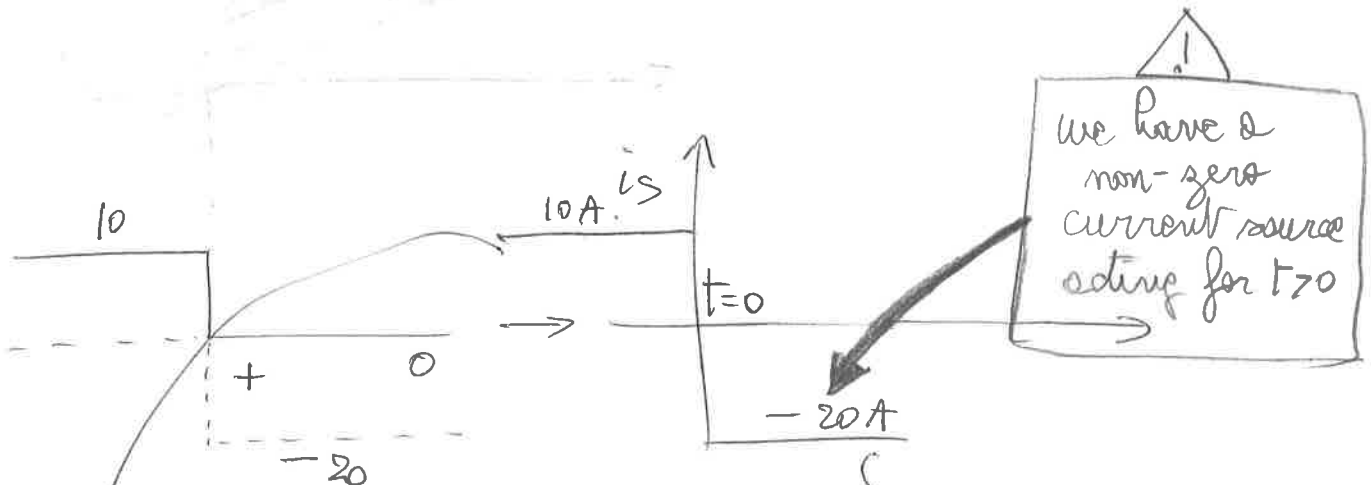- (a)  $i_L(0_-)$  (b)  $v_C(0_+)$ ; (c)  $v_R(0_+)$ ; (d)  $i_L(\infty)$ ,  $i_L(0.1 \text{ ms})$ ?



$$i_L(0_-) = 10 \text{ A}!$$


$$v_C(0_+) = v_C(0_-) = 10 \text{ A} \cdot 20 \Omega = 200 \text{ V}$$

$$v_R(0_+) = v_C(0_+) = 200 \text{ V} \quad \leftarrow \quad i_L(0_+) = i_L(0_-)$$

$$i_L(\infty) = -20 \text{ A} \leftarrow$$

$$v_C(t) = v_R + L \frac{di_L}{dt}$$

$$v_C(t) = R i_L + L \frac{di_L}{dt}$$

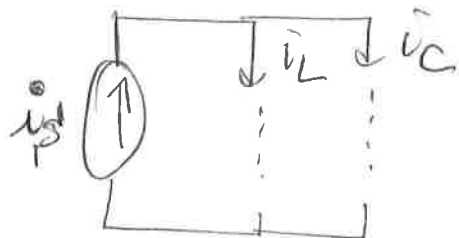

$$i_L + i_C = i_s$$

$$i_C = C \frac{dv_C}{dt} = -20 - i_L; \quad v_C = Ri_L + L \frac{di_L}{dt}$$

$$\frac{dv_C}{dt} = R \frac{di_L}{dt} + L \frac{d^2 i_L}{dt^2}$$

$$\frac{-20 - i_L}{C}$$

$$L \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt} + \frac{i_L}{C} = \frac{-20}{C}$$

$$L \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt} + \frac{i_L}{C} = 0 \quad \text{Natural response}$$

$$i(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$$

$$\lambda_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \frac{20}{2 \cdot 10^{-3}} = 10^4 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{10^{-3} \cdot 10 \cdot 10^{-6}}} = \frac{1}{\sqrt{10^{-8}}} = 10^4 \text{ rad s}^{-1}$$

$\alpha = \omega_0$  critically damped

$$i(t) = e^{-\alpha t} (A_1 t + A_2)$$

~~$t=0, i_L(0) = 10, i_C(0) = -10, v_C(0) = 0$~~

(over)



~~$i_L(t) = e^{-\alpha t} (10 + A_1 t)$~~   
 ~~$t \rightarrow \infty \quad i_L(\infty) = -20 A$~~

~~$i_L = i_f + e^{-\alpha t} (10 + A_1 t)$~~   
 Total response.  
 $i_L(t) = i_f + e^{-\alpha t} (A_1 t + A_2)$   
 $t \rightarrow \infty \quad i_L(\infty) = i_f = -20 A$

$i_L(0) = i_L(0+) = 10 = -20 + A_2$   
 $A_2 = 30 A$

$A_1?$   $i_L(t) = -20 + (30 + A_1 t) e^{-\alpha t}$

$v_L(t) = v_R(t) + L \frac{di_L(t)}{dt}$   
 $v_L(0+) = v_R(0+) = 200 V \rightarrow \left. \frac{di_L}{dt} \right|_{0+} = 0$   
 $\rightarrow (A_1 e^{-\alpha t} + (30 + A_1 t)(-\alpha) e^{-\alpha t}) \Big|_{t=0+} = 0$   
 $A_1 + 30\alpha = 0$   
 $A_1 = -30\alpha$


$\rightarrow i_L(t) = -20 + 30(1 + \alpha t) e^{-\alpha t} \rightarrow i_L(0.1 \text{ ms}) = \dots$

# Complete response

9.32


188

#60 p. 366

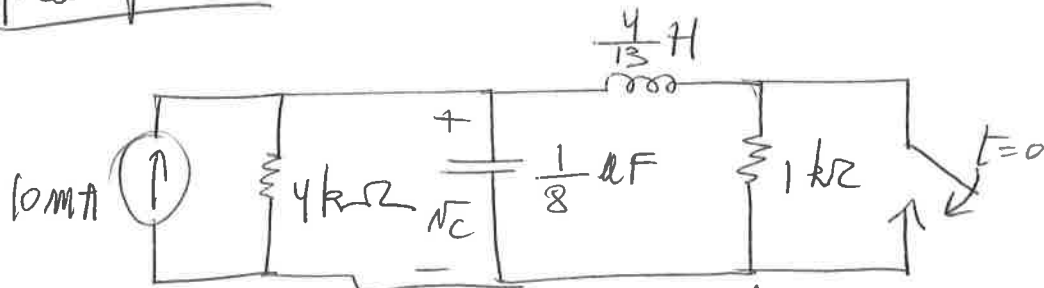

$v_C(t)$  for  $t \geq 0$ ; sketch  $v_C(t)$  for  $-0.1 < t < \infty$


$t < 0$

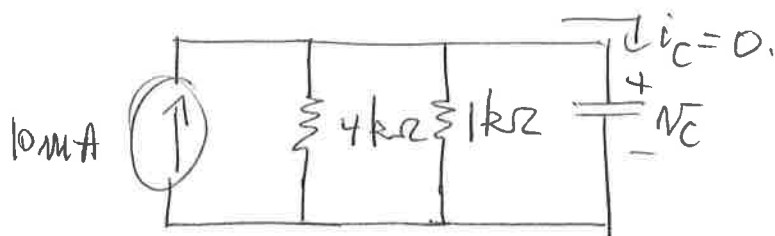

$$i_L(t=0) = \frac{8 \text{ mA}}{5} = \frac{4}{5} \text{ mA}$$

$$v_C = 10 \text{ mA} (4 \text{ k}\Omega // 1 \text{ k}\Omega) = 10 \text{ mA} \frac{4 \text{ k}\Omega}{5} = 8 \text{ V}$$

$t > 0$

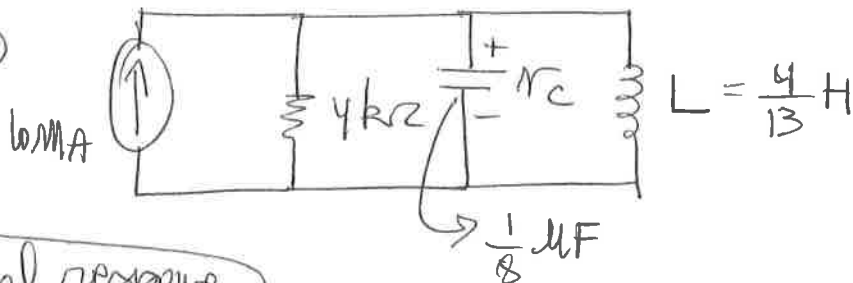

$$i_L(t=\infty) = 10 \text{ mA}$$

Natural response

without 10 mA

$(R, L, C)$  // network

$$\alpha \gtrless \omega_0$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 4 \cdot 10^3 \cdot \frac{1}{8} \cdot 10^{-6}} = 10^3 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{4}{13} \cdot \frac{10^{-6}}{8}}}$$

$$\omega_0 = \frac{10^3}{\sqrt{\frac{1}{26}}} = \sqrt{26} \cdot 10^3 \text{ s}^{-1}$$

$\omega_0 > \alpha$

$$\omega_0 = (5.1) \cdot 10^3 \text{ s}^{-1}$$

underdamped.

$$i_c(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{(26-1)} \cdot 10^3$$

$$\omega_d = 5 \cdot 10^3 \text{ rad s}^{-1}$$

Forced response  $v_f$  is response as  $t \rightarrow \infty$

$t \rightarrow \infty$   $v_L = 0$  L is a short  
10 mA goes through L

$$v_c(\infty) = v_f = 0$$

Total response  $v_c(t) = v_f + e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$

$$v_c(t=0^+) = v_c(t=0^-) = 8V = B_1$$

$B_2$ ?

$$v_c = v = L \frac{di_L}{dt}$$

$$i_L(t) = i_L(0^+) + \frac{1}{L} \int_0^t v_c(t') dt'$$

$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t v_c(t') dt'$$

$$v_c(t) = B_1 e^{-\alpha t} \cos \omega t + B_2 e^{-\alpha t} \sin \omega t$$

9.34

190

$$\int_0^t v_c(t') dt' = ?$$

$$\int e^{\alpha z} \cos bz dz = \frac{e^{\alpha z}}{\alpha^2 + b^2} (\alpha \cos bz + b \sin bz)$$

$$\int e^{\alpha z} \sin bz dz = \frac{e^{\alpha z}}{\alpha^2 + b^2} (\alpha \sin bz - b \cos bz)$$

$$\int_0^{t \rightarrow \infty} v_c(t') dt' = B_1 \left[ -\frac{\alpha}{\alpha^2 + b^2} \right] + B_2 \left[ -\left( \frac{-b}{\alpha^2 + b^2} \right) \right]$$

$$= \frac{b B_2 - \alpha B_1}{\alpha^2 + b^2}$$

$$\rightarrow \underset{\substack{\parallel \\ 10 \text{ mA}}}{i_L(t \rightarrow \infty)} = \underset{\substack{\parallel \\ 8 \text{ mA}}}{i_L(0)} + \frac{1}{L} \left[ \frac{b B_2 - \alpha B_1}{\alpha^2 + b^2} \right]$$

$$\rightarrow \left[ \frac{b B_2 - \alpha B_1}{\alpha^2 + b^2} \right] = L(2 \text{ mA})$$


$B_1$  is known  
 Solve for  $B_2$

# chapter 9

①

Pr 43 page 364

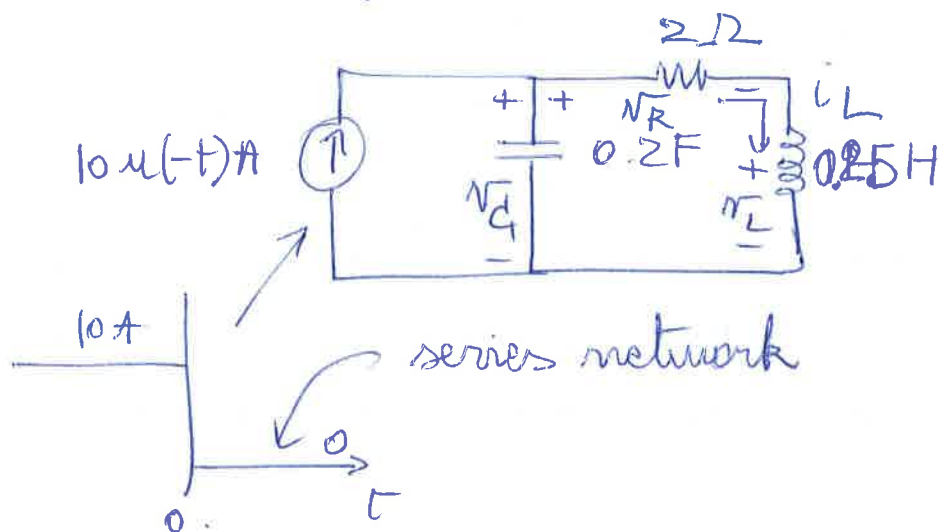Find  $i_L(t)$  for  $t > 0$  in the circuit below



$$v_R + v_L = v_C$$

$$v_C(0^+) = v_R(0^+) + v_L(0^+)$$

$$v_R(0^-) \text{ because } i_L(0^-) = i_L(0^+)$$

$$\alpha^2 < \omega_0^2$$

$$\alpha < \omega_0$$

$$\alpha = \frac{R}{2L} = \frac{2}{1/2} = 4 ; \quad \omega_0^2 = \frac{1}{LC} = \frac{4}{0.2} = 20$$

$\alpha < \omega_0$   
underdamped

$$\omega_d = \sqrt{20 - 16} = \sqrt{\omega_0^2 - \alpha^2} = 2$$

$$i_L = e^{-4t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$i_L(0) = 10A, \quad v_C(0) = 20V$$

$$\downarrow$$

$$A_1 = 10$$

$$i_L'(0^+) = \frac{1}{L} v_L(0^+) = \frac{1}{L} (v_C(0^+) - v_R(0^+))$$

$$i_L'(0^+) = 4(20 - 20) = 0$$


$$i_L' = -4e^{-4t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$+ e^{-4t} (-2A_1 \sin 2t + 2A_2 \cos 2t)$$

$$i_L'(0) = -4A_1 + 2A_2 = 2A_2 - 40 = 0 \Rightarrow A_2 = 20$$

$$\text{So } i_L(t) = e^{-4t} (10 \cos 2t + 20 \sin 2t) A, \quad t > 0$$

Problem 61

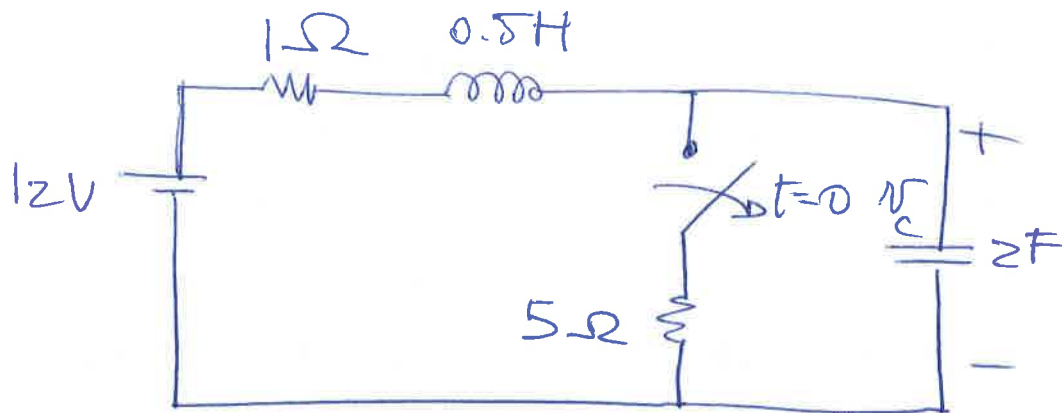

The switch in the circuit above has been closed for a long time. It opens at  $t=0$ . Find  $v_c(t)$  for  $t > 0$ .

$$\alpha = \frac{R}{2L} = \frac{1}{1} = 1, \quad \omega_0^2 = \frac{1}{LC} = 1 \quad \alpha = \omega_0$$

Critically damped

$$v_c(0^-) - v_c(0^+) = \frac{5}{6} \cdot 12 = 10V, \quad i_L(0^-) = i_L(0^+) = 2A$$

Force response (12V battery)

$$v_c(t) = v_{cf} + e^{-\alpha t} (A_1 t + A_2) = 12 + e^{-t} (A_1 t + A_2)$$

$$t \rightarrow \infty \quad v_{cf} = 12$$



$$v_c(0^+) = 10V \rightarrow A_2 = -2$$

$$v_c'(0^+) = \frac{1}{C} i_c(0^+) = \frac{1}{2} i_L(0^+) = 1$$

$$v_c'(t) = -e^{-t} (A_1 t + A_2) + e^{-t} A_1 \Big|_{t=0} = A_1 \neq A_2 = A_1 + 2 = 1 \rightarrow A_1 = -1$$

$$v_c(t) = 12 - e^{-t}(t+2), t > 0$$

# Problem 62

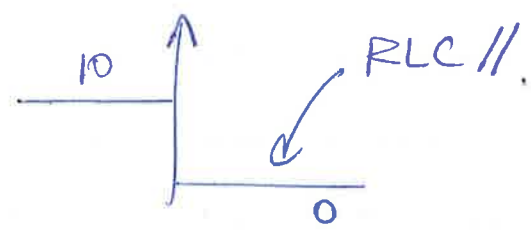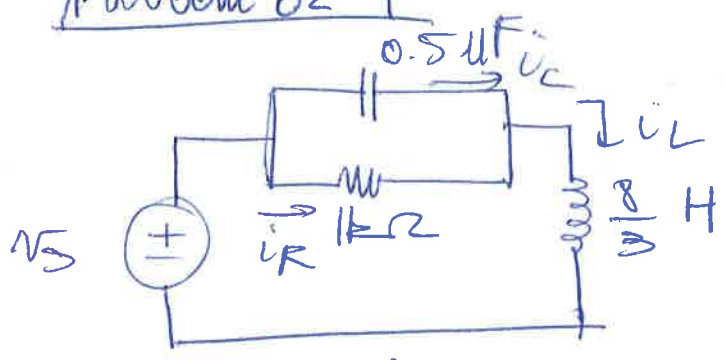

$i_R(t) \quad t > 0 \quad \text{if } v_s(t) = 10u(t)$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2000 \times 0.5} = 10^3$$

$$\omega_0^2 = \frac{1}{LC} = 0.75 \times 10^6 \rightarrow \omega_{02} = -500, -1500$$

$\alpha > \omega_0$

overdamped

$$v_C = A_1 e^{-500t} + A_2 e^{-1500t}$$

$$v_C(0^-) = 10V, \quad i_L(0^-) = 10mA$$

$$v_C(0^+) = A_1 + A_2 = 10 \quad (1) \quad i_R(0^-) \text{ because } v_C(0^+) = v_C(0^-)$$

$$v_C' = -\frac{1}{C} i_C = 2 \times 10^6 [i_L(0^+) - i_R(0^+)] = 2 \times 10^6 [10mA - 10mA] = 0$$

$$v_C' = -500A_1 e^{-500t} - 1500A_2 e^{-1500t}$$

$$v_C'(0^+) = -500A_1 - 1500A_2 = 0$$


$$-A_1 - 3A_2 = 0 \quad (2)$$

(1) & (2)  $\Rightarrow A_1 = 15, A_2 = -5$


$$v_C(t) = (15e^{-500t} - 5e^{-1500t}) V \rightarrow i_R = (15e^{-500t} - 5e^{-1500t}) mA$$

# Problem 62b

(4)

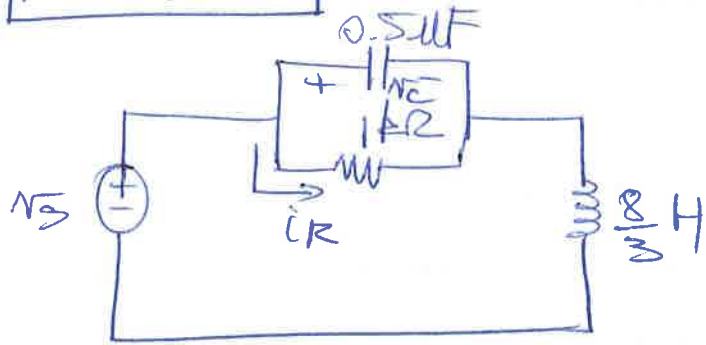

$$v_s(t) = 10u(t)$$

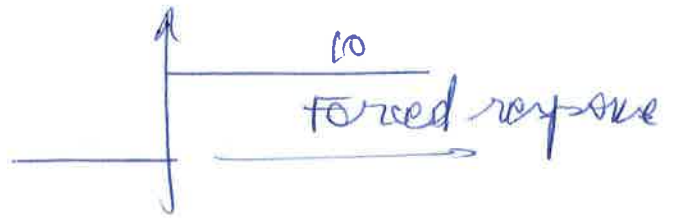

$$V_{C, f} = 10V$$

$$\rightarrow v_C = V_{C, f} + A_1 e^{-500t} + A_2 e^{-1500t}$$

$$v_C(0^+) = v_C(0^-) = 0 \quad i_L(0) = 0$$

$$A_1 + A_2 = -10V \quad (1)$$

$$v_C'(0^+) = \frac{1}{C} i_C(0^+) = 2 \times 10^6 (i_L(0^+) - i_R(0^+)) = 0$$

$\begin{matrix} \parallel \\ i_L(0) = 0 \end{matrix}$ 

 $\downarrow$   
 because  $v_C(0^+) = v_C(0^-)$

$$v_C' \Big|_{0^+} - 500A_1 - 1500A_2 = 0 \quad (2)$$

$$\rightarrow \begin{cases} A_1 + 3A_2 = 0 & (2) \\ A_1 + A_2 = -10 & (1) \end{cases}$$

$$\rightarrow A_1 = -15 \quad A_2 = 5$$

$$\rightarrow v_C(t) = 10 - 15e^{-500t} + 5e^{-1500t} \quad t > 0$$

$$\therefore i_R(t) = 10 - 15e^{-500t} + 5e^{-1500t} \text{ mA}; t > 0$$