

## DC Equations

$$I_C = I_B \beta$$

$$V_T = 25 \text{ mV at } 300 \text{ K}$$

$$I_B = I_E / (\beta + 1)$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_B = I_C / \beta$$

$$I_C = \alpha I_E$$

## AC equations

$$v_{be} = v_{\pi} = r_{\pi} i_b = r_{\pi} i_b$$

$$i_c = g_m v_{be}$$


$$r_{\pi} = \frac{V_T}{I_B}$$

$$r_e = \frac{V_T}{I_E}$$

$$g_m = \frac{I_C}{V_T}$$

## Small signal equivalent circuit

H-model

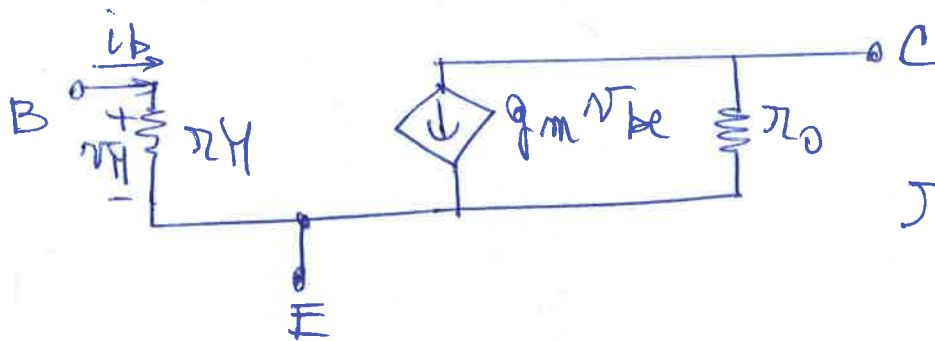

$$r_o = \frac{V_A}{I_C}$$

T-model

