

Test 1 - Fall 2011 (100pts max)

Name:

Solution

ELECTRONICS I

October 11, 2011

I. (25 pts) A current amplifier has an input resistance  $R_i = 1 \text{ k}\Omega$ , an output resistance  $R_o = 10 \text{ k}\Omega$ , and a short-circuit current gain  $A_{is} = 100 \text{ A/A}$ . It is connected between a voltage source  $v_s$  of 100 mV with a source resistance of  $100 \text{ k}\Omega$  and a load resistance of  $1 \text{ k}\Omega$ .

Calculate the value of  $v_o$ ,  $v_o/v_s$ ,  $v_o/v_i$ , where  $v_i$  is the input voltage to the amplifier.



$$v_i = \frac{1}{101} 100 \text{ mV}$$

$$v_o = A_{is} i_i \frac{10 \text{ k}\Omega \cdot 1 \text{ k}\Omega}{11 \text{ k}\Omega}$$

$$i_i = \frac{v_i}{1 \text{ k}\Omega}$$

$$\rightarrow v_o = 100 \frac{v_i}{1 \text{ k}\Omega} \frac{10 \text{ k}\Omega \cdot 1 \text{ k}\Omega}{11 \text{ k}\Omega} = 90.9 v_i$$

$$\frac{v_o}{v_i} = 90.9 \text{ V/V}$$

$$v_o = 90.9 v_i = 90 \text{ mV}$$


$$v_i = \frac{1}{101} 100 \text{ mV} = 0.99 \text{ mV} = 99 \cdot 10^{-5} \text{ V}$$

$$\frac{v_o}{v_s} = \frac{1}{101}$$

$$\rightarrow \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = \frac{90.9}{101} = 0.9$$

II. (25 pts) Calculate the transfer function  $T(s) = v_0/v_i$  for the filter shown below.

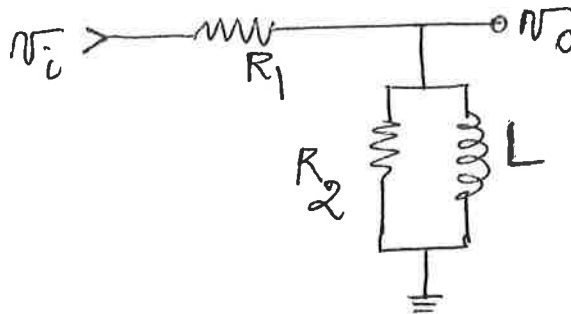(a) Is it a low-pass or high-pass filter? Discuss qualitatively.



The  $T(s)$  of the filter should be of one of the two forms

$$T(s) = \frac{K}{1 + \frac{s}{\omega_0}} \quad (1)$$

for a low-pass filter, or

$$T(s) = \frac{K}{1 + \frac{\omega_0}{s}}, \quad (2)$$

for a high-pass filter.

(b) Find the analytical expressions for  $K$  and the 3B break angular frequency  $\omega_0$ .

High-Pass  $z_L \rightarrow 0$  at  $\omega = 0 \Rightarrow v_0 = 0$   
 $z_L \rightarrow \infty$  at  $\omega = \infty \Rightarrow v_0$  finite

$$\omega \rightarrow \infty \quad v_i \rightarrow \text{---} R_1 \text{---} v_0 \rightarrow T(\omega = \infty) = K = \frac{R_2}{R_1 + R_2}$$


hooked  $L$ , ground  $v_i$ , see  $(R_1 // R_2) \Rightarrow \omega_0 = \frac{1}{\tau}$

$$\tau = \frac{L}{(R_1 // R_2)}$$

$$T(s) = \frac{\frac{R_2}{R_1 + R_2}}{1 + \frac{(R_1 // R_2)}{L} s}$$

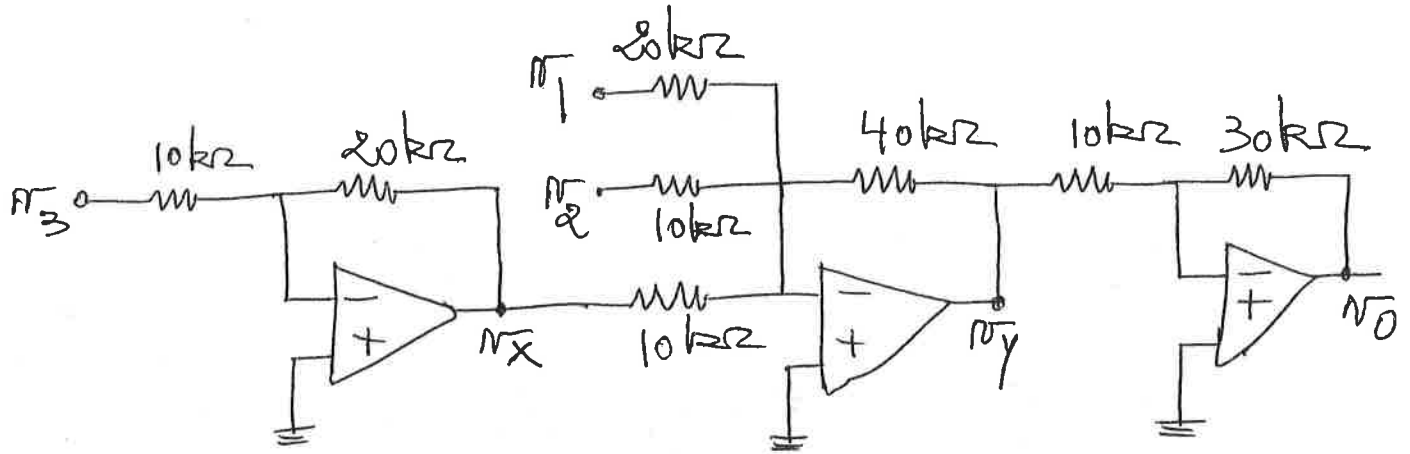III. (25 pts) In the circuit shown below,

Calculate the voltage  $v_0$  in terms  $v_1$ ,  $v_2$  and  $v_3$ . Assume all op-amps are ideal. Work your way from left to right and calculate the intermediate voltages  $v_x$  and  $v_y$ .



$$v_x = -2v_3$$

$$v_y = -2v_1 - 4v_2 - 4v_x$$

$$= -2v_1 - 4v_2 + 8v_3$$

$$v_0 = -3v_y = 6v_1 + 12v_2 - 24v_3$$

IV. (25 pts) Calculate the transfer function  $T(s) = v_0/v_i$  for the filter shown below. Assume the op-amp is ideal.


(a) Is it a low-pass or high-pass filter? Discuss qualitatively.  $\rightarrow$

$\omega \rightarrow 0 \rightarrow v_0$   
finite

(b) Find the analytical expression for K and the 3dB angular frequency  $\omega_0$

$\omega \rightarrow \infty \quad v_i \rightarrow 0$   
 $v_0 \rightarrow 0$

low-pass

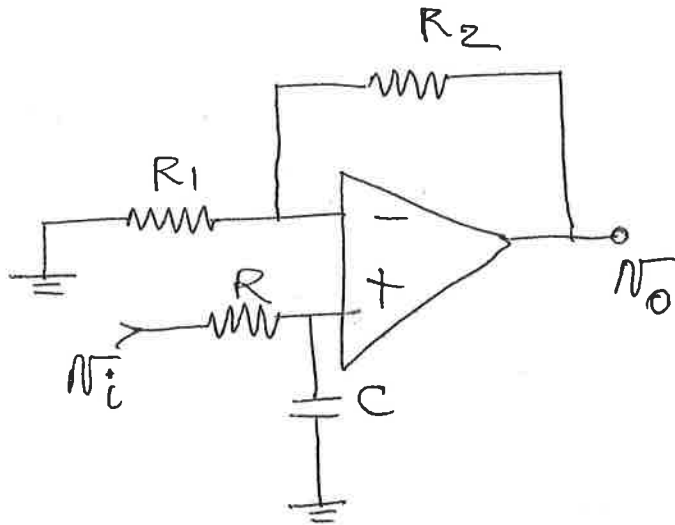

$$\frac{v_+}{v_i} = \frac{1}{1 + \frac{s}{\omega_0}}$$

$$\omega_0 = \frac{1}{RC}$$

$$v_- = v_+ \rightarrow v_0 = \left(1 + \frac{R_2}{R_1}\right) v_+$$

$$T(s) = \frac{v_0}{v_i} = \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + \frac{s}{\omega_0}} \quad \omega_0 = \frac{1}{RC}$$