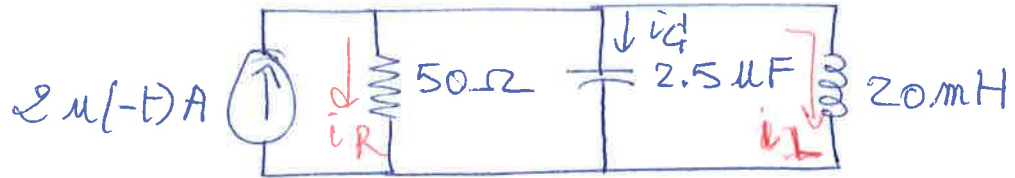


7. (25 pts) Find $i_C(t)$ for $t > 0$ in the circuit shown below.



$$\alpha = \frac{1}{2RC} = \frac{\omega^6}{100 \times 2.5} = 4000$$

$$\omega_0^2 = \frac{1}{LC} = \frac{\omega^{6+3}}{50} = 2\omega^4$$

$$\omega_d = 2000$$

$$i_C = e^{-4000t} (B_1 \cos 2000t + B_2 \sin 2000t)$$

$$i_C(0) = 2A, \quad v_C(0) = 0 \rightarrow i_C(0^+) = -2A = B_1$$

$$i_C(0^-) = 0$$

$$i_C'(0^+) = -i_L'(0^+) - i_R'(0^+)$$


$$i_C'(0^+) = -\frac{1}{L} v_C(0) - \frac{1}{R} v_C'(0^+) = 0 - \frac{1}{RC} i_C(0^+) = \frac{2 \times 10^6}{125}$$

$$\rightarrow B_1 = -2A; \quad \frac{2 \times 10^6}{125} = 16,000 = 2000 B_2 - 2(-4000)$$

$$\rightarrow B_2 = 4$$

So
$$i_C(t) = e^{-4000t} (-2 \cos 2000t + 4 \sin 2000t), \quad t > 0$$

cond solutions for #7

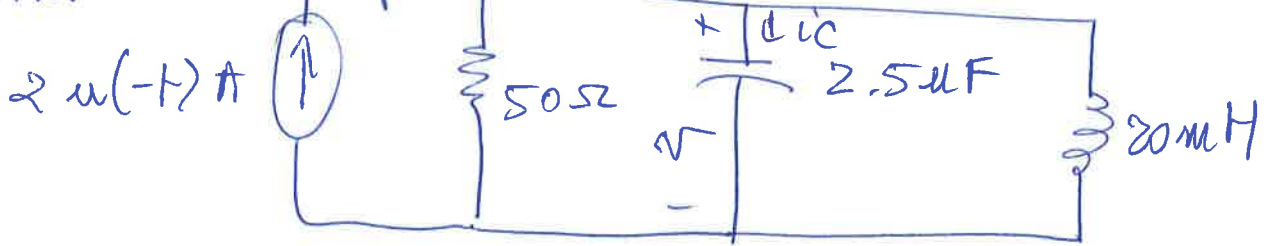

$$t > 0 \quad \alpha = 4000 \quad \omega_0 = 2 \times 10^4$$

$$\omega_d = 2000$$

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$t < 0 \quad v_C(0^-) = v_C(0^+) = 0 \rightarrow B_1 = 0$$

$$v(t) = e^{-\alpha t} B_2 \sin \omega_d t$$

$$v'(t) = -\alpha e^{-\alpha t} B_2 \sin \omega_d t + B_2 \omega_d e^{-\alpha t} \cos \omega_d t$$

$$v'(0) = B_2 \omega_d$$

$$i_C = C v'(0) = C B_2 \omega_d$$

$$i_C(0^+) = -2 \text{ A} \rightarrow B_2 = \frac{-2}{C \omega_d}$$

$$\left. \begin{aligned} i_L(0^+) &= 2 \text{ A} \\ v_C(0^+) &= 0 \end{aligned} \right\}$$

$$v(t) = \frac{-2}{C \omega_d} e^{-\alpha t} \sin \omega_d t$$


$$v'(t) = \frac{2\alpha e^{-\alpha t}}{C \omega_d} \sin \omega_d t - \frac{2}{C \omega_d} e^{-\alpha t} \omega_d \cos \omega_d t$$

$$= \frac{2 \cdot 4000}{C \cdot 2000} \sin \omega_d t e^{-\alpha t} - 2 \cos \omega_d t e^{-\alpha t}$$

$$v'(t) = (4 \sin 2000t - 2 \cos 2000t) \frac{e^{-\alpha t}}{C}$$

0 A. af-00

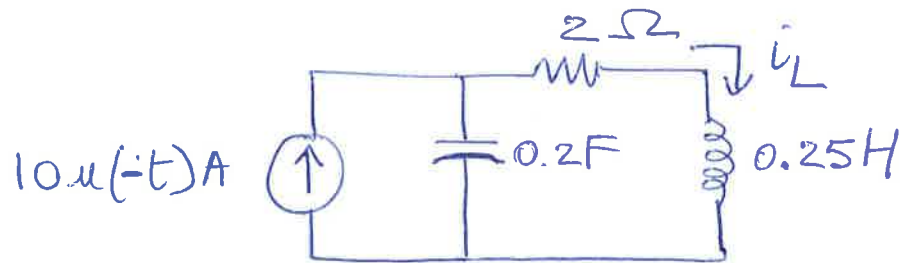8. (25 pts) Find $i_L(t)$ for $t > 0$ in the circuit shown below.



$$\alpha = \frac{R}{2L} = \frac{2}{1/2} = 4 \rightarrow \alpha^2 = 16$$

$$\omega_0^2 = \frac{1}{LC} = 20, \quad \omega_d = \sqrt{20 - 16} = 2$$

$$i_L = e^{-4t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$i_L(0) = 10A, \quad v_L(0) = 20V$$

$$A_1 = 10A; \quad i_L'(0^+) = \frac{1}{L} v_L(0^+) = 4(20 - 20) = 0$$


$$i_L'(0^+) = 2A_2 - 4 \times 10 = 0 \rightarrow A_2 = 20$$

So

$$i_L(t) = e^{-4t} (10 \cos 2t + 20 \sin 2t) A; \quad t > 0$$
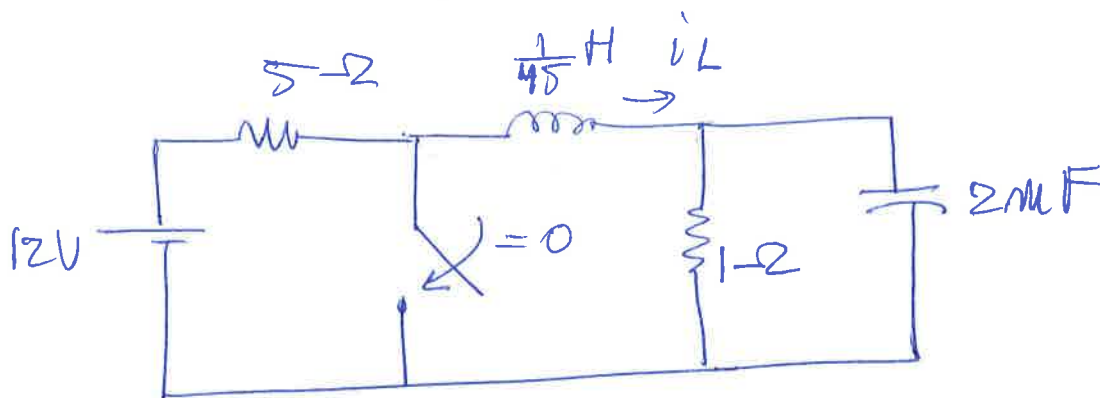
#17

Find $i_L(t)$ for $t \geq 0$ in circuit below



$$i_L(0) = \frac{12}{5+1} = 2A, \quad v_C(0) = 2V$$

$$\alpha = 250, \quad \omega_0^2 = 22500$$

$$s_{1,2} = -50, -450 \text{ rad/s}$$

$$i_L = A_1 e^{-50t} + A_2 e^{-450t}$$


$$A_1 + A_2 = 2 \quad i_L'(0^+) = 45(-2) = -50A_1 - 450A_2$$

$$A_1 + 9A_2 = 1.8$$

$$\rightarrow A_1 = 2.025$$

$$A_2 = -0.025$$
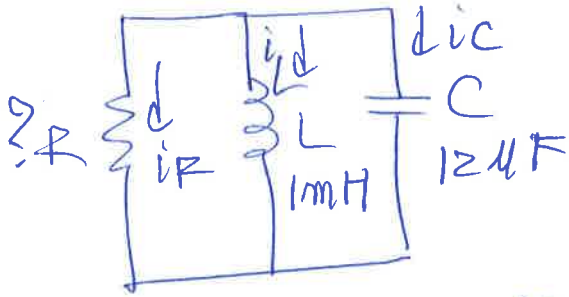
$$i_L(t) = 2.025 e^{-50t} - 0.025 e^{-450t} A, \quad t \geq 0$$



R so that circuit is critically damped.

If $v_C(0^-) = 12V$ $i_L(0^-) = 0 \rightarrow v_C(t) \forall t \geq 0$

Critically $\alpha = \omega_0 = \frac{1}{2RC} = \frac{1}{\sqrt{LC}} \rightarrow R_C = 4.564 \Omega$

$$\alpha = 9.129 \times 10^3 \text{ s}^{-1}$$

$$v(t) = e^{-\alpha t} (A_1 t + A_2)$$

$t=0$ $v = A_1 \cdot 0 + \boxed{A_2 = 12}$

$$\frac{dv}{dt} = e^{-\alpha t} [A_1] - \alpha e^{-\alpha t} (A_1 t + A_2)$$

$$e^{-\alpha t} [-\alpha A_1 t + A_1 - \alpha A_2]$$


$$i_C = -(i_R + i_L)$$

$$\alpha_1 - \alpha_2 = \left. \frac{dv}{dt} \right|_{t=0} = -\frac{1}{C} \left(\frac{v_C(0)}{R} + 0 \right) = \frac{1}{12 \times 10^{-6}} \left(\frac{12}{4.565} + 0 \right)$$

$$\rightarrow \boxed{A_1 = -109.6 \times 10^3 V}$$

$$\rightarrow \boxed{v(t) = e^{-\alpha t} (12 - 109.6 \times 10^3 t)}$$

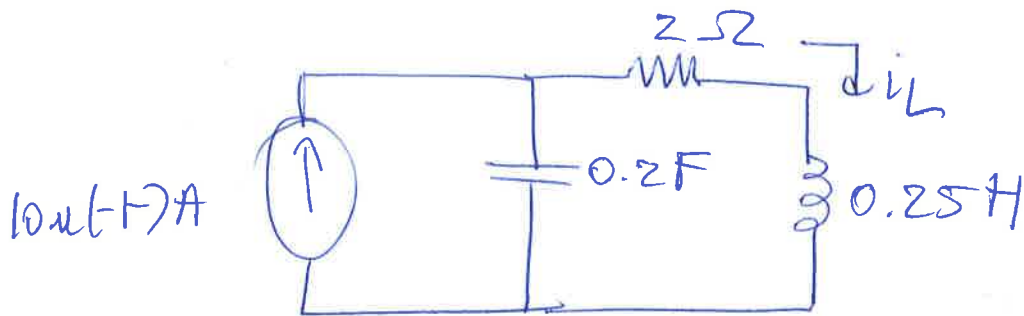Find $i_L(t)$ for $t > 0$ in the circuit below



$$\alpha = \frac{R}{2L} = 4 \quad \omega_0^2 = 20 \quad \omega_d = \sqrt{20 - 16} = 2$$

$$i_L = e^{-4t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$i_L(0) = 10, \quad v_C(0) = 20$$

$$A_1 = 10 \quad i_L'(0^+) = \frac{1}{L} v_L(0^+) = 4(20 - 20) = 0$$

$$i_L'(0^+) = 2A_2 - 4 \times 10 = 0 \rightarrow A_2 = 20$$

$$i_L(t) = e^{-4t} (10 \cos 2t + 20 \sin 2t)$$

Find $i_R(t)$ in the circuit below if

① $v_S(t) = 10 u(t)$

$$\alpha = \frac{1}{2RC} = 1000$$

$$\omega_0^2 = 0.75 \times 10^6$$

$$\alpha > \omega_0$$

$$\lambda_{1,2} = -500, -1500$$

$$v_C(t) = A_1 e^{-500t} + A_2 e^{-1500t}$$

$$\boxed{v_C(0) = 10V, \quad i_L(0) = 10mA}$$

"
 $A_1 + A_2$

$$v_C'(0^+) = 2 \times 10^6 [i_L(0) - i_R(0^+)]$$

$$= 2 \times 10^6 \left[0.01 - \frac{10}{1000} \right] = 0$$


$$-500A_1 - 1500A_2 = 0$$

$$\boxed{A_1 + 3A_2 = 0}$$

$$\boxed{A_1 + A_2 = 10}$$

$$\rightarrow v_C(t) = 15 e^{-500t} - 5 e^{-1500t}$$
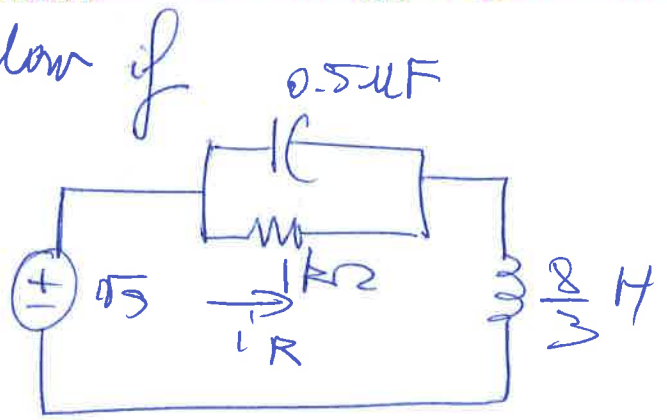
$$i_R(t) = \left(15 e^{-500t} - 5 e^{-1500t} \right) mA$$



$$\textcircled{b} \quad v_C(t) = 10 u(t)$$

$$v_C f = 10$$

$$v_C = 10 + A_3 e^{-500t} + A_4 e^{-1500t}$$

$$v_C(0) = 0 \quad , \quad i_C(0) = 0$$

$$\rightarrow A_3 + A_4 = -10$$

$$\begin{aligned} v_C'(0^+) &= 2 \cdot 10^6 [i_C(0) - i_C(0^+)] \\ &= 2 \cdot 10^6 [0 - 0] = 0 \\ &= -500 A_3 - 1500 A_4 \end{aligned}$$

$$\rightarrow A_3 = -15 \quad A_4 = 5$$

$$v_C(t) = 10 - 15 e^{-500t} + 5 e^{-1500t}, \quad t > 0$$

$$i_C(t) = 10 - 15 e^{-500t} + 5 e^{-1500t} \text{ mA}$$