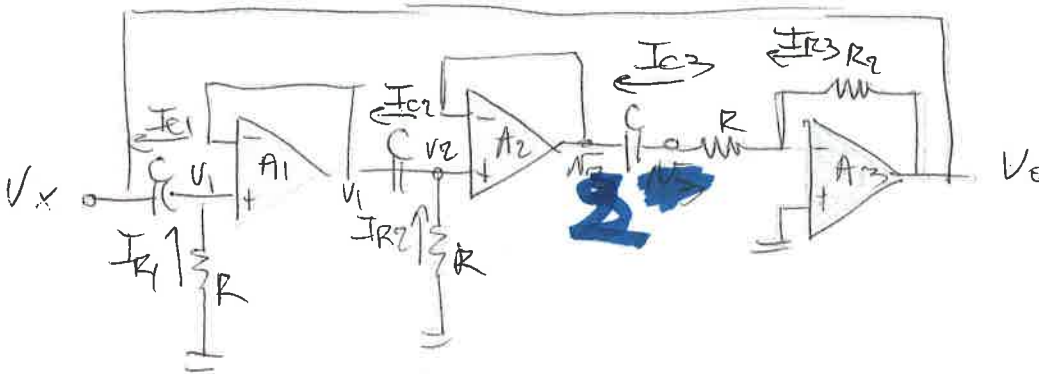


ECES 352 Electronics II
Assignment # 16
Due Monday February 26, 2007

Name: SOLUTION

1. Consider the following phase shift oscillator where the op amps can be assumed to be **ideal**. Determine an expression for the loop gain $L(s) = V_o/V_x$ in terms of the resistances R and R_2 , the capacitances C (all the same size) and the s ($=j\omega$). For the intermediate currents and voltages, use the terminology shown on the figure. Hint: Write the voltage gain V_o/V_x as a set of three ratios, one for each op amp stage. Derive an expression for each voltage ratio from the circuit in terms of the R 's and C . Determine the oscillation frequency ω_o in terms of the resistances and capacitance. Find the size of R_2 needed relative to R for oscillation.



$$\frac{V_o}{V_x} = \left(\frac{V_o}{V_2}\right) \left(\frac{V_2}{V_1}\right) \left(\frac{V_1}{V_x}\right)$$

So combining the three results we get

$$\frac{V_o}{V_x} = \left(\frac{-sCR_2}{1+sCR}\right) \left(\frac{sCR}{1+sCR}\right) \left(\frac{sCR}{1+sCR}\right)$$

$$= \frac{-s^3 C^3 R_2 R^2}{(1+sCR)^3}$$

$$= \frac{-s^3 C^3 R_2 R^2}{(1+3sCR + 3s^2 C^2 R^2 + s^3 C^3 R^3)}$$

For A_3 ideal op amps so $I_- = I_+ = 0$
 so $I_{R_2} = I_{C_3} = \frac{V_o}{R_2}$ for A_3
 $V_- = V_+ = 0$

$$V_2 = 0 - (R + \frac{1}{sC}) I_{R_2} = -\frac{V_o}{R_2} \left(R + \frac{1}{sC}\right)$$

$$\frac{V_o}{V_2} = \frac{-sCR_2 + 1}{sCR_2} \text{ so } \frac{V_2}{V_o} = \frac{-sCR_2}{1+sCR}$$

For A_2 $I_{R_2} = -\frac{V_2}{R} = I_{C_2} = \frac{V_2 - V_1}{sC} = sC(V_2 - V_1)$
 so $V_2 \left(-\frac{1}{R} - sC\right) = -sC V_1$

$$\frac{V_2}{V_1} = \frac{sCR}{1+sCR}$$

For A_1 $I_{R_1} = -\frac{V_1}{R} = I_{C_1} = \frac{V_1 - V_x}{sC} = sC(V_1 - V_x)$

$$V_1 \left(-\frac{1}{R} - sC\right) = -sC V_x$$

$$\frac{V_1}{V_x} = \frac{sCR}{1+sCR}$$

Assignment # 12 (continued)

Putting in $s = j\omega$ and simplifying we get

$$\frac{V_o}{V_R} = \frac{-j\omega^3 C^3 R_2 R^2}{1 + 3j\omega CR - 3\omega^2 C^2 R^2 - j\omega^3 C^3 R^3} = \frac{j\omega^3 C^3 R_2 R^2}{(1 - 3\omega^2 C^2 R^2) + j(3\omega CR - \omega^3 C^3 R^3)}$$

To get this to go to one we need this term to go to zero, so

$$1 - 3\omega^2 C^2 R^2 = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{3}RC}$$

Then at $\omega = \omega_0$ we have

$$\left. \frac{V_o}{V_R} \right|_{\omega = \omega_0} = \frac{\omega_0^3 C^3 R_2 R^2}{3\omega_0 CR - \omega_0^3 C^3 R^3} = \frac{\omega_0^2 C^2 R_2 R}{3 - \omega_0^2 C^2 R^2} = 1$$

$$\omega_0^2 C^2 R_2 R = 3 - \omega_0^2 C^2 R^2$$

$$R_2 R \frac{1}{3R^2} = 3 - \frac{1}{3R^2} \frac{1}{R^2}$$

$$\frac{R_2}{3R} = 3 - \frac{1}{3} = \frac{8}{3}$$

so $\frac{R_2}{R} = 8$

$$\frac{\omega^3 C^3 R_2 R^2}{(3\omega CR - \omega^3 C^3 R^3) + j(3\omega CR - \omega^3 C^3 R^3)}$$

$$\begin{pmatrix} 1 & 0 \\ 0 & 0 \end{pmatrix}$$

$$= \begin{pmatrix} 1 & 0 \\ 0 & 0 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$$

Test 3 - Spring 2003 (100pts max) - M. Cahay

Name: SOLUTION

ELECTRONICS II

May 27, 2003

I. (20 pts): A second order filter has its poles at

$$s = -\frac{1}{4} \pm j\frac{\sqrt{8}}{4}$$

The transfer function is zero at $\omega = 3$ rad/s and is equal to 4 at DC.

Find the analytical expression for the transfer function $T(s)$.

$$T(s) = k \frac{(s + j3)(s - j3)}{\left(s + \frac{1}{4} + j\frac{\sqrt{8}}{4}\right)\left(s + \frac{1}{4} - j\frac{\sqrt{8}}{4}\right)}$$

$$T(s) = k \frac{(s^2 + 9)}{\left(s + \frac{1}{4}\right)^2 + \left(\frac{\sqrt{8}}{4}\right)^2} = k \frac{s^2 + 9}{s^2 + \frac{s}{2} + \frac{1}{16} + \frac{8}{16}}$$

$$T(s) = k \frac{s^2 + 9}{s^2 + \frac{s}{2} + \frac{9}{16}} = \frac{16k (s^2 + 9)}{[16s^2 + 8s + 9]}$$

as $s \rightarrow 0$ (DC)

$$T(0) = 16k = 4$$

$$\Rightarrow k = 1/4$$

$$\therefore T(s) = \frac{1}{4} \frac{(s^2 + 9)}{\left[s^2 + \frac{s}{2} + \frac{9}{16}\right]}$$


IV. (30 pts): The filter below is said to be of the high-pass notch type, i.e.,

$$T(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad (4)$$

with ω_n lesser than ω_0 .

Derive the expression for $T(s)$ from the circuit diagram and give analytical expressions for ω_n , ω_0 and Q in terms of R , L_1 , L_2 , and C .

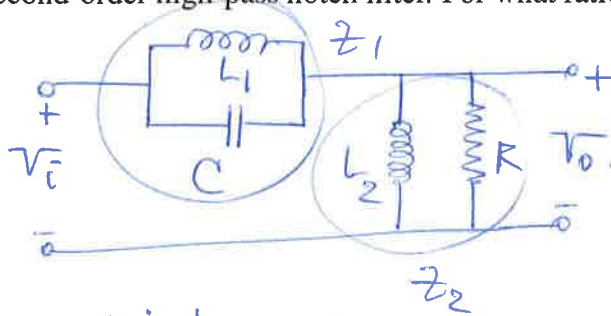The notch in the transfer function occurs at the angular frequency ω_n (see attached table for the second-order high-pass notch filter. For what ratio of L_1/L_2 does $\omega_n = 0.9 \omega_0$?



$$T(s) = \frac{z_2}{z_1 + z_2} = \frac{\frac{Rj\omega L_2}{R + j\omega L_2}}{\left[\frac{j\omega L_1 + \frac{1}{j\omega C}}{j\omega L_1 + \frac{1}{j\omega C}} \right] + \left(\frac{Rj\omega L_2}{R + j\omega L_2} \right)} = \frac{\frac{\Delta R L_2}{R + \Delta R L_2}}{\left(\frac{L_1}{C} \right) (R + \Delta R L_2) + R \Delta L_2 \left(\Delta L_1 + \frac{1}{\Delta C} \right)} = \frac{\Delta R L_2}{\left(\Delta L_1 + \frac{1}{\Delta C} \right) (R + \Delta R L_2)}$$

$$T(s) = \frac{\Delta R L_2 (\Delta L_1 + \frac{1}{\Delta C})}{\frac{L_1}{C} R + \Delta \frac{R L_1 L_2}{C} + \Delta^2 L_1 L_2 R + \frac{R L_2}{C}}$$

$$T(s) = \frac{\Delta^2 L_1 L_2 R + \frac{R L_2}{C}}{\Delta^2 L_1 L_2 R + \frac{\Delta R L_1 L_2}{C} + \frac{R(L_1 + L_2)}{C}}$$

$$\Rightarrow T(s) = \frac{\Delta^2 + \frac{1}{L_1 C}}{\Delta^2 + \frac{\Delta}{C} + \left(\frac{L_1 + L_2}{L_1 L_2} \right) \frac{1}{C}} = \frac{\Delta^2 + \frac{1}{L_1 C}}{\Delta^2 + \frac{\Delta}{C} + \frac{1}{(L_1 // L_2) C}}$$

so notch is at $\omega_n^2 = \frac{1}{L_1 C} \Rightarrow \omega_n = \frac{1}{\sqrt{L_1 C}} \quad (Q_2 = 1)$


$$a_0 = \frac{1}{\sqrt{(L_1 // L_2) C}} \Rightarrow a_0^2 = \left(\frac{L_1 + L_2}{L_2} \right) \omega_n^2 \quad \text{for } \omega_n^2 = (0.9 \omega_0)^2$$

$$a_m = \frac{1}{\sqrt{L_1 C}} \Rightarrow \boxed{\frac{L_1}{L_2} = 0.2346}$$

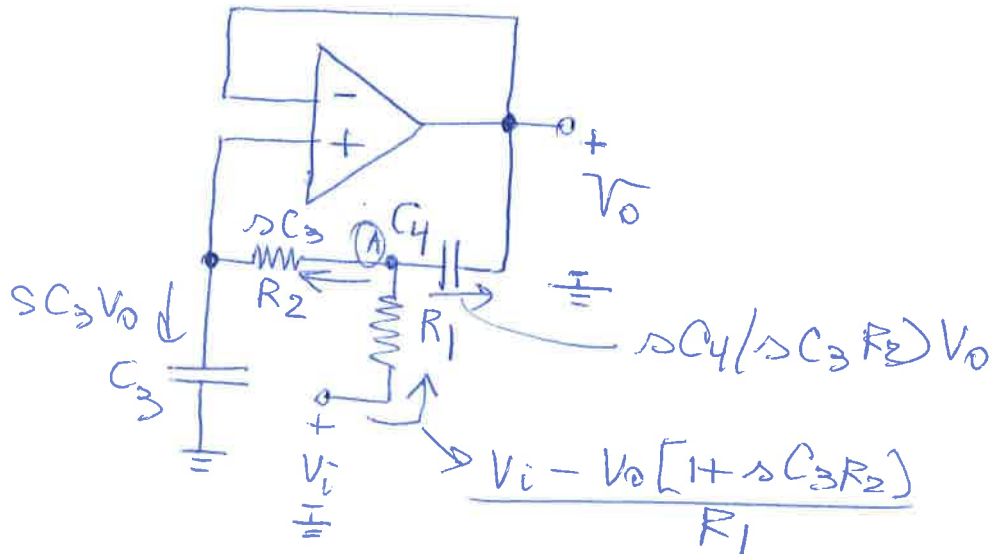III. (30 pts): Consider the circuit below in which the op-amp is assumed to be ideal (i.e., infinite input resistance looking into the positive and negative terminals). Show that the transfer function for that filter $T(s) = V_o/V_i$ is of second order and can be expressed as follows

$$T(s) = \frac{a_0}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2} \quad (3)$$

Give analytical expressions for ω_0 and Q in terms of R_1 , R_2 , and C_3 , C_4 .



Potential at node A $V_o(1 + sC_3R_2)$

Node equation at A

$$\frac{V_i - V_o(1 + sC_3R_2)}{R_1} = sC_3V_o + s^2C_3C_4R_2V_o$$

$$\rightarrow \frac{V_i}{R_1} = V_o \left[s^2C_3C_4R_2 + sC_3 + \frac{sC_3R_2}{R_1} + \frac{1}{R_1} \right]$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{1/C_3C_4R_1R_2}{s^2 + s \frac{1}{R_2C_4} \left(1 + \frac{R_2}{R_1} \right) + \frac{1}{C_3C_4R_1R_2}}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{C_3C_4R_1R_2}}$$

$$Q = \frac{1}{\sqrt{C_3C_4R_1R_2}} C_4 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$