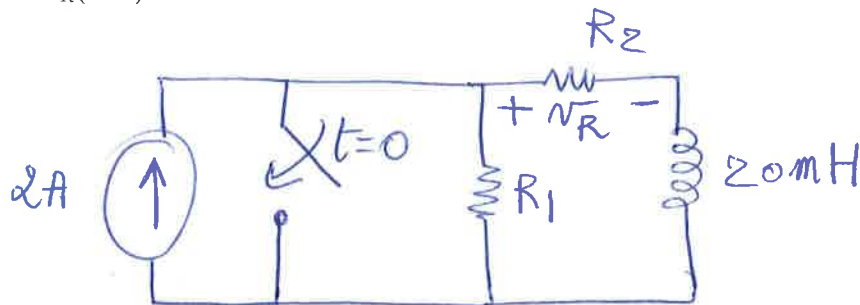


Final - Fall 2010 (200 pts max) - M. Cahay
 Name:

NETWORK ANALYSIS I
 Friday, December 10, 2010

1. (20 pts) Select the values of R_1 and R_2 in the circuit below so that $v_R(0)^+ = 10$ V and $v_R(1\text{ms}) = 5$ V.



$$t < 0 \quad v_R = \frac{2 R_1 R_2}{R_1 + R_2}$$

$$i_L(0) = \frac{2 R_1}{R_1 + R_2}$$

$$t > 0 \quad i_L(t) = \frac{2 R_1}{R_1 + R_2} e^{-50 R_2 t}$$

$$\rightarrow v_R(t) = \frac{2 R_1 R_2}{R_1 + R_2} e^{-50 R_2 t}$$


$$v_R(0^+) = 10 = \frac{2 R_1 R_2}{R_1 + R_2} \rightarrow R_1 // R_2 = 50 \Omega$$

$$v_R(1\text{ms}) = 5 = 10 e^{-\frac{50 R_2}{1000}} \rightarrow 0.05 R_2 = 0.6931$$

$$\rightarrow \boxed{R_2 = 13.86 \Omega}$$

$$\rightarrow \boxed{R_1 = 7.821 \Omega}$$

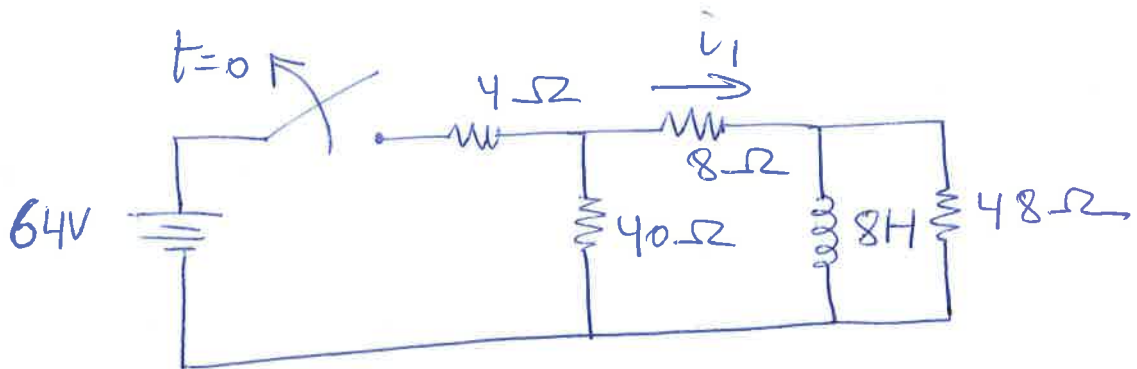2. (20 pts) Determine i_1 at $t = -0.1s$ (the circuit has been set for a long time) and $i_1(t = 0.1s)$ in the circuit below.



$$i_L(0) = \frac{64}{4 + (40/8)} \cdot \frac{40}{58} = 5A$$

$$i_L(t) = 5e^{-\frac{24t}{8}} = 5e^{-\frac{3t}{1}} A$$


$$\bar{i}_1(t) = 2.5e^{-3t} A$$

$t > 0$

$$\bar{i}_1(-0.1) = 2.5A$$

$$\bar{i}_1(0.1) = 1.852A$$

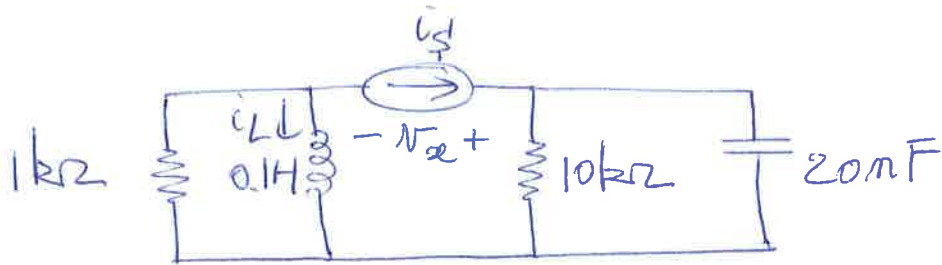3. (30 pts) The value of i_s in the circuit below is 1 mA for $t < 0$, and zero for $t > 0$. Find v_x for (a) $t < 0$ and (b) $t > 0$.



$$t < 0 \quad i_s = 1 \text{ mA}$$

$$v_c(0) = 10 \text{ V}$$

$$i_L(0) = -1 \text{ mA}$$

$$v_x(0) = 10 \text{ V}, \quad t < 0$$


$$t > 0 \quad v_c(t) = 10 e^{-\frac{t}{10^4 \times 20 \times 10^{-9}}} = 10 e^{-5000t} \text{ V}$$

$$i_L(t) = -10^{-3} e^{-\frac{t}{0.1}} = -10^{-3} e^{-10^4 t} \text{ A}$$

$$\rightarrow v_L(t) = e^{-10000t} \text{ V}, \quad t > 0$$

$$v_x = v_c - v_L(t) = 10 e^{-5000t} - e^{-10^4 t}, \quad t > 0$$

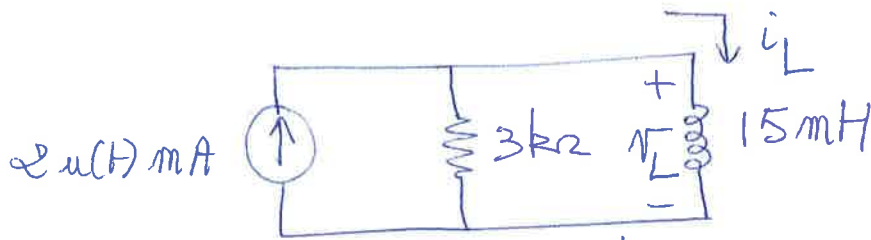4. (30 pts) In the circuit below, find $i_L(t)$ for $t > 0$. Use that expression to find $v_L(t)$ for $t > 0$.



$$i_L(t) = \left(i_{L0} + A e^{-\frac{Rt}{L}} \right) u(t) \text{ mA}$$


$$2\text{ mA} \rightarrow A = -2\text{ mA}$$

$$i_L(t) = \left(2 - 2 e^{-2 \times 10^5 t} \right) u(t) \text{ mA}$$

$$v_L = L \dot{i}_L = 15 \times 10^{-3} \times (-2) \left(-2 \times 10^5 e^{-2 \times 10^5 t} \right) u(t) \text{ V}$$

$$v_L(t) = 6 e^{-2 \times 10^5 t} u(t) \text{ V}$$

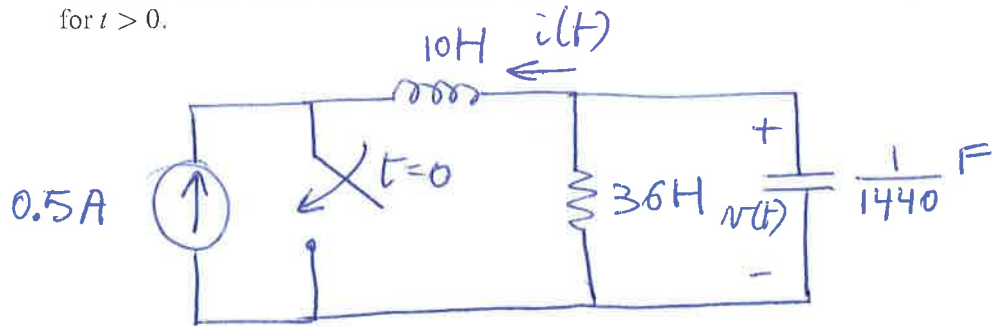5. (25 pts) The circuit below was put together a long time ago and has reached steady-state (no more time variation) before the switch is closed. Find $v(t)$ and $i(t)$ for $t > 0$.



$$\alpha = \frac{1}{2RC} = \frac{1440}{72} = 20 \quad ; \quad \omega_0^2 = \frac{1440}{10} = 144$$

$$s_{1,2} = -20 \pm \sqrt{400 - 144} = -4, -36$$

$$v = A_1 e^{-4t} + A_2 e^{-36t}$$

$$v(0) = 18 = A_1 + A_2 \quad (1) \quad ; \quad v'(0) = 1440 \left(\frac{1}{2} - \frac{18}{36} \right) = 0$$

$$-4A_1 - 36A_2 = 0 \quad (2)$$


$$(1)(2) \Rightarrow A_1 = 20.25 \quad ; \quad A_2 = -2.25$$

$$v(t) = (20.25 e^{-4t} - 2.25 e^{-36t}) \text{ V for } t > 0$$

$$i(t) = \frac{v}{36} + \frac{v'}{1440} = 0.5625 e^{-4t} - 0.0625 e^{-36t} - 0.05625 e^{-4t} + 0.05625 e^{-36t}$$

$$\Rightarrow i(t) = 0.50625 e^{-4t} - 0.00625 e^{-36t}$$

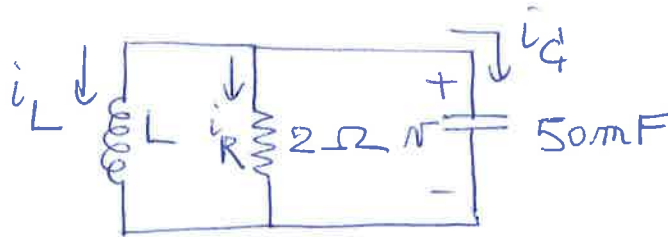6. (25 pts) Referring to the circuit below, what value of L will result in a transient response of the form $v = Ae^{-4t} + Be^{-6t}$? Find A and B if $i_R(0^+) = 10A$ and $i_C(0^+) = 15A$.



(a) we want $v = Ae^{-4t} + Be^{-6t}$

$$\alpha = \frac{1}{2RC} = 5 \text{ s}^{-1}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4 = -5 + \sqrt{25 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6 = -5 - \sqrt{25 - \omega_0^2}$$

$$\rightarrow \omega_0 = 4.899 \text{ rad/s}$$

$$\omega_0^2 = \frac{1}{LC} \rightarrow \boxed{L = \frac{1}{\omega_0^2 C} = 833.3 \text{ mH}}$$

(b) $i_R(0^+) = 10A$ $i_C(0^+) = 15A$

$$i_R(0^+) = 10A, \quad v_R(0^+) = v(0^+) = v_C(0^+) = 20V$$

$$v(0) = A + B = 20$$


$$i_C = C \frac{dv}{dt} = 50 \times 10^{-3} (-4A e^{-4t} - 6B e^{-6t})$$

$$i_C(0^+) = 50 \times 10^{-3} (-4A - 6B) = 15$$

$$\rightarrow A = 20V; \quad B = -190V$$

$$\rightarrow \boxed{v(t) = 20e^{-4t} - 190e^{-6t}; \quad t > 0}$$

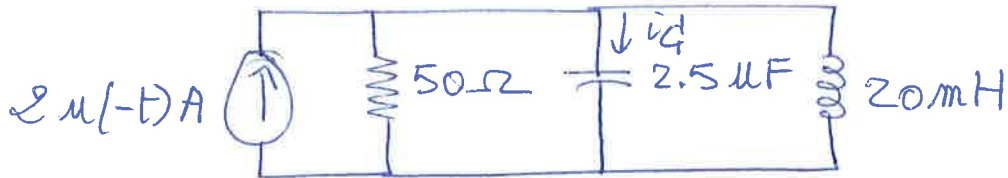7. (25 pts) Find $i_C(t)$ for $t > 0$ in the circuit shown below.



$$\alpha = \frac{1}{2RC} = \frac{10^6}{100 \times 2.5} = 4000$$

$$\omega_0^2 = \frac{1}{LC} = \frac{10^6 + 3}{50} = 2 \times 10^4$$

$$\omega_d = 2000$$

$$i_C = e^{-4000t} (B_1 \cos 2000t + B_2 \sin 2000t)$$

$$i_C(0) = 2A, \quad v_C(0) = 0 \rightarrow i_C(0^+) = -2A$$

$$i_C'(0^+) = -i_L'(0^+) - i_R'(0^+)$$

$$i_C'(0^+) = -\frac{1}{L} v_C(0) - \frac{1}{R} v_C'(0^+) = 0 - \frac{1}{RC} i_C(0^+) = \frac{2 \times 10^6}{125}$$


$$\rightarrow B_1 = -2A; \quad \frac{2 \times 10^6}{125} = 16,000 = 2000 B_2 - 2(-4000)$$

$$\rightarrow B_2 = 4$$

So

$$i_C(t) = e^{-4000t} (-2 \cos 2000t + 4 \sin 2000t), \quad t > 0$$

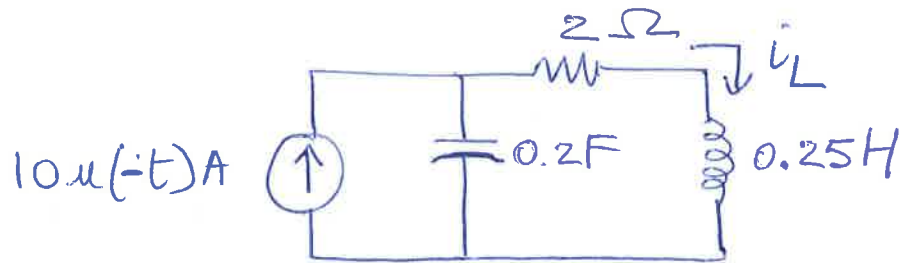8. (25 pts) Find $i_L(t)$ for $t > 0$ in the circuit shown below.



$$\alpha = \frac{R}{2L} = \frac{2}{1/2} = 4$$

$$\omega_0^2 = \frac{1}{LC} = 20, \quad \omega_d = \sqrt{20 - 16} = 2$$

$$i_L = e^{-4t} (A_1 \cos 2t + A_2 \sin 2t)$$

$$i_L(0) = 10A, \quad v_L(0) = 20V$$

$$A_1 = 10A; \quad i_L'(0^+) = \frac{1}{L} v_L(0^+) = 4(20 - 20) = 0$$

$$i_L'(0^+) = 2A_2 - 4 \times 10 = 0 \rightarrow A_2 = 20$$

So

$$i_L(t) = e^{-4t} (10 \cos 2t + 20 \sin 2t) A; \quad t > 0$$