

Fall 2011
EECE 351

Due Friday Oct. 28, 2011

Team Effort

Names:

Consider the following half-wave rectifier.
Assume both the op-amp and diode are ideal.

Explain how to calculate the transfer characteristic of this half-wave rectifier, i.e., v_o vs v_i .

