

Hwk 5

Due Monday, Oct. 24, 2011

In the circuit below, what is the value of R_2 (in terms of R_1 and R_T) for

- (a) Maximum power transfer to R_2 .
- (b) Maximum power transfer to R_1 .
- (c) Maximum power transfer to $R_L = \frac{R_1 R_2}{R_1 + R_2}$.

