

Ex 5.1

A 0.18- μm fabrication process is specified to have $t_{ox} = 4 \text{ nm}$, $\mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}$, and $V_t = 0.5 \text{ V}$. Find the value of the process transconductance parameter k'_n . For a MOSFET with minimum length fabricated in this process, find the required value of W so that the device exhibits a channel resistance r_{DS} of $1 \text{ k}\Omega$ at $v_{GS} = 1\text{V}$.

Ans. $388 \mu\text{A}/\text{V}^2$; $0.93 \mu\text{m}$

Ex: 5.1

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{34.5 \text{ pF/m}}{4 \text{ nm}} = 8.625 \text{ fF}/(\mu\text{m})^2$$

$$\mu_n = 450 \text{ cm}^2/\text{VS}$$

$$k'_n = \mu_n C_{ox} = 388 \mu\text{A}/\text{V}^2$$

$$V_{OV} = (v_{GS} - V_t) = 0.5 \text{ V}$$

$$g_{DS} = \frac{1}{1 \text{ k}\Omega} = k'_n \frac{W}{L} V_{OV} \Rightarrow \frac{W}{L} = 5.15$$

$$L = 0.18 \mu\text{m}, \text{ so } W = 0.93 \mu\text{m}$$

A circuit designer intending to operate a MOSFET in saturation is considering the effect of changing the device dimensions and operating voltages on the drain current I_D . Specifically, by what factor does I_D change in each of the following cases?

- (a) The channel length is doubled.
- (b) The channel width is doubled.
- (c) The overdrive voltage is doubled.
- (d) The drain-to-source voltage is doubled.

Ex: 5.3 $I_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2$ in saturation

Change in I_D is:

- (a) double L, 0.5
- (b) double W, 2
- (c) double V_{OV} , $2^2 = 4$
- (d) double V_{DS} , no change (ignoring length modulation)

EX 5.4

An NMOS transistor is operating at the edge of saturation with an overdrive voltage V_{OV} and a drain current I_D . If V_{OV} is doubled, and we must maintain operation at the edge of saturation, what should V_{DS} be changed to? What value of drain current results?

Ans. $2 V_{OV}$; $4 I_D$

Ex: 5.4 In saturation $v_{DS} \geq V_{OV}$, so $2V_{OV}$

$$I_D = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2, \text{ so } 4 I_D.$$

Ex D5.9

For the circuit in Fig. E5.9, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_{tn} = 0.5$ V, $\mu_n C_{ox} = 0.4$ mA/V², $W/L = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}$, and $\lambda = 0$.

Ans. 13.9 k Ω


 


Figure E5.9

Ex: 5.9

 

$$\frac{W}{L} = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}} = 4.0$$

$$\lambda = 0$$

saturation mode ($v_{GD} = 0 < V_{tn}$)

$$V_D = 0.8 \text{ V} = 1.8 - I_D R_D$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_D - V_{tn})^2 = 72 \mu\text{A}$$

$$\therefore R = \frac{1.8 - 0.8}{72 \mu\text{A}} = 13.9 \text{ k}\Omega$$


$$V_{tn} = 0.5 \text{ V}.$$

$$\mu_n C_{ox} = 0.4 \text{ mA/V}^2$$

Ex. 5.18


Consider the amplifier circuit of Fig. 5.39(a) without the load resistance R_L and with channel length modulation neglected. Let $V_{DD} = 5\text{ V}$, $V_t = 0.7\text{ V}$, and $k_n = 1\text{ mA/V}^2$. Find V_{OV} , I_D , R_D , and R_G to obtain a voltage gain of 25 V/V and an input resistance of $0.5\text{ M}\Omega$. What is the maximum allowable input signal, \hat{v}_i ?

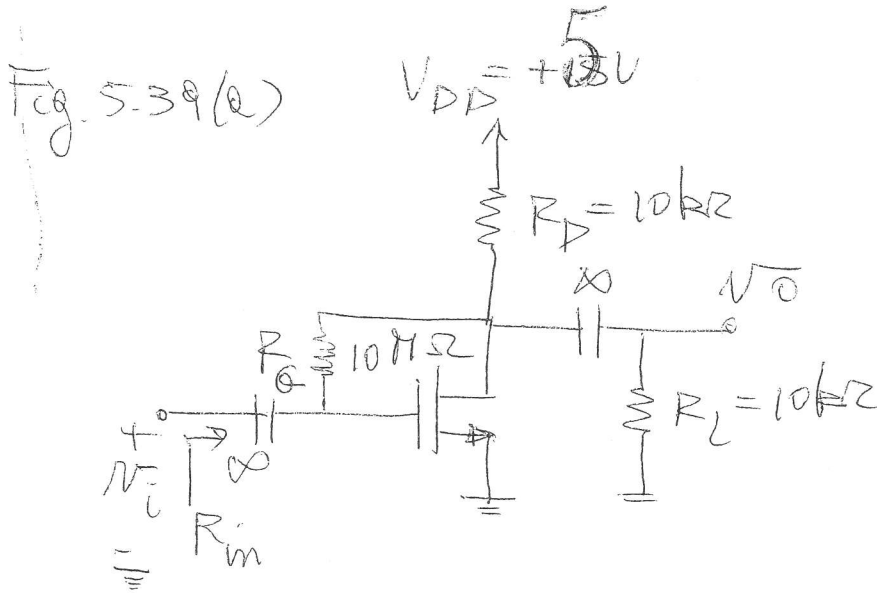Ans. 0.319 V ; $50.7\text{ }\mu\text{A}$; $78.5\text{ k}\Omega$; $13\text{ M}\Omega$; 27 mV



$$V_t = 0.7\text{ V.}$$

$$k_n = 1\text{ mA/V}^2$$

 

$$\text{Design for } A_v = \frac{v_o}{v_i} = -25, R_{in} = 500\text{ k}\Omega$$

$$\therefore g_m R_D = 25 = k_n V_{OV} R_D$$

$$R_{in} = \frac{v_i}{i_i} = \frac{v_i}{v_i - v_o} R_G$$

$$\Rightarrow R_G = 26 R_{in} = 13\text{ M}\Omega$$

$$I_D R_D = \left(\frac{1}{2} k_n V_{OV}^2 \right) R_D$$

$$= \frac{1}{2} g_m R_D V_{OV} = 12.5 V_{OV}$$

and

$$V_{OV} = V_{DD} - V_t - I_D R_D = 4.3 - 12.5 V_{OV}$$

$$\therefore V_{OV} = 0.319\text{ V.}$$

$$g_m = 319\text{ }\mu\text{A/V}$$

$$R_D = 78.5\text{ k}\Omega$$

$$V_{DS} = V_{OV} + V_t$$


$$\hat{v}_{GD} = 0 + 26 \hat{v}_i \leq V_t$$

$$\therefore |\hat{v}_i| < \frac{V_t}{26} = 27\text{ mV.}$$

EX 5.37



Consider the circuit of Fig. 5.56 for the case $V_{DD} = V_{SS} = 10\text{ V}$, $I = 0.5\text{ mA}$, $R_G = 4.7\text{ M}\Omega$, $R_D = 15\text{ k}\Omega$, $V_t = 1.5\text{ V}$, and $k'_n(W/L) = 1\text{ mA/V}^2$. Find V_{OV} , V_{GS} , V_G , V_S , and V_D . Also, calculate the values of g_m and r_o , assuming that $V_A = 75\text{ V}$. What is the maximum possible signal swing at the drain for which the MOSFET remains in saturation?

 Ans. See Fig. E5.37; without taking into account the signal swing at the gate, the drain can swing to -1.5 V , a negative signal swing of 4 V



$$V_{OV} = 1\text{ V}$$

$$V_{GS} = 2.5\text{ V}$$

 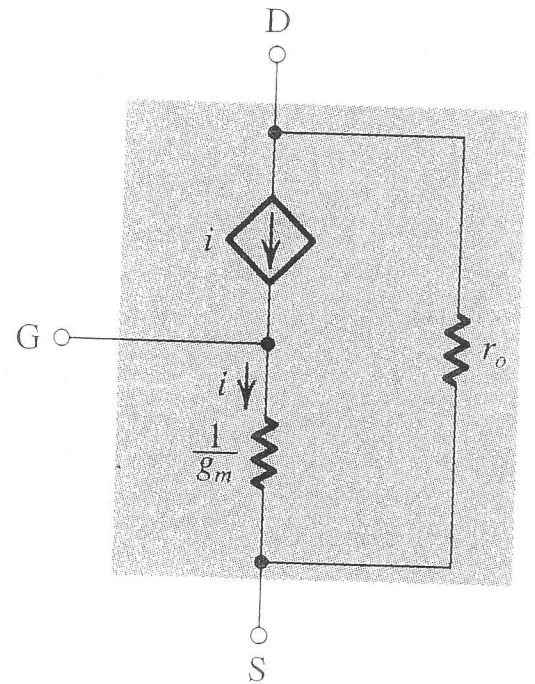

$$g_m = 1\text{ mA/V}$$

$$r_o = 150\text{ k}\Omega$$

$$1/g_m = 1\text{ k}\Omega$$


Ex: 5.37

$$V_t = 1,5 \text{ V}$$

$$k_n \frac{W}{L} = 1 \text{ mA/V}^2$$

$$V_A = 75 \text{ V.}$$
 
$$I_D = 0.5 \text{ mA} = \frac{1}{2} k_n \frac{W}{L} V_{OV}^2 \Rightarrow V_{OV} = 1.0 \text{ V.}$$



$$V_{GS} = V_t + V_{OV} = 2.5 \text{ V}$$

$$V_G = 0$$

$$V_S = -2.5 \text{ V.}$$

$$V_D = V_{DD} - I_D R_D = +2.5 \text{ V.}$$

$$g_m = k_n \frac{W}{L} V_{OV} = 1 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = 150 \text{ k}\Omega$$

$$V_{GD} - \hat{v}_{gd} = V_t$$

$$-\hat{v}_{gd} \cong \hat{v}_d = V_t - V_{GD} = 4.0 \text{ V.}$$

Ex. 5.43

For a depletion-type NMOS transistor with $V_t = -2$ V and $k_n'(W/L) = 2$ mA/V², find the minimum v_{DS} required to operate in the saturation region when $v_{GS} = +1$ V. What is the corresponding value of i_D ?

Ans. 3 V; 9 mA

Ex: 5.43

$$V_{GS} = +1 \text{ V}, V_t = -2 \text{ V}$$

$$V_{GS} - V_t = 3 \text{ V}$$

TO OPERATE IN SATURATION REGION:

$$V_{DS \text{ min}} = V_{GS} - V_t = 3 \text{ V}$$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 2 \times 3^2 = 9 \text{ mA}$$

Problem

5.9 An NMOS transistor with $k_n = 1 \text{ mA/V}^2$ and $V_t = 1 \text{ V}$ is operated with $V_{GS} = 2.5 \text{ V}$. At what value of V_{DS} does the transistor enter the saturation region? What value of I_D is obtained in saturation?

$$\begin{aligned} 5.9 \quad V_{DS \text{ sat}} &= V_{ov} \\ V_{ov} &= V_{GS} - V_t = 2.5 - 1 = 1.5 \text{ V} \\ \Rightarrow V_{DS \text{ sat}} &= 1.5 \text{ V} \end{aligned}$$

In saturation:

$$i_D = \frac{1}{2} K'_n \left(\frac{W}{L}\right) V_{ov}^2 = \frac{1}{2} K_n V_{ov}^2$$

$$i_D = \frac{1}{2} \times \frac{1 \text{ mA}}{\text{V}^2} \times (1.5 \text{ V})^2$$

$$i_D = (1.125 \text{ mA})$$

Problem

5.14 Consider an n -channel MOSFET with $t_{ox} = 9 \text{ nm}$, $\mu_n = 500 \text{ cm}^2/\text{V}\cdot\text{s}$, $V_t = 0.7 \text{ V}$, and $W/L = 10$. Find the drain current in the following cases:

- (a) $v_{GS} = 5 \text{ V}$ and $v_{DS} = 1 \text{ V}$
- (b) $v_{GS} = 2 \text{ V}$ and $v_{DS} = 1.3 \text{ V}$
- (c) $v_{GS} = 5 \text{ V}$ and $v_{DS} = 0.2 \text{ V}$
- (d) $v_{GS} = v_{DS} = 5 \text{ V}$

$$5.14 \quad t_{ox} = 9 \text{ nm}, \quad \mu_n = 500 \text{ cm}^2/\text{V}\cdot\text{s},$$

$$V_t = 0.7 \text{ V}, \quad \frac{W}{L} = 10$$

$$k_n' = \mu_n \cdot C_{ox} = \mu_n \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

$$500 \times 10^{-4} \times \frac{3.45 \times 10^{-11}}{9 \times 10^{-9}} = 191.7 \frac{\mu\text{A}}{\text{V}^2}$$

(a) triode region: $V_{DS} < V_{GS} - V_t$

$$\begin{aligned} i_D &= k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \\ &= 191.7 \times 10^{-6} \times 10 \\ &\quad \left[(5 - 0.7) \times 1 - \frac{1}{2} \times 1^2 \right] = 7.3 \text{ mA} \end{aligned}$$

(b) saturation region: $V_{DS} > V_{GS} - V_t$

$$\begin{aligned} i_D &= \frac{1}{2} \times 191.7 \times 10^{-6} \times 10 \times (2 - 0.7)^2 \\ &= 1.62 \text{ mA} \end{aligned}$$

(c) triode region: $V_{DS} < V_{GS} - V_t$

$$\begin{aligned} i_D &= 191.7 \times 10^{-6} \times 10 \left[(5 - 0.7) \times 0.2 - \frac{1}{2} (0.2)^2 \right] \\ &= 1.61 \text{ mA} \end{aligned}$$

(d) saturation region: $V_{DS} > V_{GS} - V_t$

$$\begin{aligned} i_D &= \frac{1}{2} \times 191.7 \times 10^{-6} \times 10 \times (5 - 0.7)^2 \\ &= 17.7 \text{ mA} \end{aligned}$$

Problem

5.17 An NMOS transistor having $V_t = 1$ V is operated in the triode region with v_{DS} small. With $V_{GS} = 1.5$ V, it is found to have a resistance r_{DS} of 1 k Ω . What value of V_{GS} is required to obtain $r_{DS} = 200$ Ω ? Find the corresponding resistance values obtained with a device having twice the value of W .

$$5.17 \text{ Eq.4.13: } r_{DS} = \left[k'_n \frac{W}{L} (V_{GS} - V_t) \right]^{-1}$$

therefore:

$$\frac{r_{DS1}}{r_{DS2}} = \frac{V_{GS2} - V_t}{V_{GS1} - V_t} \Rightarrow \frac{1000}{200} = \frac{V_{GS2} - 1}{1.5 - 1}$$

$$\Rightarrow V_{GS2} = 3.5 \text{ V}$$

Now for a device with twice the width:

$$\frac{r_{DS1}}{r_{DS2}} = \frac{W_2(V_{GS2} - V_t)}{W_1(V_{GS2} - V_t)}$$

for $V_{GS} = 1.5$ V

$$\frac{r_{DS1}}{r_{DS2}} = 2 \Rightarrow r_{DS2} = \frac{1000}{2} = 500 \text{ } \Omega$$

$$\text{for } V_{GS} = 3.5 \text{ V } r_{DS2} = \frac{200}{2} = 100 \text{ } \Omega$$

Problem

5.18 A particular enhancement MOSFET for which $V_t = 0.5$ V and $k'_n(W/L) = 0.1$ mA/V² is to be operated in the saturation region. If i_D is to be 12.5 μ A, find the required v_{GS} and the minimum required v_{DS} . Repeat for $i_D = 50$ μ A.

$$5.18 \quad V_{tn} = 0.5 \text{ V}$$

2

$$k'_n \frac{W}{L} = 0.1 \text{ mA/V}^2$$

Saturation mode

$$v_{DS} \geq (v_{GS} - V_{tn})$$

for $i_D = 12.5$ μ A

$$v_{GS} = 1.0 \text{ V and } v_{DS} \geq 0.5 \text{ V}$$

for $i_D = 50$ μ A

$$v_{GS} = 1.5 \text{ V, and } v_{DS} \geq 1.0 \text{ V}$$

Problem

5.22 For an NMOS transistor, for which $V_t = 0.5$ V, operating with v_{GS} in the range of 0.8 V to 1.8 V, what is the largest value of v_{DS} for which the channel remains continuous?

$$5.22 \quad V_t = 0.5 \text{ V.}$$

$$0.8 \leq v_{GS} \leq 1.8 \text{ V.}$$

largest v_{DS} for ohmic operation?

$$v_{DS} \leq v_{OV} = v_{GS} - V_t = 0.3 \sim 1.3 \text{ V.}$$

$\therefore v_{DS} \leq 0.3$ V will ensure ohmic mode

Problem

5.47 The transistor in the circuit of Fig. P5.47 has $k'_n = 0.4 \text{ mA/V}^2$, $V_t = 0.5 \text{ V}$, and $\lambda = 0$. Show that operation at the edge of saturation is obtained when the following condition is satisfied:

$$\left(\frac{W}{L}\right)R_D = 1.5 \text{ k}\Omega$$

 


Figure P5.47

$$k'_n = 0.4 \text{ mA/V}^2$$

$$V_t = 0.5 \text{ V},$$

$$\lambda = 0$$

$$\text{sat. boundary } V_{GD} = 0.5 \text{ V}, = I_D R_D$$

$$0.5 \text{ V}, = \frac{1}{2} k'_n \frac{W}{L} (1.8 - 0.5)^2 R_D$$

$$\therefore \frac{W}{L} R_D = 1.48 \text{ k}\Omega$$

Problem P5.50

Both NMOS

$$V_T = 0.5 \text{ V}$$

$$\mu_n C_{ox} = 250 \mu\text{A}/\text{V}^2$$

$$\lambda = 0$$

$$L_1 = L_2 = 0.25 \mu\text{m}$$

What is value of gate width of both NMOS

and value of R to obtain values of voltages and current indicated?

 


Figure P5.50

$$L_1 = L_2 = 0.25 \mu\text{m}$$

$$R = \frac{2.5 - 1.8}{0.25 \text{ mA}} = 2.8 \text{ k}\Omega$$

for Q_1

$$0.25 \text{ mA} = \frac{1}{2} (250 \mu\text{A}/\text{V}^2) \frac{W_1}{L_1} (1 - 0.5)^2$$

$$\therefore W_1 = 8L_1 = 2 \mu\text{m}$$

for Q_2

$$0.25 \text{ mA} = \frac{1}{2} (250 \mu\text{A}/\text{V}^2)$$

$$\frac{W_2}{L_2} (1.8 - 1.0 - 0.5)^2$$

$$\therefore W_2 = 22.2L_2 = 5.6 \mu\text{m}$$

Problem

5.57 For each of the circuits shown in Fig. P5.57, find the labeled node voltages. The NMOS transistors have $V_t = 1\text{ V}$ and $k'_n W/L = 5\text{ mA/V}^2$.


 


Figure P5.57

 5.57 (a) $V_t = 1\text{V}$, $k_n \frac{W}{L} = 5 \frac{\text{mA}}{\text{V}^2}$, $\lambda = 0$



Q_1 is in saturation

Q_2 assume sat.

$$V_2 = -V_{GS2} = -2.5 + I_D 1\text{k}$$

$$-V_{GS2} = -2.5 + (1) \left(\frac{1}{2} \right) (5) [V_{GS2} - 1]^2$$

$$0 = 2.5 V_{GS2}^2 - 4V_{GS2} + 0$$

$$V_{GS2} = +1.6\text{V} \text{ (0, bad root } < V_t \text{)}$$


$$I_D = 0.90\text{ mA}$$

$$V_{GS1} = +1.6\text{V}$$

$$V_1 = +2.5 - V_{GS1} = +0.9\text{V}$$

$$V_{GD2} = -0.9 < V_t \therefore Q_2 \text{ sat.}$$

$$V_2 = -1.6\text{V.}$$

 

Both Q_1 and Q_2 in sat.

$$(V_{GD1} = V_{GD2} = 0)$$

\therefore both Q_1 and Q_2 have same V_{GS}

$$+5 - 1\text{k}I_D - V_{GS} - V_{GS} - 1\text{k}I_D = 0$$

$$5 - (2) \left(\frac{1}{2} \right) (5) [V_{GS} - 1]^2 - 2V_{GS} = 0$$

$$0 = -5V_{GS}^2 + 8V_{GS}$$

$$V_{GS} = +1.60\text{V}, \text{ (bad root } < V_t \text{)}$$

$$I_D = 0.90\text{mA} = \frac{1}{2} \left(5 \frac{\text{mA}}{\text{V}^2} \right) [1.6 - 1]^2$$

$$V_1 = +5 - (1\text{k})I_D = +4.1\text{V.}$$

$$V_2 = V_1 - V_{GS} = +2.5\text{V.}$$

$$V_3 = V_2 - V_{GS} = (1\text{k})I_D = 0.9\text{V}$$

Problem

5.76 For the NMOS amplifier in Fig. P5.76, replace the transistor with its T equivalent circuit, assuming $\lambda = 0$. Derive expressions for the voltage gains v_s/v_i and v_d/v_i .


 


Figure P5.76

 

$$v_i = (g_m v_{gs}) \left(\frac{1}{g_m} + R_S \right)$$

$$v_d = -g_m v_{gs} R_D$$

$$v_s = +g_m v_{gs} R_S$$

$$\therefore \frac{v_s}{v_i} = \frac{R_S}{\frac{1}{g_m} + R_S} = \frac{+g_m R_S}{1 + g_m R_S}$$

$$\frac{v_d}{v_i} = \frac{-R_D}{\frac{1}{g_m} + R_S} = \frac{-g_m R_D}{1 + g_m R_S}$$

Problem


*5.79 Figure P5.79 shows a discrete-circuit amplifier. The input signal v_{sig} is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite).

(a) If the transistor has $V_t = 1$ V, and $k_n = 2$ mA/V², verify that the bias circuit establishes $V_{GS} = 2$ V, $I_D = 1$ mA, and $V_D = +7.5$ V. That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.

(b) Find g_m and r_o if $V_A = 100$ V.

(c) Draw a complete small-signal equivalent circuit for the amplifier, assuming all capacitors behave as short circuits at signal frequencies.

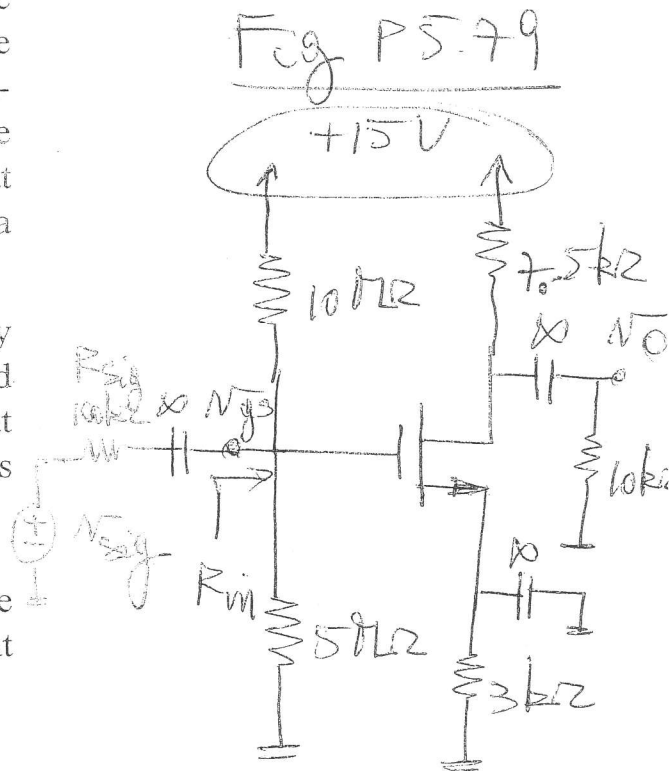(d) Find R_{in} , v_{gs}/v_{sig} , v_o/v_{gs} , and v_o/v_{sig} .



$$5.79 \quad V_t = 1V, k_n' = \frac{W}{L} = 2 \text{ mA/V}^2$$

$$(a) \text{ dc analysis } V_G = \frac{5}{15} 15V = 5V, \text{ assume}$$

$$I_D = 1 \text{ mA}$$

$$V_S = 3V, V_{GS} = 2V, V_{OV} = 1V.$$


$$I_D = \frac{1}{2} k' V_{OV}^2 = 1 \text{ mA (check)}$$

$$V_D = V_{DD} - I_D R_D = 7.5 \text{ V.}$$

$$(b) r_0 = \frac{V_A}{I_D} = \frac{100 \text{ V.}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$g_m = \sqrt{2k_n I_D} = 2 \text{ mS}$$

(c)

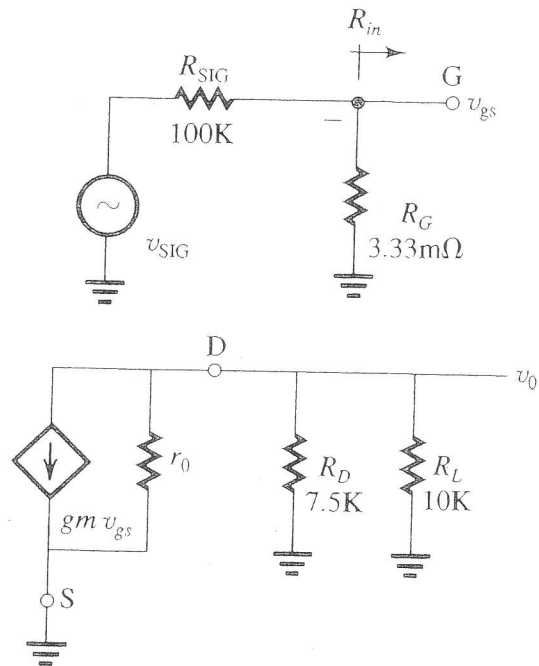

$$(d) R_{in} = R_G = 3.33 \text{ M}\Omega$$

$$\frac{v_{gs}}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = 0.97$$

$$\frac{v_0}{v_{gs}} = -g_m (r_0 \parallel R_D \parallel R_L) = -8.2$$

$$\frac{v_0}{v_{sig}} = -8.0$$


Problem

5.93 A CG amplifier using an NMOS transistor for which $g_m = 4 \text{ mA/V}$ has a $5\text{-k}\Omega$ drain resistance R_D and a $5\text{-k}\Omega$ load resistance R_L . The amplifier is driven by a voltage source having a 500Ω resistance. What is the input resistance of the amplifier? What is the overall voltage gain G_v ? By what factor must the bias current I_D of the MOSFET be changed so that R_{in} matches R_{sig} ?

$$5.93 \quad R_{in} = \frac{1}{g_m} = 250 \Omega$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} g_m (R_D \parallel R_L) = +3.3$$

 $g_m = \sqrt{2k_n I_D}$, so for $\frac{1}{g_m} = R_{sig}$, g_m must decrease to $1/2$, and I_D must decrease to $1/4$



Problem

5.112 The NMOS transistor in the CS amplifier shown in Fig. P5.112 has $V_t = 0.7$ V and $V_A = 50$ V.

- (a) Neglecting the Early effect, verify that the MOSFET is operating in saturation with $I_D = 0.5$ mA and $V_{OV} = 0.3$ V. What must the MOSFET's k_n be? What is the dc voltage at the drain?
- (b) Find R_{in} and G_v .
- (c) If v_{sig} is a sinusoid with a peak amplitude \hat{v}_{sig} , find the maximum allowable value of \hat{v}_{sig} for which the transistor remains in saturation. What is the corresponding amplitude of the output voltage?
- (d) What is the value of resistance R_s that needs to be inserted in series with capacitor C_s in order to allow us to double the input signal \hat{v}_{sig} ? What output voltage now results?

5.112

$$V_t = 0.7 \text{ V.}$$

$$V_A = 50 \text{ V.}$$

$$\text{a) with } I_D = 0.5 \text{ mA}$$

$$V_G = +2 \text{ V } V_S = +1 \text{ V. } V_{GS} = +1 \text{ V.}$$

$$V_{OV} = 0.3 \text{ V}$$

$$0.5 \text{ mA} = \frac{1}{2} k_n V_{OV}^2 \Rightarrow k_n = 11.1 \frac{\text{mA}}{\text{V}^2}$$

$$V_D = 5 - (5 \text{ K})(0.5 \text{ mA}) = +2.5 \text{ V.}$$

$$V_{GD} = -0.5 \text{ V} < V_t \therefore \text{Saturation}$$

$$\text{b) } R_{in} = 200 \text{ K} \parallel 300 \text{ K} = 120 \text{ k}\Omega$$

$$G_v = \frac{v_o}{v_{sig}} = -\frac{R_{in}}{120 \text{ K} - R_{in}} g_m$$

$$(5 \text{ K} \parallel r_o \parallel 5 \text{ K})$$

$$g_m = \frac{2I_D}{V_{OV}} = 3.33 \text{ mS}$$

$$r_o = \frac{V_A}{I_D} = 100 \text{ k}\Omega$$

$$G_v = -4.1$$

$$\text{c) } v_{sig} = \hat{v}_{sig} \sin \omega t$$

$$g_m(5 \text{ K} \parallel 5 \text{ K} \parallel 100 \text{ K}) = 8.12$$

$$V_{gd} + V_{GD} = \hat{v}_o + \frac{\hat{v}_o}{8.12} - 0.5$$

$$\leq V_t = 0.7 \text{ V.}$$

$$\hat{v}_o \text{ max} = 1.07 \text{ V}_{pk}$$

$$\therefore \hat{v}_{gs} \text{ max} = \frac{\hat{v}_o \text{ max}}{8.12} = 132 \text{ mV}_{pk}$$

$$\hat{v}_{sig} \text{ max} = \frac{\hat{v}_o \text{ max}}{4.1} = 261 \text{ mV}_{pk}$$

$$\text{d) Add } R_s = \frac{I}{g_m} = 300 \Omega,$$

$$\text{then } v_{gs} = \frac{v_g}{1 + g_m R_s} = \frac{v_g}{2}$$

$$\frac{g_m R_L}{1 + g_m R_s} = \left| \frac{v_o}{v_g} \right| = 4.06$$

$$\hat{v}_o + \frac{\hat{v}_o}{4.06} - 0.5 \leq 0.7 \text{ V.}$$

$$\Rightarrow \hat{v}_o \text{ max} = 0.96 \text{ V.}$$