
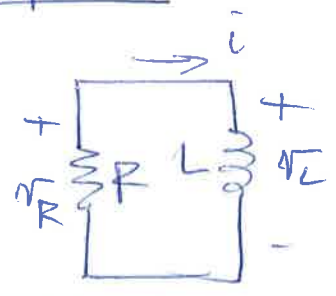


Review
Source free

Chapters

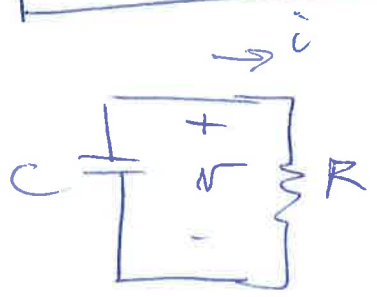

$$\boxed{\frac{di}{dt} + \frac{R}{L} i = 0} \rightarrow \text{sol: } i(t) = I_0 e^{-\frac{Rt}{L}}$$



$$\boxed{\frac{dv}{dt} + \frac{v}{RC} = 0}$$


sol: $v(t) = V_0 e^{-\frac{t}{RC}}$

Driven (forced) network.


$$i(t) = \overset{i(t \rightarrow \infty)}{I_f} + I_0 e^{-\frac{Rt}{L}}$$

$$v(t) = \overset{v(t \rightarrow \infty)}{V_f} + V_0 e^{-\frac{t}{RC}}$$

Constitutive equations

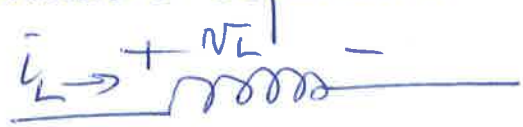


$$\boxed{v_L = L \frac{di_L}{dt}}$$

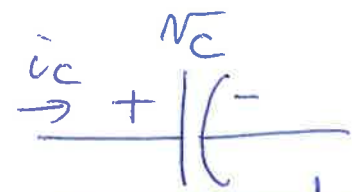

$$\boxed{i_C = C \frac{dv_C}{dt}}$$

Passive sign convention

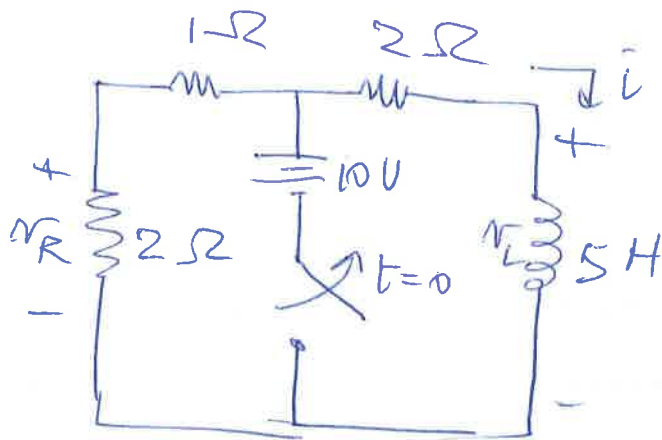

- ① Write differential eq for v_R for $t > 0$
 ② Solve characteristic equation
 ③ v_R ? Before opening the switch, just after opening switch, and at $t = 1s$

④ After opening switch.

$$L \frac{di}{dt} + \frac{R_{eq}}{i} = 0 \quad R_{eq} = 5 \Omega$$

$$v_R = -2i$$

$$L \frac{d\left(-\frac{v_R}{2}\right)}{dt} + 5\left(-\frac{v_R}{2}\right) = 0$$

$$2.5 \frac{dv_R}{dt} + 2.5 v_R = 0 \quad \frac{dv_R}{dt} + v_R = 0$$

$$v_R = A e^{\lambda t} \quad \text{⑤} \quad A \lambda e^{\lambda t} + A e^{\lambda t} = 0$$

$$\lambda + 1 = 0$$

$$\lambda = -1$$

$$\rightarrow v_R = A e^{-t}$$

⑥ $t = 0^- \quad i(0^-) = 5A = i(0^+) \rightarrow v_R(0^+) = -2i(0^+) = -10$


$$\rightarrow A = -10$$

$$v_R(0^-) = \frac{2}{3} 10 = 6.667V$$

$$v_R(1) = -10e^{-1} = -3.679V$$

(61)

(3)

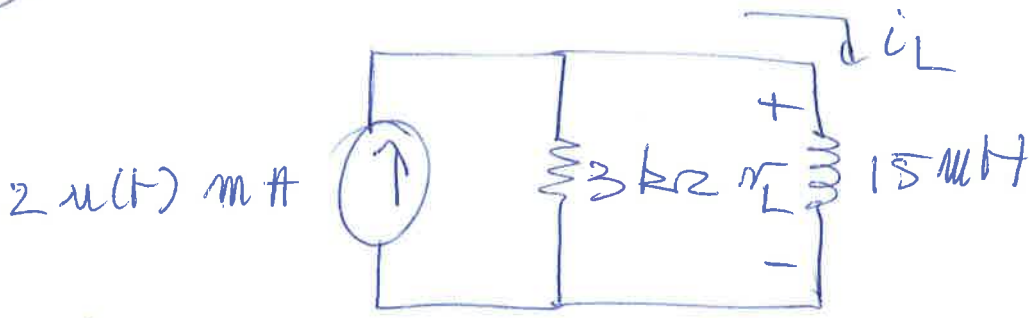

- (a) find $i_L(t)$
- (b) Use $i_L(t)$ to get $v_L(t)$.

$$i_L(t) = i_f + A e^{-\frac{t}{\tau}} = i_f + A e^{-2000t}$$

$$\tau = \frac{L}{R} = \frac{15\text{ mH}}{3\text{ k}\Omega} = 5 \cdot 10^{-6}$$

$$\frac{1}{\tau} = 2000$$

$t \rightarrow \infty \quad i_f = 2\text{ mA}$


$t = 0^- \quad i_L(0^-) = 0 = i_L(0^+) \rightarrow A = -2\text{ mA}$

$$i_L(t) = [2 - 2e^{-2000t}] u(t) \text{ mA}$$

$t > 0$

$$v_L = L \frac{di_L}{dt} = 15 \cdot 10^{-3} (-2000^2) (-2000) e^{-2000t}$$

$$v_L(t) = 6e^{-2000t} \text{ V}$$

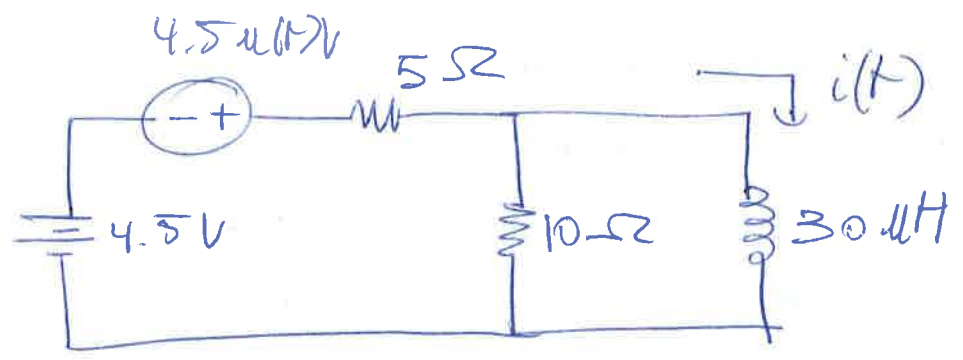

Ⓐ i(t) vs t Ⓑ i(t) at t = 1.5 μs.

Natural response $\tau = \frac{L}{R_{TH}} = \frac{30 \mu\text{H}}{(5 // 10)} = 9 \mu\text{s}$

$$i(t) = i_f + A e^{-\frac{10^6}{9}t}$$

$$i_f = \frac{9}{5} \text{ A}$$

$$i(t) = \frac{9}{5} + A e^{-\frac{10^6}{9}t}$$

At t = 0 $i(0^-) = i(0^+) = \frac{4.5}{5} \rightarrow A = -\frac{4.5}{5} = -0.9$


So $i(t) = \frac{9}{5} - 0.9 e^{-\frac{10^6}{9}t} \text{ A}$

Ⓑ at t = 1.5 μs

$i(t) = 1.038 \text{ A}$

66

5

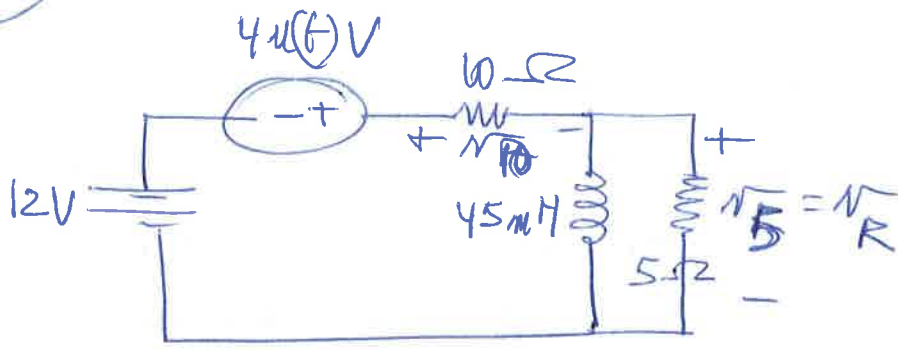

(a) Find $v_R(t)$ $\forall t$

(b) $v_R(t)$ at $t = 2ms$

(c) $\tau = \frac{L}{R_{eq}} = \frac{45 \times 10^{-3}}{(5//10)} = 0.0135s$

$v_R(t) = v_f + v_n$

\downarrow
 $= 0$ since short acts as a short
 $- 74.07t$

$v_R(t) = A e^{-74.07t}$

$t=0^- \quad i_L(0^-) = \frac{12}{10} = 1.2A = i_L(0^+)$

at $t=0^+$ KVL $12 + 4 \neq v_R(0^+) + 10 \left[1.2 + \frac{v_R(0^+)}{5} \right]$


$\rightarrow v_R(0^+) = \frac{4}{3} V$

$\rightarrow v_R(t) = \frac{4}{3} e^{-74.07t}$

(b) at $t = 2ms \rightarrow v_R(2ms) = 1.15V$

69 The switch in circuit below has been open for a long time. (a) Find $i_L(t)$ for $t < 0$.
 (b) $i_L(t)$ for $t > 0$

6

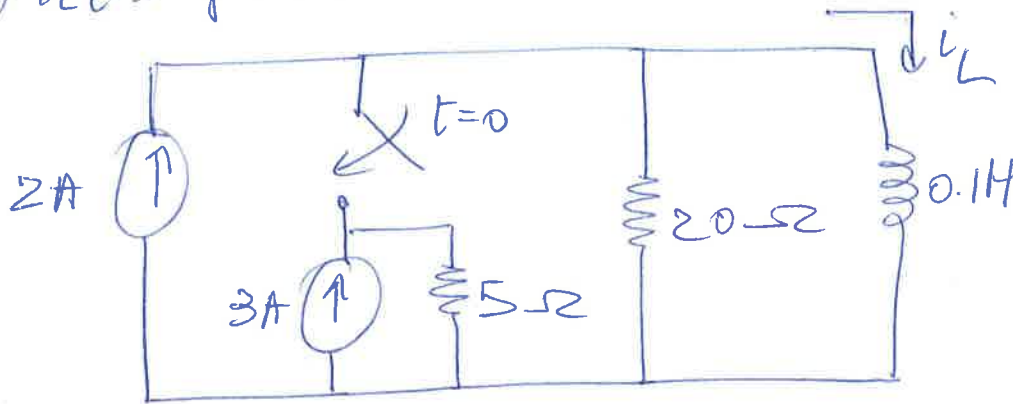

$t < 0$ ~~$i_L(t) = 2A$~~ $i_L(0^-) = 2A$



$$i_L(t) = i_f + A e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{(5/20)} = \frac{L}{4}$$

$$i_L(t) = \underset{5A}{i_f} + A e^{-40t}$$

$\rightarrow A = -3$ since $i_L(0^+) = i_L(0^-) = 2A$



$\Rightarrow i_L(t) = 5 - 3e^{-40t} \text{ A}$

72

a) i_L for $t < 0$

b) $i_L(0^+)$ c) $i_L(\infty)$; d) $i_L(t) \forall t > 0$

7

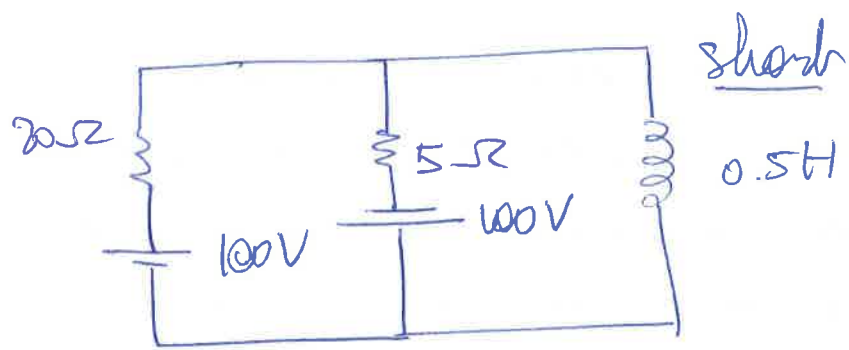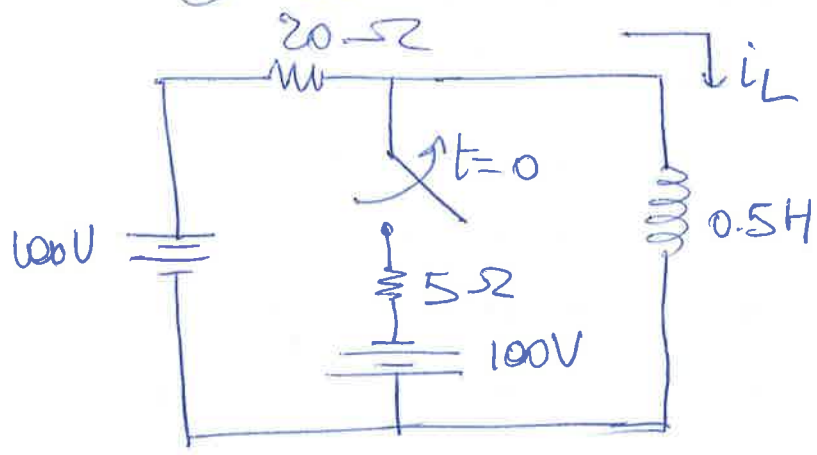

$$i_L(0^-) = \frac{100}{20} - \frac{100}{5} = -15A \quad t < 0$$

$$i_L(0^+) = -15A$$

$$i_L(\infty) = 5A$$

$$-\frac{t}{\tau} \quad \tau = \frac{0.5}{20} = \frac{1}{40}$$

$$i_L(t) = i_L(\infty) + A e^{-40t}$$

$$i_L(t) = 5A + A e^{-40t}$$


$$i_L(0^+) = -15 \rightarrow A = -20$$

$$i_L(t) = (5 - 20 e^{-40t}) A$$


NETWORK ANALYSIS I

November 12, 2010

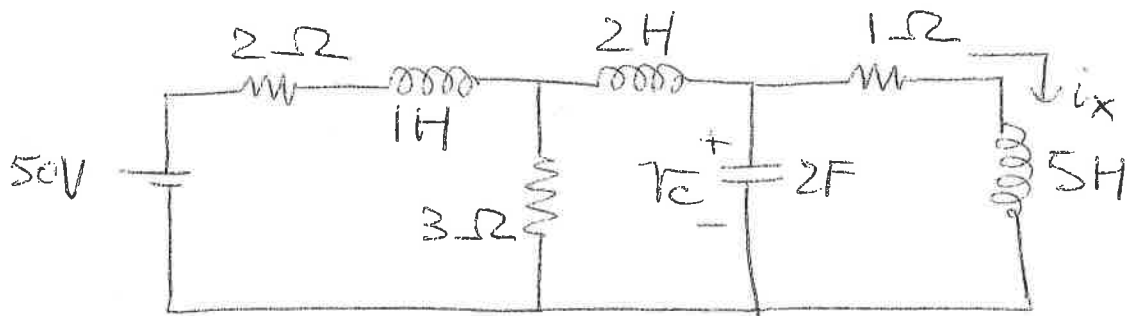I. (25 pts) The circuit below has been connected a long time ago. Calculate the current i_x and the potential V_C across the capacitor.



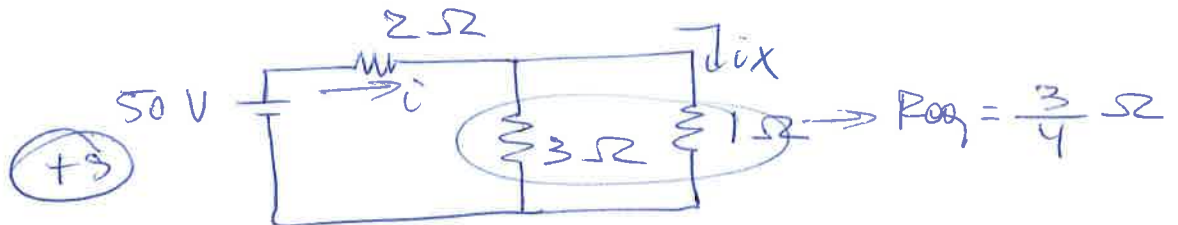long time $\left. \begin{array}{l} L = \text{short} \\ C = \text{open} \end{array} \right\} (+5)$




$$\bar{i} = \frac{50}{2.75} = 18.2 \text{ A} \quad (+5)$$

Current divider

$$\bar{i}_x = \frac{3}{4} \bar{i} = 13.6 \text{ A} \quad (+5)$$

$$V_C = 1\Omega \cdot \bar{i}_x = 13.6 \text{ V} \quad (+5)$$

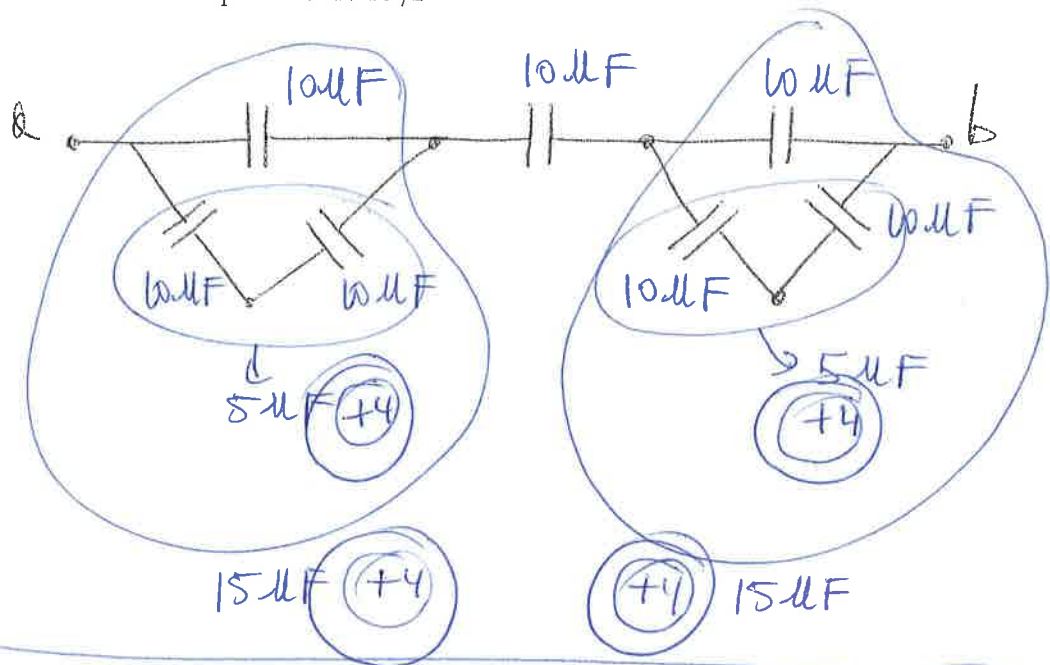II. (25 pts) Determine the equivalent capacitance between points a and b for the network below if all capacitors are $10 \mu\text{F}$.



$$\frac{1}{C_{eq}} = \frac{1}{15 \mu\text{F}} + \frac{1}{15 \mu\text{F}} + \frac{1}{10 \mu\text{F}} = \frac{2}{15 \mu\text{F}} + \frac{1}{10 \mu\text{F}} \quad (+7)$$

$$C_{eq} = \frac{150 \mu\text{F}}{20+15} = \frac{150}{35} \mu\text{F} = 4.286 \mu\text{F}$$

(+2)

III. (25 pts) A voltage $V(t) = 3 \text{ V}$ for $t < 0$, and $3e^{-t/5} \text{ V}$, for $t \geq 0$, is applied to a $300 \mu\text{F}$ capacitor.

(a) Compute the difference in energy stored on capacitor between time $t=0\text{s}$ and $t=2\text{ms}$.

(b) Determine the current flowing through the capacitor at $t = 1.2\text{s}$.

$$\textcircled{a} \quad W_C(t=2\text{ms}) - W_C(0) = \int_0^{t=2\text{ms}} p \, dt = \frac{1}{2} C [V^2(t=2\text{ms}) - V^2(0)]$$

$$= -1.080 \mu\text{J}$$

$+15$

$$\textcircled{b} \quad i_C = C \frac{dV_C}{dt} = 300 \cdot 10^{-6} \left(-\frac{3}{5} e^{-\frac{t}{5}} \right)_{t=1.2\text{s}}$$

$$\textcircled{+10} \quad \Rightarrow i_C = -\frac{900}{5} \cdot 10^{-6} e^{-\frac{1.2}{5}} = -141.593 \mu\text{A}$$

IV. (25 pts) Starting with the time dependent signal for the inductor current i_L shown below, sketch the voltage v_L across the inductor as a function of time in the time interval $0 < t < 60$ ms.

$$L = 0.2 \text{ H}$$

$$v_L = L \frac{di}{dt}$$

