

6. (30 pts) In the circuit below, find the value of the current source I and the resistance R_B to bias the transistor so that $I_c = 1\text{mA}$ and $V_C = 1.5\text{ V}$. Assume $\beta = 100$.

