

BJT equations.

DC Analysis

$$I_C = I_S e$$

$$I_B = I_C / \beta$$

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

$$V_{BE} / V_T$$

$$V_T = 25 \text{ mV}$$

$$\text{at } T = 300 \text{ K}$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}; \quad \alpha = \frac{\beta}{\beta + 1}$$



AC Analysis

$$g_m = \frac{I_C}{V_T}; \quad r_{\pi} = \frac{V_T}{I_B} = \frac{\beta}{g_m}; \quad r_o = \frac{V_A}{I_C}$$

$$r_e = \frac{\alpha}{g_m} = \frac{V_T}{I_E}; \quad r_{\pi} = (\beta + 1) r_e$$


Small signal equivalent circuit

Hybrid- π -model

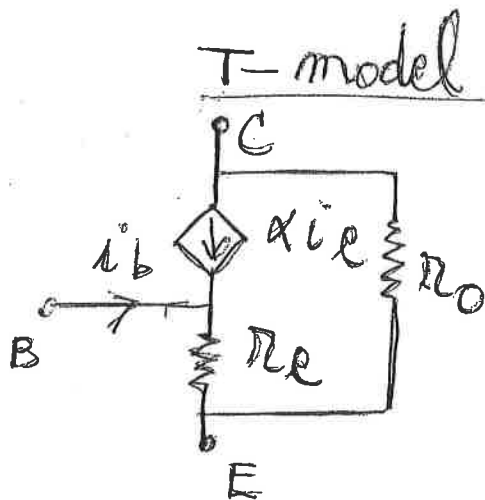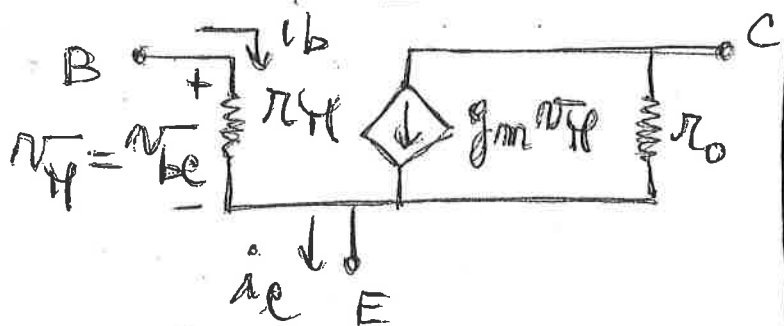

High-frequency hybrid- π

more complete model

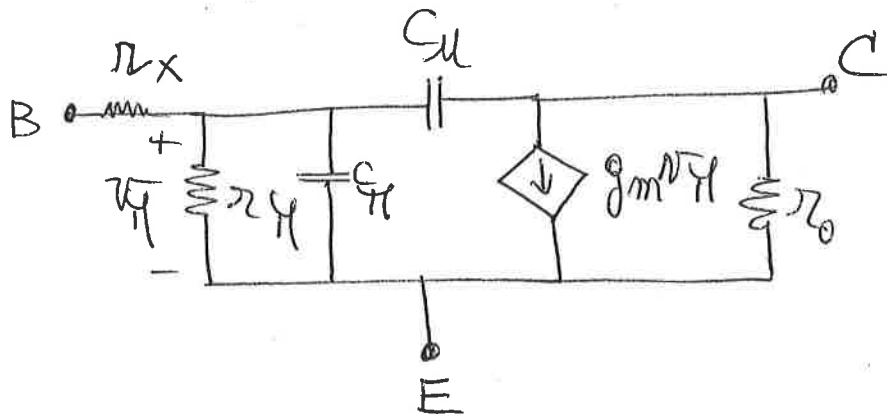

MOSFET Equations

Triode Mode

$$I_D = k_m' \left(\frac{W}{L}\right) \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$n \rightarrow p$ for PMOS


Saturation Mode

$$I_D = \frac{1}{2} k_m' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$


Typically, we assume $\lambda = 0$ in DC analysis.

$$\lambda = 1/V_A$$

DC analysis

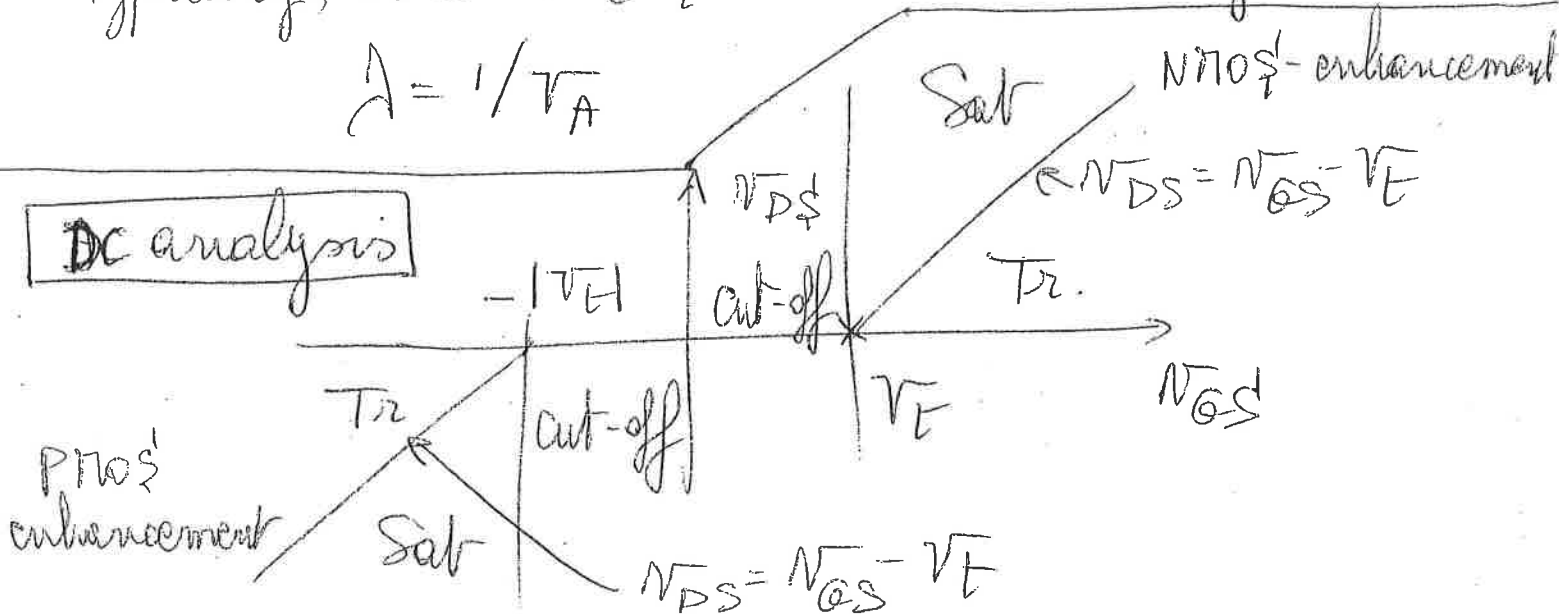


AC analysis

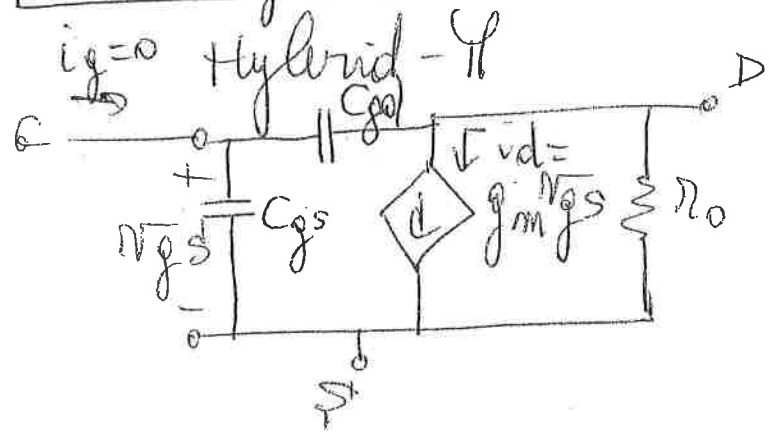

$$g_m = k_m' \frac{W}{L} (V_{GS} - V_T)$$

T-model

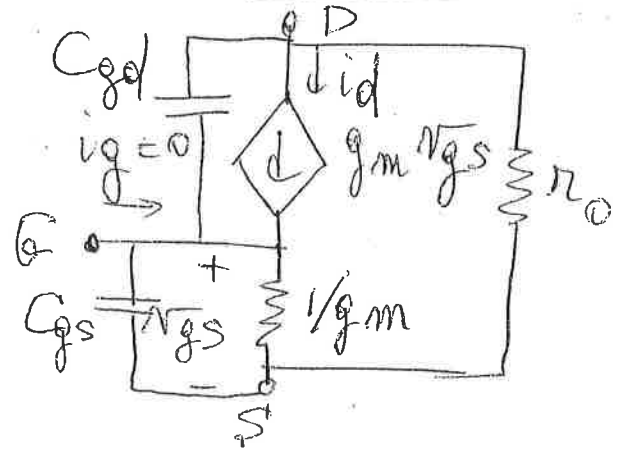

$$r_o = \frac{V_A}{I_D}; \quad r_o = \infty \text{ if neglected}$$