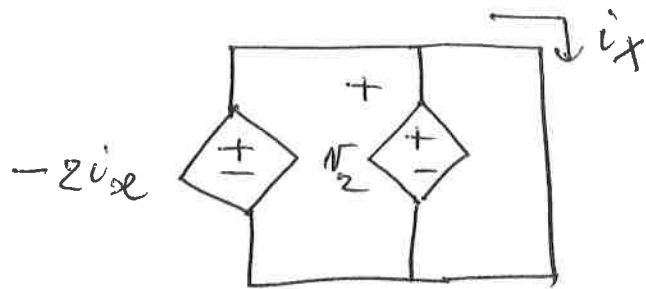


## Problem 2.24

$i_x = -1 \text{ mA}$ , calculate  $v_2$




$$\rightarrow \boxed{v_2 = -2i_x = 2 \text{ mV}}$$

## Review for Test 1
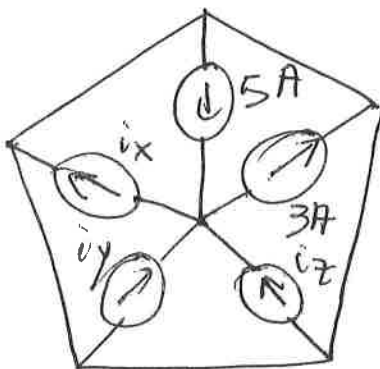
## Problem 3.8

Ⓐ Find  $i_x$  if  $i_y = 2 \text{ A}$   
 $i_z = 0$



$$\text{KCL} \quad \boxed{3 + i_x = 5 + i_y + i_z}$$

$$\rightarrow \boxed{i_x = 2 + i_y + i_z = 4 \text{ A}}$$

Ⓑ Find  $i_y$  if  $i_x = 2 \text{ A}$ ,  $i_z = 2i_y$

$$\begin{aligned} i_y &= 3 + i_x - 5 - i_z \\ &= -2 + 2 - 2i_y \end{aligned}$$

$$\rightarrow \boxed{i_y = 0}$$


Ⓒ Find  $i_z$  if  $i_x = i_y = i_z$

$$5 + i_y + i_z = 3 + i_x$$

$$5 + 2i_x = 3 + i_x$$

$$\rightarrow \boxed{i_x = -2 \text{ A}}$$

Problem 3.13

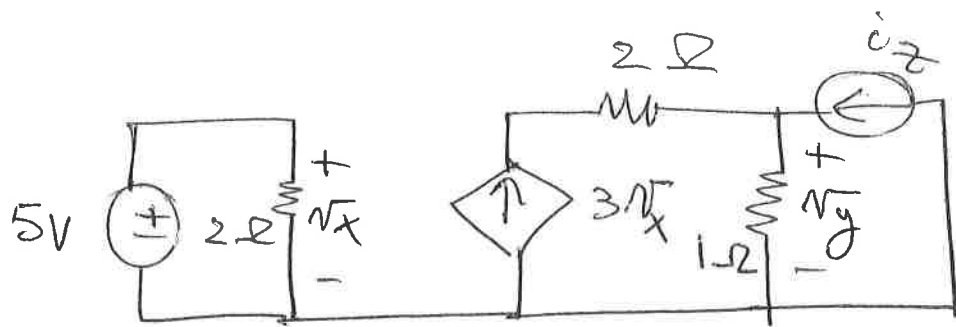

① Calculate  $v_y$  if  $i_2 = -3A$ .

$$v_y = 3v_x + i_2$$


$$v_x = 5 \quad i_2 = -3A \Rightarrow v_y = 15 - 3 = 12V$$

② What voltage would need to replace the 5V source to obtain  $v_y = -6V$  if  $i_2 = 0.5A$ ?

$$v_y = 3v_x + i_2 = -6 \Rightarrow \boxed{v_x = -2.167V}$$

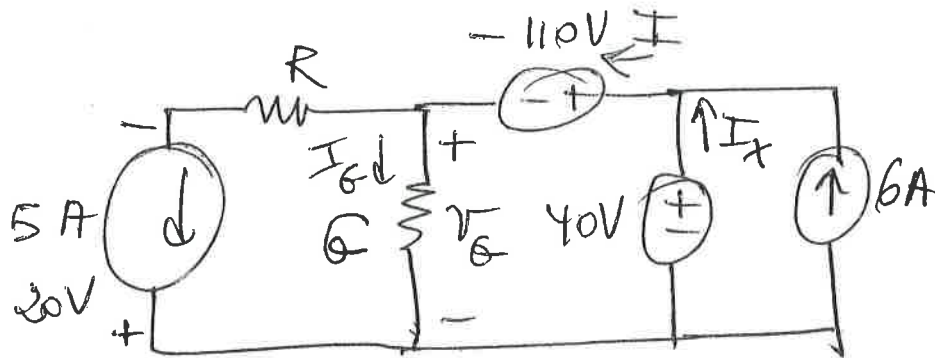Problem 3.15

Find  $R$  &  $G$  in circuit below if the 5A source is supplying 100W and the 40V source is supplying 500W



5A (↓) 100W → Terminal voltage 20V

40V 500W →  $I_x = 12.5A$

(1) KVL  $-40 - 110 + R(5) - 20 = 0$

→  $R = 34\Omega$

(2) KVL  $-V_G - (-110) + 40 = 0$

→  $V_G = 150V$


$I = I_x + 6 = 18.5A$

→  $I_G = 13.5A = G V_G$

→  $G = \frac{13.5}{150} = 90mS$
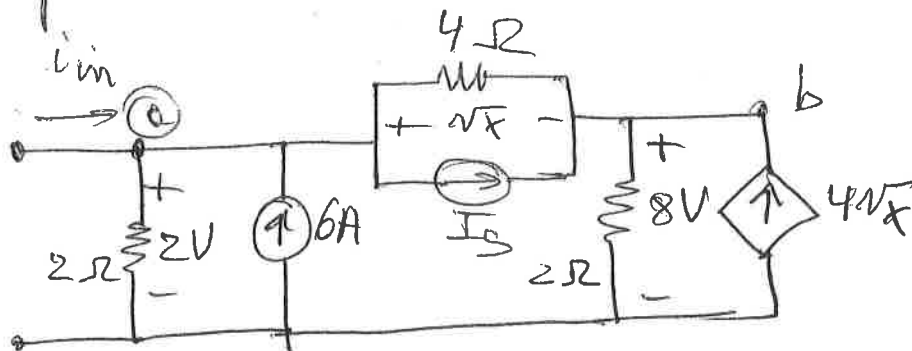
### Problem 3.20

Use Ohm & Kirchhoff's law in the circuit below to find  $v_x$ ,  $i_{in}$ ,  $I_S$ , the power provided by the dependent source.



(a) KVL  $-2 + v_x + 8 = 0$

$$\boxed{v_x = -6V}$$

(b) KCL at (a)  $i_{in} + 6 = \frac{v_x}{4} + I_S + \frac{2}{2} \rightarrow \boxed{i_{in} = 23A}$

(c) KCL at (b)

$$I_S + 4v_x + \frac{v_x}{4} = \frac{8}{2} = 4$$


$$\rightarrow \boxed{I_S = 29.5A}$$

Power provided by dependent source

$$\boxed{8(4v_x) = -192W}$$
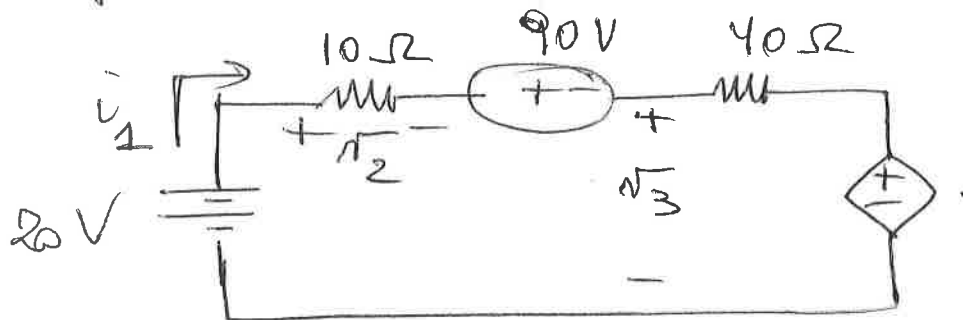
### Problem 3.26

Find  $i_1$  in the circuit below if the dependent voltage source is labeled (a)  $2\sqrt{2}$ ; (b)  $1.5\sqrt{3}$ ; (c)  $-15i_1$



(a) KVL  $-20 + 10i_1 + 90 + 40i_1 + 2\sqrt{2} = 0$

$$\sqrt{2} = 10i_1$$

$$\rightarrow 70 + 70i_1 = 0$$

$$\rightarrow \boxed{i_1 = -1A}$$

(b) KVL  $-20 + 10i_1 + 90 + 40i_1 + 1.5\sqrt{3} = 0$

$$\sqrt{3} = 20 - 10i_1 - 90 = -70 - 10i_1$$

$$\text{or } \boxed{\begin{aligned} \sqrt{3} &= 40i_1 + 1.5\sqrt{3} \\ \rightarrow \sqrt{3} &= -80i_1 \end{aligned}}$$

$$\rightarrow \boxed{i_1 = 1A}$$


(c) KVL

$$-20 + 10i_1 + 90 + 40i_1 - 15i_1 = 0$$


$$\rightarrow \boxed{i_1 = -2A}$$
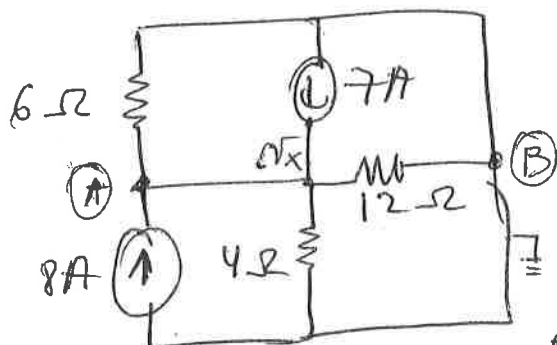
### Problem 3.37

Find the power absorbed by each element in the single-node-pair circuit shown below, and show that the sum is equal to zero.



redraw circuit

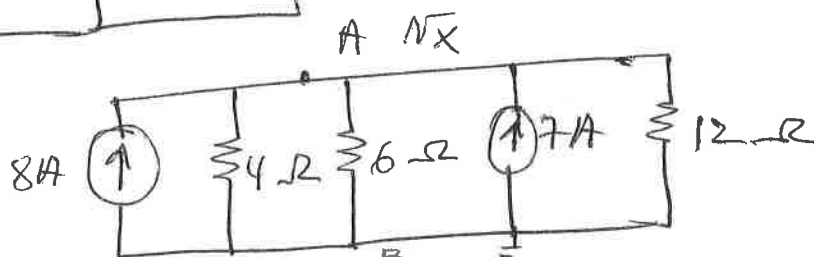

This is a single-node-pair circuit.

Center node

$$8 - \frac{V_x}{6} + 7 - \frac{V_x}{12} - \frac{V_x}{4} = 0 \Rightarrow V_x = 30V$$

Power absorbed by each element

$$P_{8A} = -8V_x = -240W$$

$$P_{6\Omega} = \frac{V_x^2}{6} = 150W$$


$$P_{7A} = -7V_x = -210W$$

$$P_{12\Omega} = \frac{V_x^2}{12} = 75W$$

$$P_{4\Omega} = \frac{V_x^2}{4} = 225W$$

$$\sum P = 0$$

# Problem 3.38

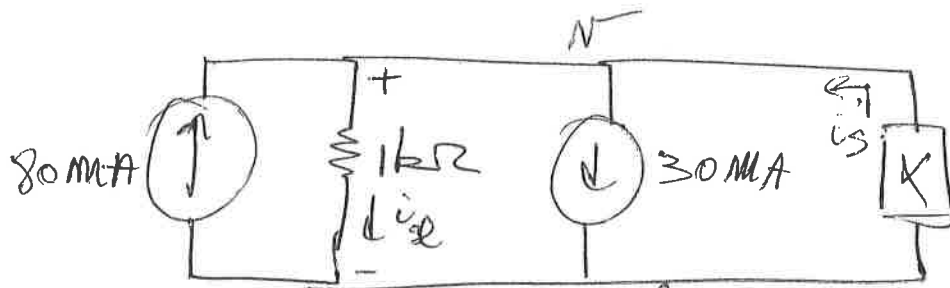

Find power absorbed by element X if it is

- (a) a  $4\text{ k}\Omega$  resistor
- (b)  $20\text{ mA}$  independent source, arrow pointing down
- (c) dependent current source  $2i_x$
- (d)  $60\text{ V}$  independent voltage source

(a)  $80 \times 10^{-3} - 30 \times 10^{-3} = \frac{V}{1000} + \frac{V}{4000} \Rightarrow V = 40\text{ V}$

$P_{4\text{k}\Omega} = \frac{V^2}{10^3} = 400\text{ mW}$

(b)  $80 \times 10^{-3} - 30 \times 10^{-3} - 20 \times 10^{-3} = \frac{V}{1000} \Rightarrow V = 30\text{ V} \Rightarrow P_{20\text{ mA}} = \frac{V^2}{20 \times 10^{-3}} = 600\text{ mW}$

(c)  $80 \times 10^{-3} - 30 \times 10^{-3} - 2i_x = \frac{V}{1000}$       $i_x = \frac{V}{1000}$   
 $\Rightarrow V = 16.67\text{ V} \Rightarrow P = V \cdot 2i_x = 555.8\text{ mW}$


(d)  $i_x = \frac{60}{1000} = 60\text{ mA}$   
 KLC:  $80 - 30 + i_s - i_x = 0$

$\Rightarrow i_s = 10\text{ mA}$

$P_{60\text{ V}} = 60(-10)\text{ mW} = -600\text{ mW}$

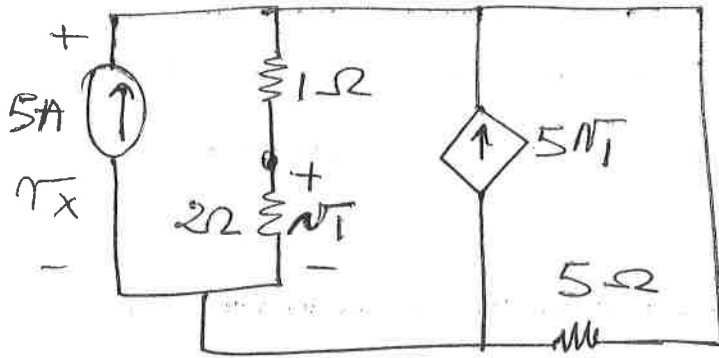Problem 3, 41

Find power absorbed by  $5\ \Omega$  resistor in circuit below



KCL

$$5 + 5i_1 - \frac{v_x}{1+2} - \frac{v_x}{5} = 0$$
$$i_1 = \frac{2}{2+1} v_x = \frac{2v_x}{3}$$

$\Rightarrow$  solve

$$v_x = -1.786\text{V}$$

Power absorbed by  $5\ \Omega$  resistor is

$$\frac{v_x^2}{5} = 638\text{mW}$$