
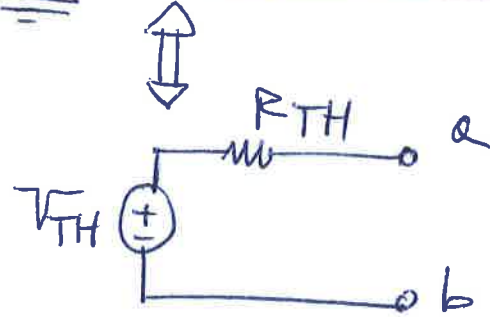


R_{TH} , V_{TH} Calculation



(Extra credit)

Due: Friday Nov. 6, '09 in class

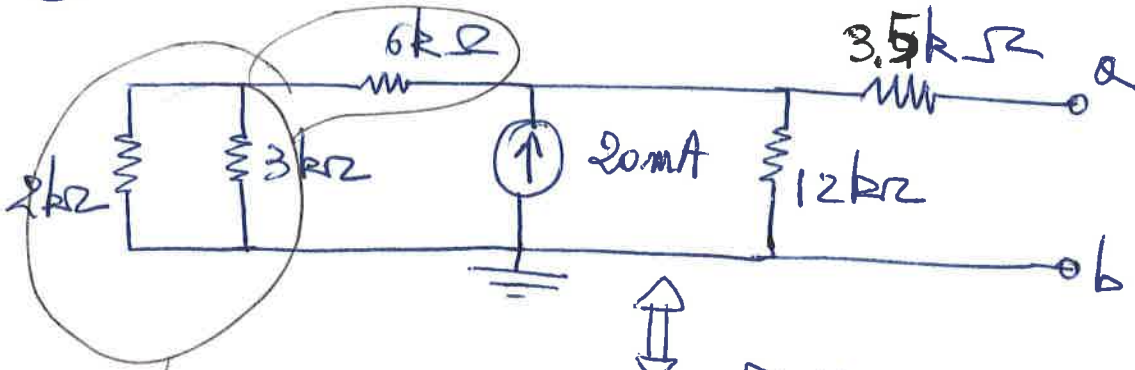① For the network shown below, calculate V_{TH} & R_{TH}



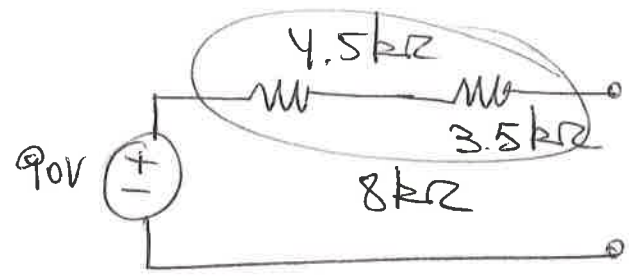
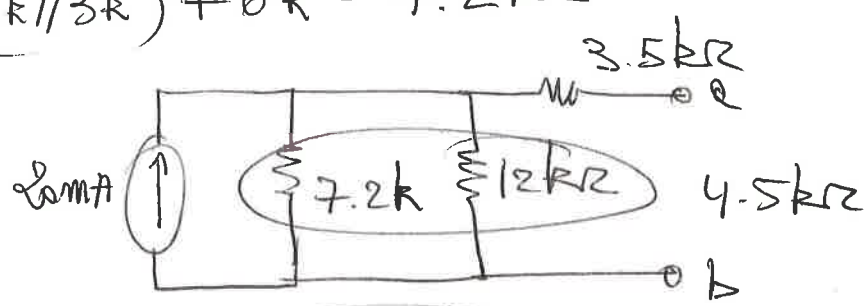
$$\rightarrow (2k // 3k) + 6k = 7.2k\Omega$$



$$V_{TH} = 90V$$

$$R_{TH} = 8k\Omega$$

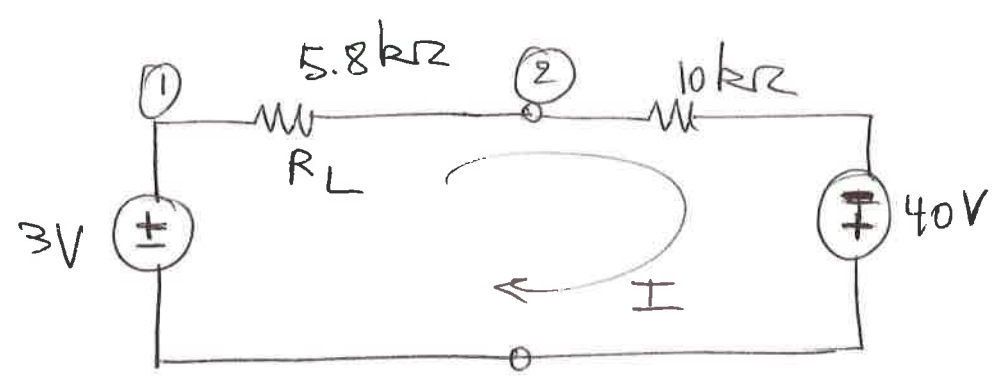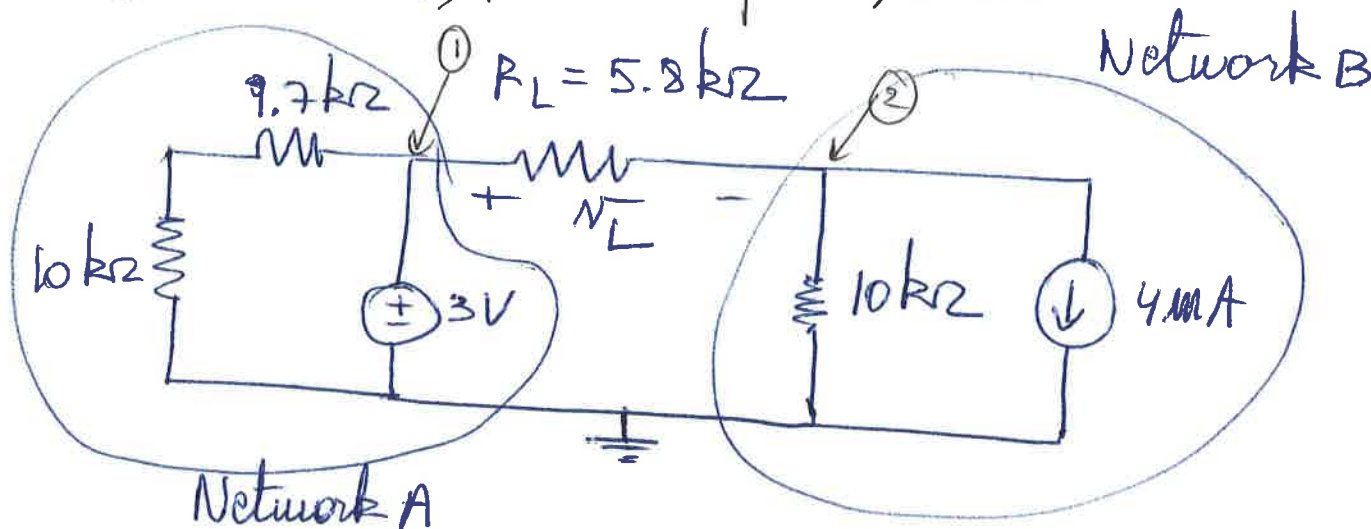② For the network shown below, consider the $5.8 \text{ k}\Omega$ to be a load. Replace networks (A) and (B) by their Thevenin equivalents and calculate the voltage V_L across the load, power dissipated in $5.8 \text{ k}\Omega$.




$$I = \frac{43}{15.8} \text{ mA}$$

$$P_{5.8 \text{ k}\Omega} = I^2 \cdot 5.8 \cdot 10^3 = 42.97 \text{ mW}$$

voltage across load.

$$V_{12} = V_L = 5.8 \text{ k}\Omega \cdot \frac{43}{15.8} \text{ mA} = \frac{5.8(43)}{15.8} \text{ V}$$


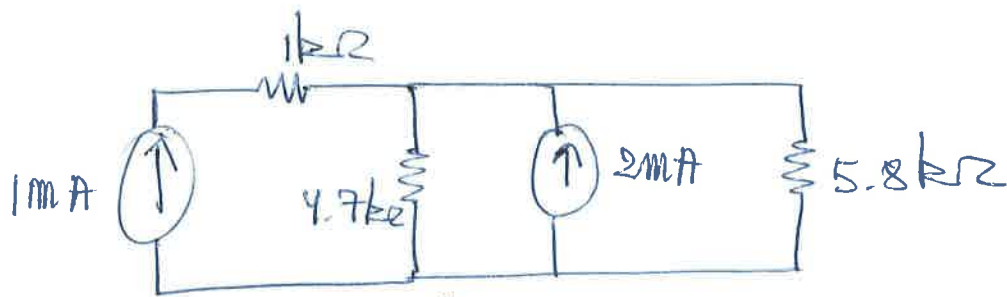
Using source transformation to first simplify the circuit, determine the power dissipated by $5.8\text{ k}\Omega$ resistor



$$i_1 = \frac{4.7}{4.7 + 5.8} 3\text{ mA} = 1.343\text{ mA}$$

$$\rightarrow P_{5.8\text{ k}\Omega} = 5.8 \times 10^3 \cdot i_1^2 = 10.46\text{ mW}$$

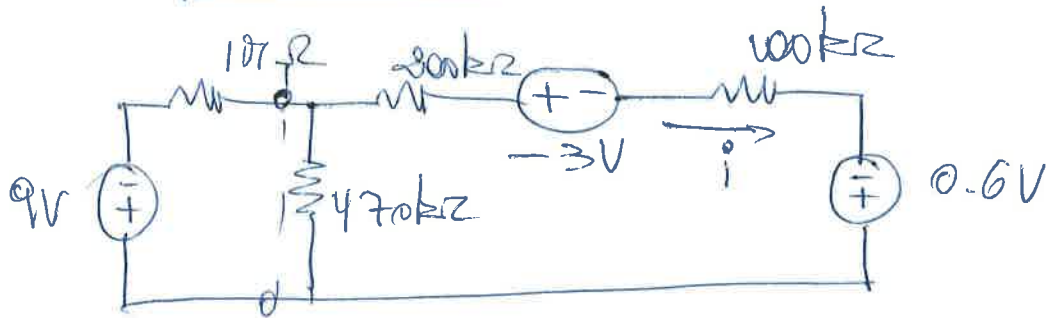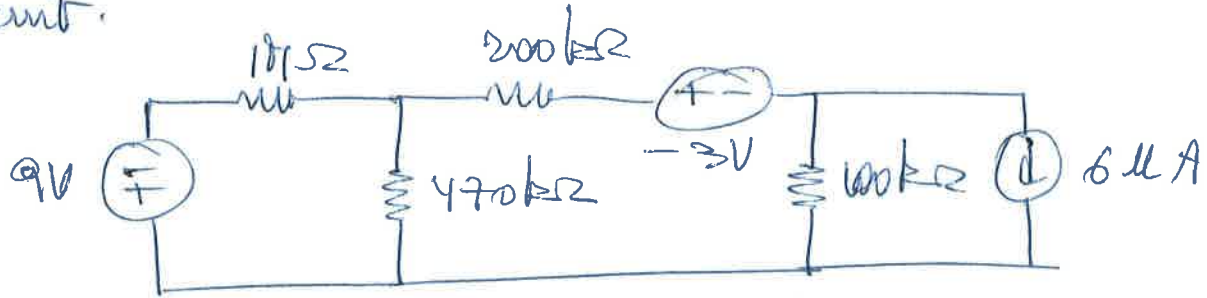
Determine power dissipated by $101\ \Omega$ resistor using source transformation to simplify circuit.



$$R_{TH} = (470k \parallel 300k) = 183.1k\ \Omega$$

$$i_N = -3.6V / 300k\ \Omega = -12\ \mu A$$

$$V_{TH} = R_{TH} i_N = -2.197V$$

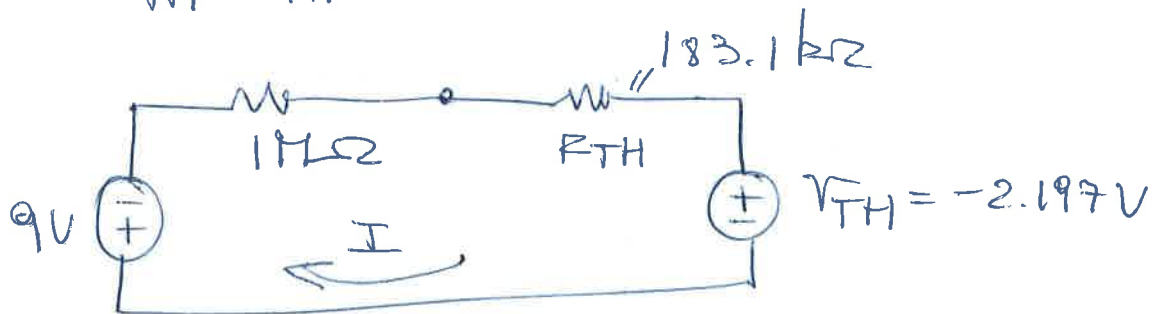


$$9 + 1183.1 \times 10^3 I - 2.197 = 0$$

$$\rightarrow \boxed{I = -5.750\ \mu A}$$

$$\rightarrow \boxed{P = I^2 R = 33.06\ \mu W}$$

$101\ \Omega$

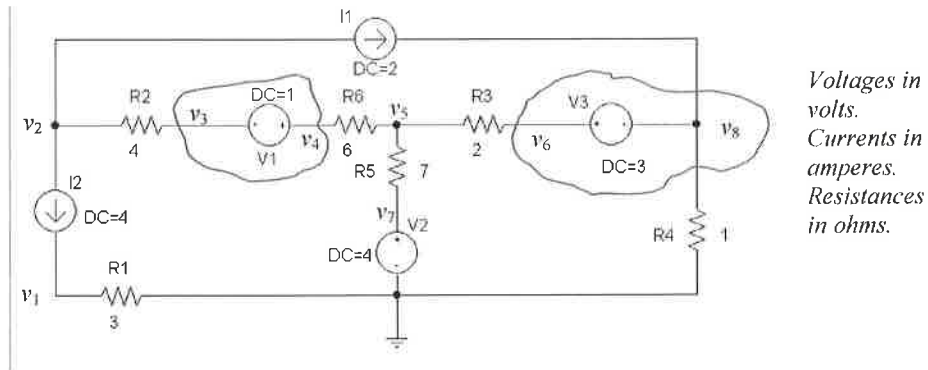24. We begin by selecting the bottom node as the reference, naming each node as shown below, and forming two different supernodes as indicated.



*Voltages in volts.
Currents in amperes.
Resistances in ohms.*

By inspection, $v_7 = 4 \text{ V}$ and $v_1 = (3)(4) = 12 \text{ V}$.

At node 2: $-4 - 2 = (v_2 - v_3)/4$ or $v_2 - v_3 = -24$ [1]

At the 3-4 supernode:
 $0 = (v_3 - v_2)/4 + (v_4 - v_5)/6$ or $-6v_2 + 6v_3 + 4v_4 - 4v_5 = 0$ [2]

At node 5:
 $0 = (v_5 - v_4)/6 + (v_5 - 4)/7 + (v_5 - v_6)/2$ or $-14v_4 + 68v_5 - 42v_6 = 48$ [3]

At the 6-8 supernode: $2 = (v_6 - v_5)/2 + v_8/1$ or $-v_5 + v_6 + 2v_8 = 4$ [4]

3-4 supernode KVL equation: $v_3 - v_4 = -1$ [5]

6-8 supernode KVL equation: $v_6 - v_8 = 3$ [6]

Rewriting Eqs. [1] to [6] in matrix form,

$$\begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 \\ -6 & 6 & 4 & -4 & 0 & 0 \\ 0 & 0 & -14 & 68 & -42 & 0 \\ 0 & 0 & 0 & -1 & 1 & 2 \\ 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_8 \end{bmatrix} = \begin{bmatrix} -24 \\ 0 \\ 48 \\ 4 \\ -1 \\ 3 \end{bmatrix}$$

Solving, we find that

$v_2 = -68.9 \text{ V}, v_3 = -44.9 \text{ V}, v_4 = -43.9 \text{ V}, v_5 = -7.9 \text{ V}, v_6 = 700 \text{ mV}, v_8 = -2.3 \text{ V}.$


The power generated by the 2-A source is therefore $(v_8 - v_6)(2) = 133.2 \text{ W}.$

Should be v_2

v_2

Herby

43. Define four mesh currents

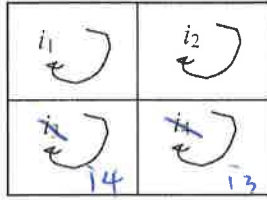

By inspection, $i_1 = -4.5$ A.

We form a supermesh with meshes 3 and 4 as defined above.

$$\text{MESH 2:} \quad 2.2 + 3 i_2 + 4 i_2 + 5 - 4 i_3 = 0 \quad [1]$$

$$\text{SUPERMESH:} \quad 3 i_4 + 9 i_4 - 9 i_1 + 4 i_3 - 4 i_2 + 6 i_3 + i_3 - 3 = 0 \quad [2]$$

$$\text{Supermesh KCL equation:} \quad i_4 - i_3 = 2 \quad [3]$$

Simplifying and combining terms, we may rewrite these three equations as:

$$7 i_2 - 4 i_3 = -7.2 \quad [1]$$

$$-4 i_2 + 11 i_3 + 12 i_4 = -37.5 \quad [2]$$

$$-i_3 + i_4 = 2 \quad [3]$$

Solving, we find that $i_2 = -2.839$ A, $i_3 = -3.168$ A, and $i_4 = -1.168$ A.

The power supplied by the 2.2-V source is then $2.2 (i_1 - i_2) = -3.654$ W.

10

5 points

[1] 30 points

[2] 35 points

[3] 20 points

10 points

47. (a) Select terminal **b** as the reference terminal, and define a nodal voltage V_1 at the top of the 200- Ω resistor. Then,

$$0 = \frac{V_1 - 20}{40} + \frac{V_1 - V_{TH}}{100} + \frac{V_1}{200} \quad [1]$$

$$1.5 i_1 = (V_{TH} - V_1)/100 \quad [2]$$


where $i_1 = V_1/200$, so Eq. [2] becomes $150 V_1/200 + V_1 - V_{TH} = 0$ [2]

Simplifying and collecting terms, these equations may be re-written as:

$$(0.25 + 0.1 + 0.05) V_1 - 0.1 V_{TH} = 5 \quad [1]$$

$$(1 + 15/20) V_1 - V_{TH} = 0 \quad [2]$$

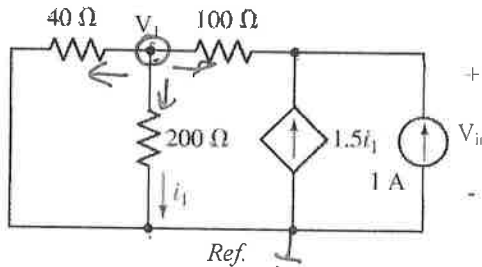Solving, we find that $V_{TH} = 38.89 \text{ V}$. To find R_{TH} , we short the voltage source and inject 1 A into the port:



$$0 = \frac{V_1 - V_{in}}{100} + \frac{V_1}{40} + \frac{V_1}{200} \quad [1]$$

$$1.5 i_1 + 1 = \frac{V_{in} - V_1}{100} \quad [2]$$

$$i_1 = V_1/200 \quad [3]$$

Combining Eqs. [2] and [3] yields $1.75 V_1 - V_{in} = -100$ [4]

Solving Eqs. [1] & [4] then results in $V_{in} = 177.8 \text{ V}$, so that $R_{TH} = V_{in}/1 \text{ A} = 177.8 \Omega$.

(b) Adding a 100- Ω load to the original circuit or our Thévenin equivalent, the voltage across the load is

$$V_{100\Omega} = V_{TH} \left(\frac{100}{100 + 177.8} \right) = 14.00 \text{ V}, \text{ and so } P_{100\Omega} = (V_{100\Omega})^2 / 100 = 1.96 \text{ W}.$$

