

IV. (40 pts): A voltage amplifier (A-amplifier) has an open-circuit voltage gain $A_{v,0}$ of 100V/V, an input resistance R_i of 250 k Ω and an output resistance R_o of 1 k Ω . It is connected in a negative feedback loop with a series-shunt topology.


When port 1 of the feedback network is open-circuited, the feedback network (looking from side 2) has an input resistance of 2 k Ω .

When port 2 is short-circuited, the feedback network (looking from side 1) has an input resistance of 5 k Ω .

The feedback factor is 0.1V/V.

The amplifier is fed with a ~~current~~ ^{voltage} source with a resistance R_s of 5 k Ω and is feeding a load resistance R_L of 2 k Ω .

- Which small parameters should you use to model the feedback network?
- Draw the full circuit diagram including source resistance, voltage amplifier, its feedback network, and the load resistance.
- Draw the A' amplifier and calculate its gain. Specify the units.
- Calculate the input resistance R_i' and output resistance R_o' of the A' -amplifier.
- Finally, calculate the input resistance R_{if} and output resistance R_{of} of the amplifier with feedback.

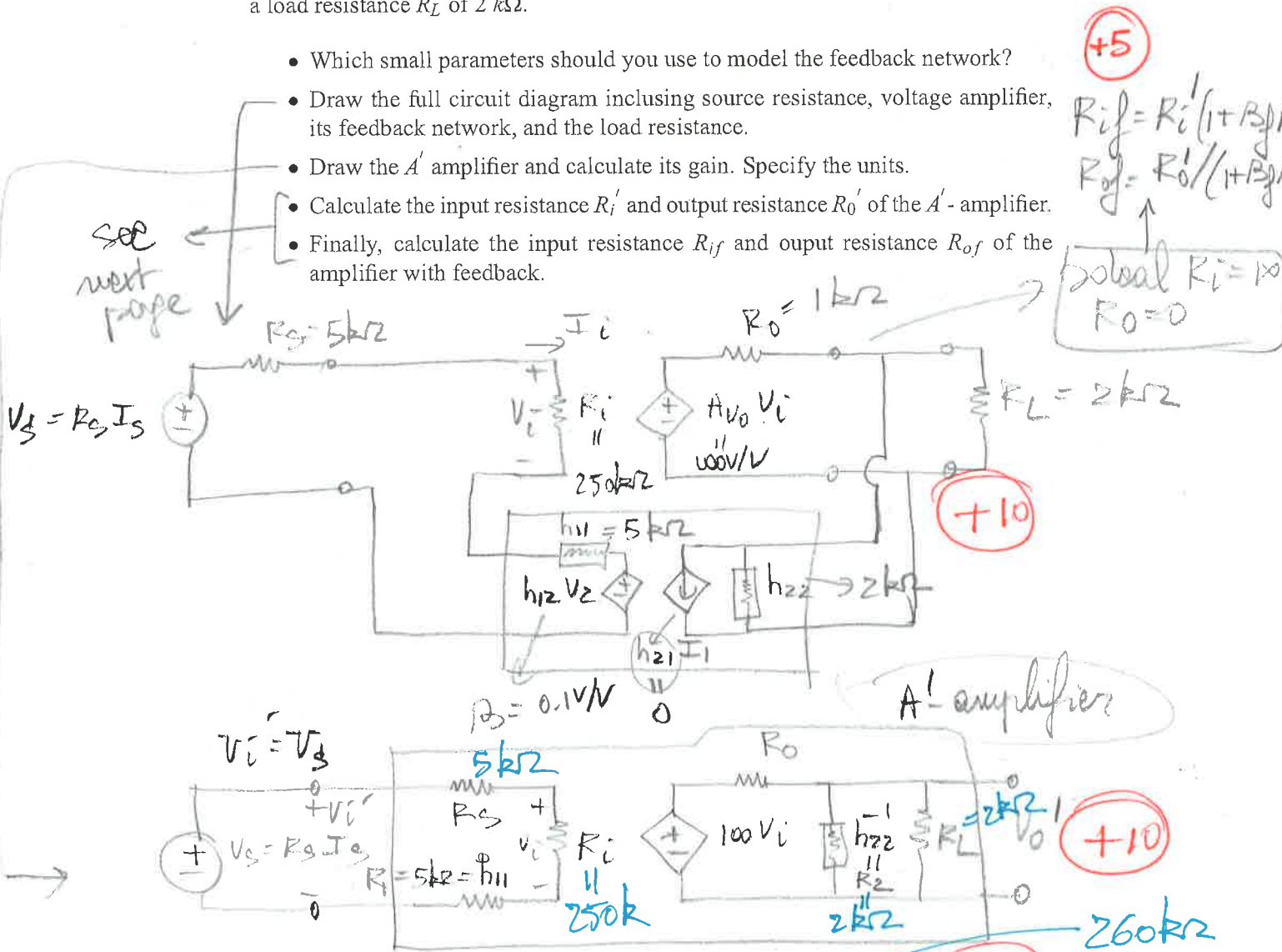

+5

$$R_{if} = R_i' (1 + \beta A')$$

$$R_{of} = R_o' / (1 + \beta A')$$

total $R_i = 10$
 $R_o = 0$

+10

A' amplifier

+10

$$R_i' = R_s + R_i + h_{11} = R_s + R_i + R_1 = \text{+2.5}$$

$$R_o' (V_s=0) = [R_L // h_{22}^{-1} // R_L] = [R_L // R_2 // R_L] = \text{+2.5}$$

$$= 500 \Omega$$

$$V_i = \frac{R_i}{R_i + R_s + R_1} V_i'$$

$$V_o' = A_{vo} V_i \frac{(R_L \parallel R_2)}{[(R_L \parallel R_2) + R_o]}$$

$$A' = \frac{V_o'}{V_i} = A_{vo} \frac{(R_L \parallel R_2)}{[(R_L \parallel R_2) + R_o]} \cdot \left[\frac{R_i}{R_i + R_s + R_1} \right] \quad (+5)$$

$$A' = 100 \frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot \left(\frac{250}{260} \right) = 48$$

$$1 + \beta_f A' = 1 + 0.1(48) = 5.8$$

$$R_{if} = R_i' (1 + \beta_f A') \quad (2.5) = 260(5.8) = \boxed{1.51k\Omega}$$


$$R_{of} = R_o' / (1 + \beta_f A') \quad (2.5) = \frac{500\Omega}{5.8} = \boxed{86\Omega}$$

Team
members:

ECE352
SPRING 2011
Team Project 3

Due Monday
May 9, 2011

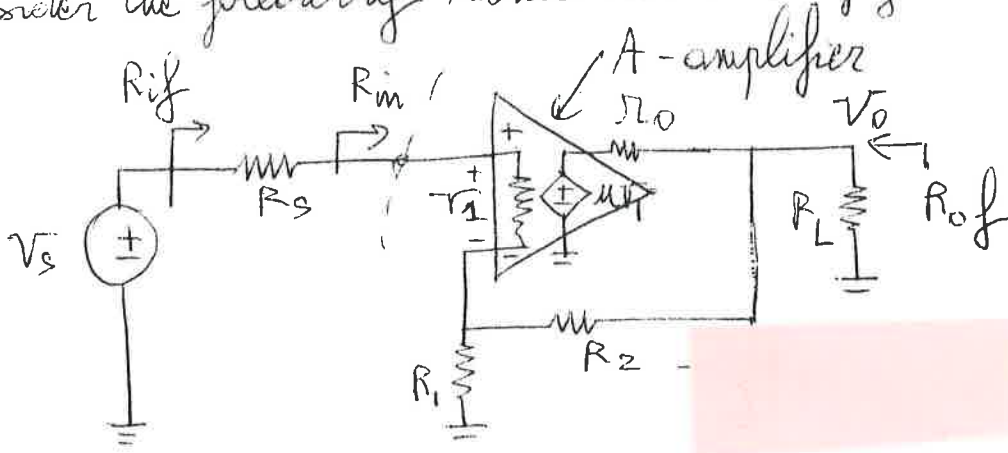Consider the following series-shunt configuration



- Circle the feedback network
- Calculate the h-parameters for the feedback network
- Show how to build the A' -amplifier
- Calculate the gain of the A' -amplifier
- Calculate the gain $A_f = \frac{v_o}{v_s}$
- Determine the input and output resistances of the A' -amplifier
- Calculate the input (R_{if}) and output (R_{of}) resistances of the amplifier with feedback.

Use the following values in the calculations above

$$R_{id} = 100 \text{ k}\Omega$$

$$\mu = 10^4$$

$$r_o = 1 \text{ k}\Omega$$

$$R_L = 2 \text{ k}\Omega$$


$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1 \text{ M}\Omega$$


$$R_s = 10 \text{ k}\Omega$$

Find A' gain of A' circuit Series-Shunt Extra example


①

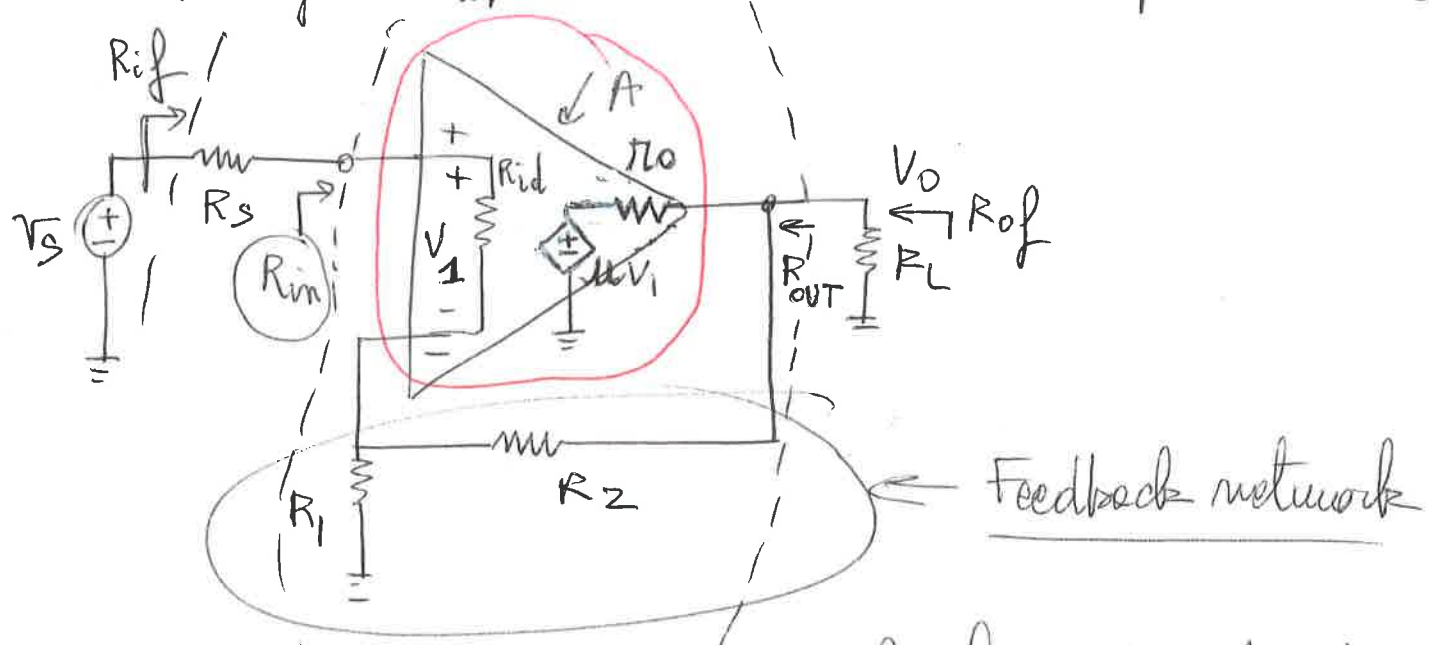

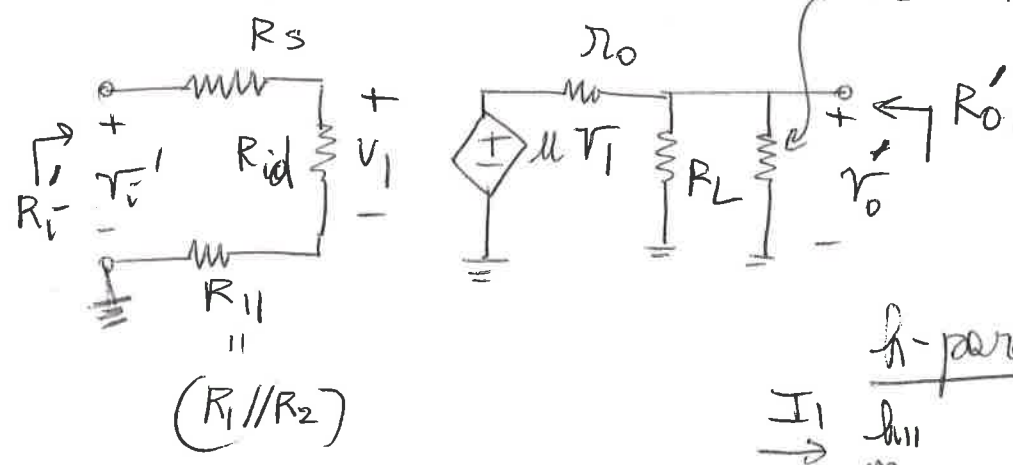A' circuit using h-parameters for feedback network. $R_{22} = R_1 + R_2$



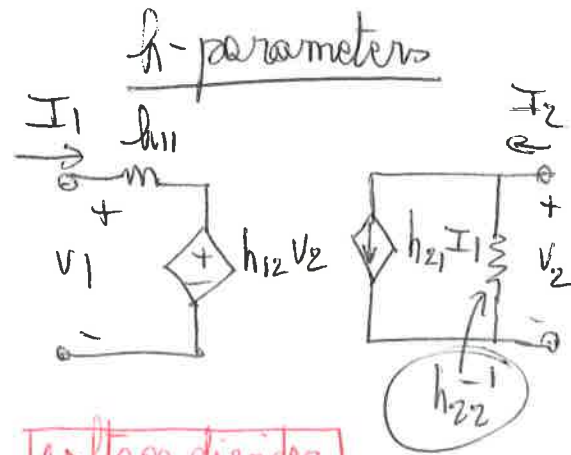
$R_{11} = h_{11}$ & $R_{22} = h_{22}^{-1} = R_1 + R_2$
from h-parameters analysis.



Voltage divider

$$B_f = \frac{V_f'}{V_o'} = \frac{R_1}{R_1 + R_2}$$

B_f?

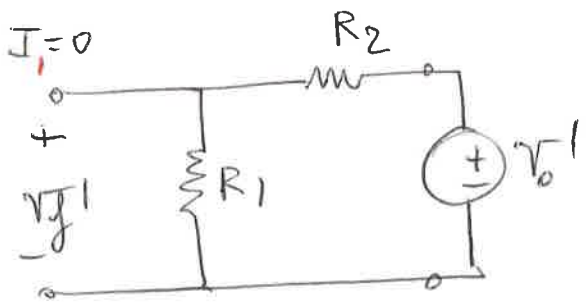

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

A' = Gain of A' circuit is $\frac{V_o'}{V_i'}$

$$A' = \mu \frac{(R_L // R_{22})}{(R_L // R_{22}) + r_o} \cdot \frac{R_{id}}{[R_{id} + R_s + R_{11}]}$$

$\mu = 10^4$
 $r_o = 1 \text{ k}\Omega$
 $R_L = 2 \text{ k}\Omega$
 $R_1 = 1 \text{ k}\Omega$
 $R_2 = 1 \text{ M}\Omega, R_s = 10 \text{ k}\Omega$

$\rightarrow A' \approx 6000 \text{ V/V}$

$$\beta_{of} = \frac{R_1}{R_1 + R_2} \approx 10^{-3} \text{ V/V}$$

voltage gain with feedback is given by

$$A_f = \frac{V_o}{V_s} = \frac{A'}{1 + A'\beta_{of}} = \frac{6000}{7} = 857 \text{ V/V}$$

output resistance with feedback

$$R_{if} = R_i (1 + A'\beta_{of})$$

where R_i is the input resistance of A' circuit.

From previous page, we get

$$R_i = R_s + R_{id} + R_{11} = R_s + R_{id} + (R_1 // R_2) \approx 111 \text{ k}\Omega$$

$$\rightarrow \boxed{R_{if} \approx 777 \text{ k}\Omega}$$

But $R_{in} + R_S = R_{if}$

$$\rightarrow R_{in} = R_{if} - R_S = \underline{739 \Omega}$$

$R_{of} = \frac{R_o'}{1 + A\beta_f}$ where R_{out} is output resistance of A' circuit

$$R_o' = r_o \parallel R_L \parallel (R_1 + R_2) \approx 667 \Omega$$

$$\rightarrow R_{of} = \frac{R_o'}{1 + \beta_f} = \frac{667}{7} \approx 95.3 \Omega$$

But

$$R_{of} = (R_L \parallel R_{out})$$

$$\rightarrow R_{out} \approx 100 \Omega$$

see how it is defined on diagram.