

Test 1 - Fall 2008 (100pts max) - M. Cahay

Name: *Omsaye Akomolede*


100/100

*M. Cahay*

### NETWORK ANALYSIS I

October 14, 2008

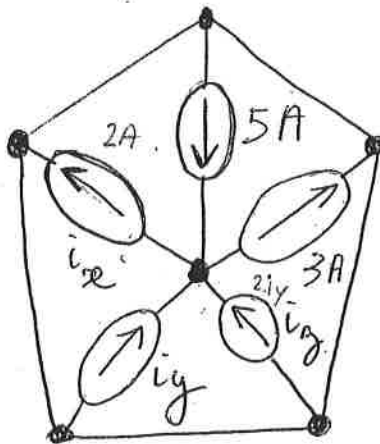I. (20 pts) In the circuit below, find  $i_y$  if  $i_x = 2A$  and  $i_z = 2i_y$ .



$$i_y + 2i_y + 5A = 3A + 2A$$

$$3i_y + 5A = 3A + 2A$$


$$3i_y = 0A$$

$$i_y = 0A$$


20

$$i_y + 2i_y + 5A - 2A - 3A = 0$$

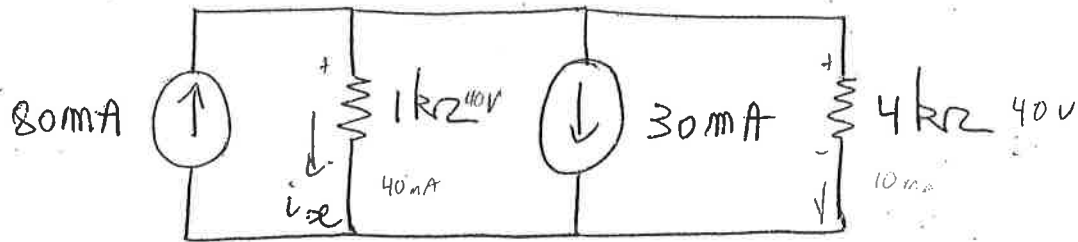II. (20 pts) In the circuit below, find the power absorbed by the  $4\text{ k}\Omega$  resistor.


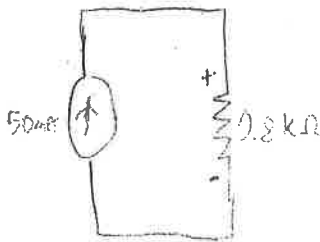
$$1\text{ k}\Omega \parallel 4\text{ k}\Omega = \frac{1 \times 4\text{ k}\Omega}{1 + 4} = \frac{4}{5}\text{ k}\Omega = 0.8\text{ k}\Omega$$




$$V_{R_{eq}} = I R_{eq} = 50 \times 10^{-3}\text{ A} \cdot 0.8 \times 10^3\ \Omega = 40\text{ V}$$

$$P = \frac{(40)^2}{4\text{ k}\Omega} = 0.4\text{ W}$$

20

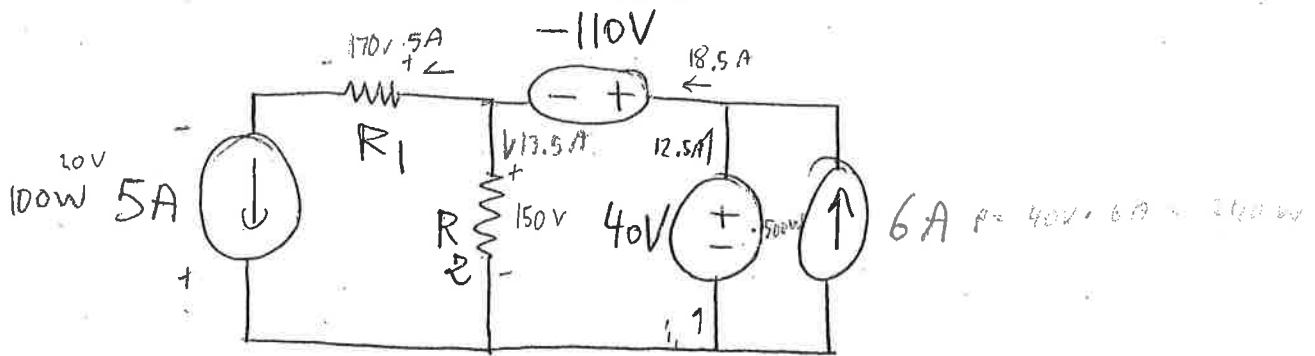III. (30 pts) Find the values of the resistors  $R_1$  and  $R_2$  in the circuit below if the 5A current source is supplying 100 W and the 40 V source is supplying 500 W.



$$V_{R_1} = 150V - 20V = 130V$$

$$V_{R_1} = 170V \quad 170V / 5A = 34 \Omega$$

$$R_1 = \frac{V_{R_1}}{I} = \frac{170V}{5A} = 34 \Omega$$

$$R_2 = \frac{150V}{13.5A} = 11.11 \Omega$$

$$P_{R_2} = 13.5^2 \cdot 11.11 \Omega = 2035 W$$

$$P = iV$$

$$500W = i_1 \cdot 40V$$

$$i_1 = 12.5A$$

$$V_{R_2} = 40V + 110V = 150V$$

$$V_{R_2} = 150V$$

$$R_2 = \frac{V_{R_2}}{I} = \frac{150V}{13.5A} = 11.11 \Omega$$

$$P = iV$$

$$P = 18.5A \cdot (-110V) = -2035 W$$

$$R = \frac{170}{5A} = 34 \Omega$$

$$P_{R_1} = 850 W$$


$$\begin{array}{r} 850 W \\ + 2035 W \\ + -500 W \\ + -100 W \\ + -2035 W \\ + -240 W \\ \hline 0 W \end{array}$$

$$R_1 = 34 \Omega$$

$$R_2 = 11.11 \Omega$$

30

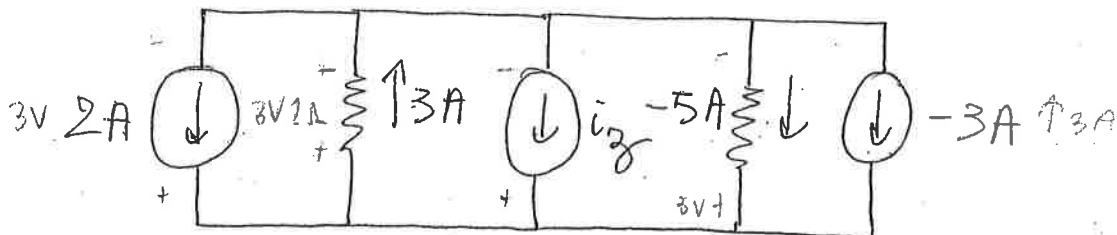IV. (30 pts) If the resistor carrying 3 A has a value of  $1 \Omega$ , what is the value of the resistor carrying -5 A?



$$i_2 + 2A + (-3A) + (-5A) + (-3A) = 0$$

$$i_2 = 9A$$

$$1 \Omega \cdot 3A = 3V$$

$$R = \frac{-3V}{-5A} = 0.6 \Omega$$

20


$$\begin{array}{r}
 -6W \\
 + 0W \\
 - 27W \\
 + 15W \\
 \hline
 0W
 \end{array}$$

Test 1 - Fall 2007 (100pts max) - M. Cahay  
Name:


NETWORK ANALYSIS I  
October 11, 2007

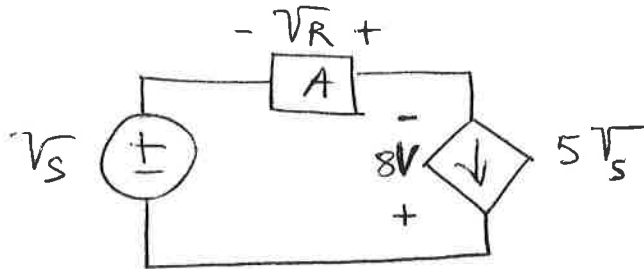I. (20 pts) In the circuit below, assume  $V_s = 1\text{ V}$  and  $V_R = 9\text{ V}$  and compute:


- The power absorbed by element A.
- The power supplied by each of the two sources (the voltage source on the left and the current source on the right).
- Check that the total power supplied is equal to the total power absorbed.



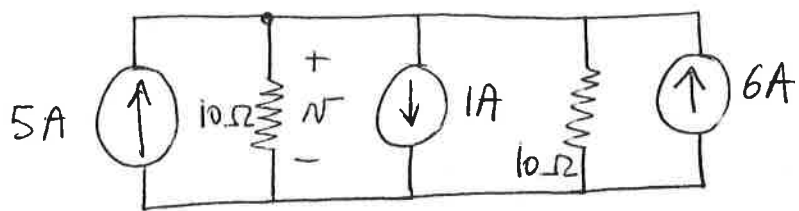II. (20 pts) Determine the voltage  $v$  in the circuit below.



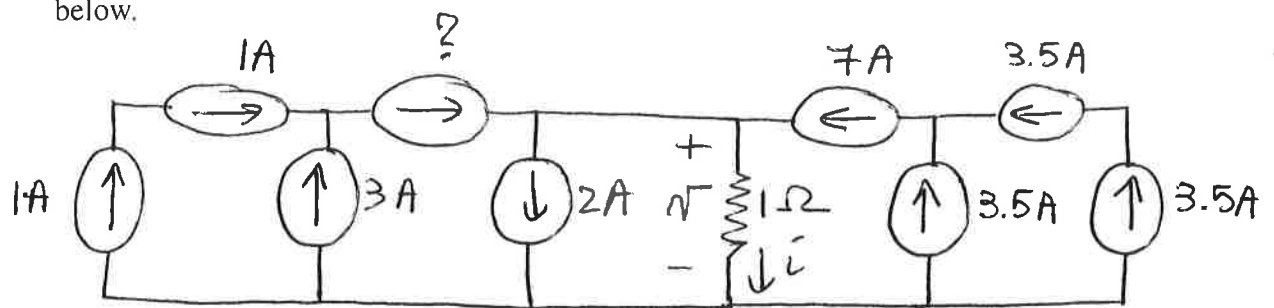III. (30 pts) Using combination of sources, compute the current  $i$  in the circuit below.



IV. (30 pts) Use the supernode technique and compute the current  $i_1$  in the circuit below.

