

NETWORK ANALYSIS II  
April 19, 2011

I. (15 pts) Using the table of trigonometric identities below, compare the two waveforms  $v_1$  and  $v_2$  and determine which one is leading the other. Determine by what angle.

$$\begin{aligned} -\sin \omega t &= \sin(\omega t \pm 180^\circ) \\ -\cos \omega t &= \cos(\omega t \pm 180^\circ) \\ \mp \sin \omega t &= \cos(\omega t \pm 90^\circ) \\ \pm \cos \omega t &= \sin(\omega t \pm 90^\circ) \end{aligned}$$

- $v_1 = -33 \sin(8t - 9^\circ) = -33 \cos(8t - 9^\circ - 90^\circ)$
- and,  $v_2 = 12 \cos(8t - 1^\circ)$

$$V_2 = 12 \angle -1^\circ$$

$$\begin{aligned} v_1 &= -33 \cos(8t - 99^\circ) \\ &= 33 \cos(8t - 99^\circ + 180^\circ) = 33 \cos(8t + 81^\circ) \end{aligned}$$

$$V_1 = 33 \angle 81^\circ$$

$\Rightarrow v_1$  leads  $v_2$  by  $82^\circ$

II. (15 pts) Express the following complex number in both rectangular and polar forms.


$$\mathbf{z} = (8 - j15)(4 + j16) - j$$

$$z = (8 - j15)(4 + j16) - j$$

$$= 32 + j128 - j60 + 240 - j$$

$$= 272 + j67 = 280.1 \angle 13.84^\circ$$

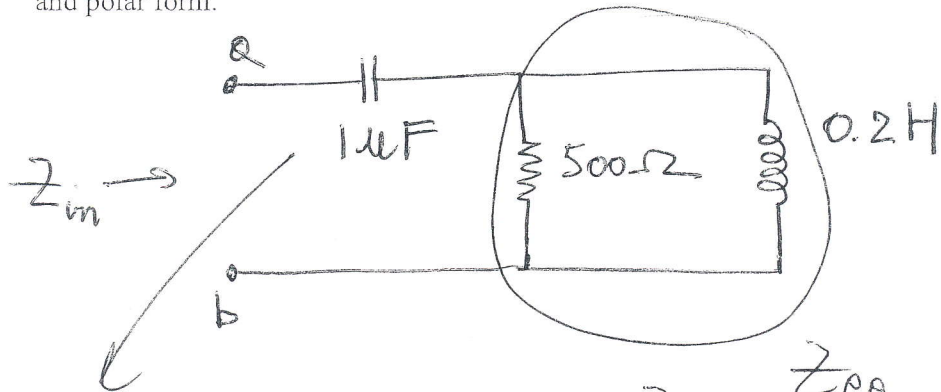III. (20 pts) Consider the combination of impedances in the circuit below and determine the impedance  $Z_{in}$  seen between points a and b, if the circuit operates at the angular frequency  $\omega = 10^3$  rad/s. Express the impedance  $Z_{in}$  both in rectangular and polar form.



$$Z_C = \frac{1}{j 10^3 \cdot 10^{-6}} = -j 10^3 \quad Z_{eq}$$

$$Z_L = j 10^3 (0.2) = 200j$$

$$Z_{eq} = \frac{Z_L R}{R + Z_L} = \frac{500 (200j)}{500 + 200j} = \frac{1000j}{5 + 2j}$$

$$Z_{eq} = \frac{1000j (5 - 2j)}{25 + 4} = \frac{2000 + 5000j}{29}$$

$$\rightarrow Z_{in} = -1000j + \frac{2000 + 5000j}{29}$$

$$Z_{in} = \frac{2000}{29} + \left( \frac{5000}{29} - 1000 \right) j = 69 + j 828$$


$$Z_{in} = \sqrt{69^2 + (828)^2} \tan^{-1} \left( -\frac{828}{69} \right)$$

$$= 831 \angle -85.24^\circ$$

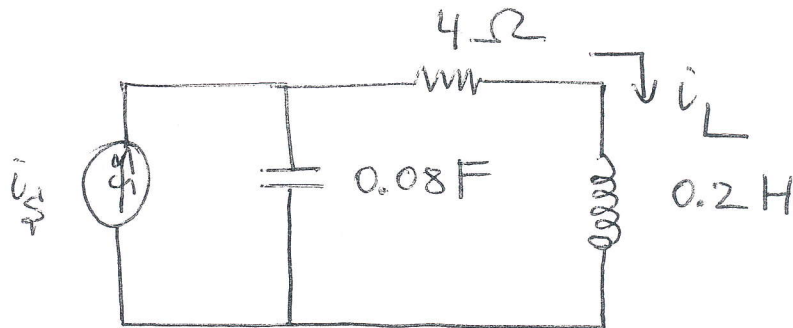IV. (25 pts) We look at the steady state response of the circuit below. If the current  $i_L$  is given by the phasor

$$i_L = 20e^{j(10t+25^\circ)} \quad (1)$$

Express the source current  $i_s(t)$  as a function of time.



$$v_L = L \frac{di_L}{dt} = 0.2 \frac{d}{dt} [20 e^{j(10t+25^\circ)}]$$

$$v_L = j40 e^{j(\omega t + 25^\circ)}$$

$$v_R = 80 e^{j(\omega t + 25^\circ)}$$

$$v_s = (80 + j40) e^{j(\omega t + 25^\circ)}$$

$$i_C = 0.08(80 + j40) j10 e^{j(\omega t + 25^\circ)} = (-32 + j64) e^{j(\omega t + 25^\circ)}$$

$$\rightarrow i_s = (-12 + j64) e^{j(\omega t + 25^\circ)}$$

$$i_s = 65.12 e^{j(10t + 125.62^\circ)} \text{ A}$$


V. (25 pts) Use mesh analysis to write the two equations satisfied by the circulating phasor currents  $I_1$  and  $I_2$  in the circuit below if

$$v_1 = 20\cos(1000t)V$$

and

$$v_2 = 20\sin(1000t)V$$

DO NOT SOLVE THESE EQUATIONS.

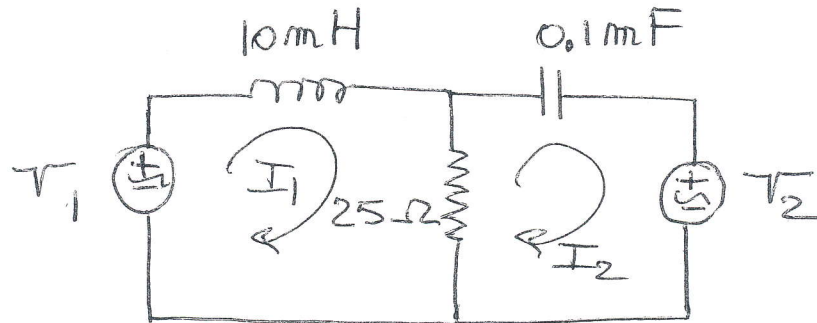

$$V_1 = 20\angle 0^\circ \quad V_2 = 20 \cos(1000t - 90^\circ)$$

$$\rightarrow V_2 = -j20 \text{ or } 20\angle -90^\circ$$

$$0.01H \rightarrow j10\Omega$$

$$0.1mF \rightarrow -j10\Omega$$

$$\begin{cases} -20\angle 0^\circ + j10I_1 + 25(I_1 - I_2) = 0 \\ 25(I_2 - I_1) - j10I_2 + V_2 = 0 \end{cases}$$

$$\boxed{\begin{aligned} (25 + j10)I_1 - 25I_2 &= 20\angle 0^\circ \\ -25I_1 + (25 - j10)I_2 &= 20\angle 90^\circ \end{aligned}}$$