


Test 1 - Winter 1995 - M. Cahay

Name: KEY

ELECTRONICS I

January 23, 1995

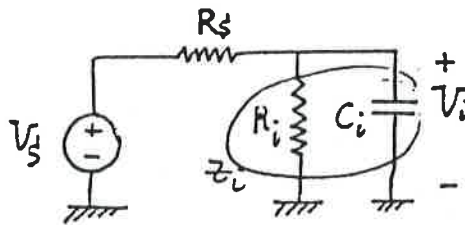I. The figure below shows a voltage source connected to the input of an amplifier. R_s is the source resistance. R_i and C_i are the input resistance and input capacitance of the amplifier, respectively. Derive an expression for $V_i(s)/V_s(s)$ and show that it is a low-pass STC type. Find the 3-dB frequency for the case where $R_s = 5k\Omega$, $R_i = 200k\Omega$, and $C_i = 20pF$. (25 pts).



5pts $\frac{V_i}{V_s} = \frac{z_i}{R_s + z_i}$

$z_i?$ $Y_i = \frac{1}{R_i} + \Delta C_i = \frac{1 + \Delta R_i C_i}{R_i}$

$z_i = \frac{1}{Y_i} = \frac{R_i}{1 + \Delta R_i C_i}$

$\frac{V_i}{V_s} = \frac{R_i}{1 + \Delta R_i C_i} \cdot \frac{1}{R_s + \frac{R_i}{1 + \Delta R_i C_i}}$ 5pts

$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i + \Delta R_i R_s C_i} = \frac{R_i / R_s + R_i}{1 + \frac{\Delta R_i R_s C_i}{R_s + R_i}} = \frac{K}{1 + \frac{\Delta}{\omega_b}}$

$\omega_b = \frac{R_s + R_i}{R_i R_s C_i} = \frac{1}{(R_i // R_s) C_i}$ 10pts


$R_s = 5k\Omega$
 $R_i = 200k\Omega$
 $C_i = 20pF$

$\omega_b = \frac{205k\Omega}{200k\Omega \cdot 5k\Omega \cdot 20pF} = \frac{205}{20,000 \cdot 10^3 \cdot 10^{-12}}$

$f_b = \frac{205}{20,000} \cdot 10^9 \cdot \frac{1}{2\pi} = 1.63 \cdot 10^6 \text{ Hz}$

$f_b = 1.63 \text{ MHz}$ 5pts

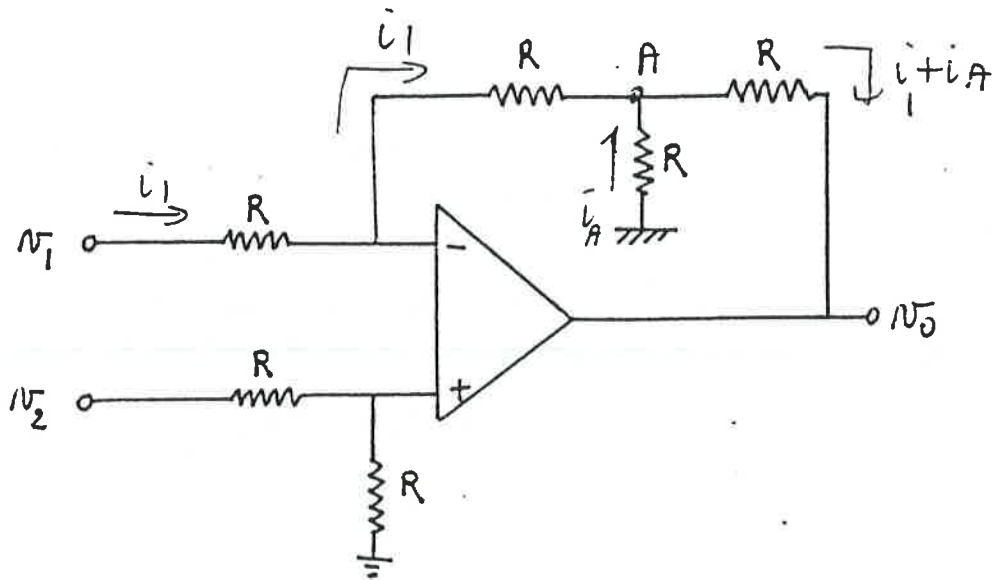II. In the diagram below the op-amp is assumed to be ideal and all resistors are assumed to be equal to 1Ω for simplicity. Find an expression of v_o in terms of v_1 and v_2 . Hint: Use the principle of superposition. (30pts)



$A = \infty$

(I) Solution

$v_+ = \frac{v_2}{2}$

$v_- = v_+ = \frac{v_2}{2}$

$i_1 = \frac{v_1 - \frac{v_2}{2}}{1} = v_1 - \frac{v_2}{2}$

at A $v_A = v_- - R i_1 = \frac{v_2}{2} - v_1 + \frac{v_2}{2} = v_2 - v_1$

$i_A = \frac{-v_A}{R} = i_A = v_1 - v_2$

$\rightarrow v_o = v_A - R [i_A + i_1] = v_2 - v_1 - [v_1 - v_2 + v_1 - \frac{v_2}{2}]$

$v_o = v_2 - v_1 - [2v_1 - \frac{3}{2}v_2] = \frac{5}{2}v_2 - 3v_1$

(II) Principle of Superposition (solution)

$v_2 = 0$

$\rightarrow v_+ = v_- = 0 \rightarrow i_1 = v_1 \rightarrow v_A = -v_1$

$\rightarrow i_A = v_1$

$\rightarrow v_{o1} = -v_1 - 2v_1 = -3v_1$

$v_1 = 0$


$\rightarrow v_+ = v_- = \frac{v_2}{2} \Rightarrow i_1 = -\frac{v_2}{2}$

$\Rightarrow v_A = \frac{v_2}{2} + \frac{v_2}{2} = v_2$


$\rightarrow i_A = -\frac{v_2}{2}$

$\rightarrow v_{o2} = v_A - R(i_1 + i_A) = v_2 - (-\frac{3v_2}{2}) = \frac{5}{2}v_2$

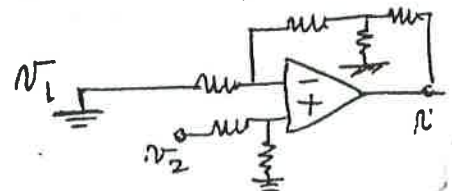$\rightarrow v_o = v_{o1} + v_{o2} = \frac{5}{2}v_2 - 3v_1$



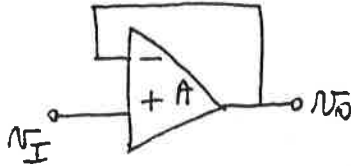IV. Consider a voltage follower (buffer amplifier) built with an ideal op-amp except for having a finite voltage gain A . Calculate the value of the close-loop gain for $A=10, 100$, and 1000 . In each case calculate the % error in gain magnitude compared to the gain obtained with an ideal op-amp. (15pts).



$$\left. \begin{aligned} V_O &= A(V_I - V_-) \\ V_- &= V_O \end{aligned} \right\} \rightarrow \frac{V_O}{A} = V_I - V_O$$

or

$$V_O \left[1 + \frac{1}{A} \right] = V_I$$


Close-loop
Gain

$$\rightarrow G = \frac{V_O}{V_I} = \frac{1}{1 + \frac{1}{A}}$$

A	$G(A=\infty)$	G	% error
10	1	0.909	9.1%
100	1	0.990	1%
1000	1	0.999	0.1%

$$\% \text{ error} = \left| \frac{G - G(A=\infty)}{G(A=\infty)} \right| = \left| \frac{\frac{1}{1 + \frac{1}{A}} - 1}{1} \right| = \frac{1}{A} \frac{A}{A+1} = \frac{1}{1+A}$$

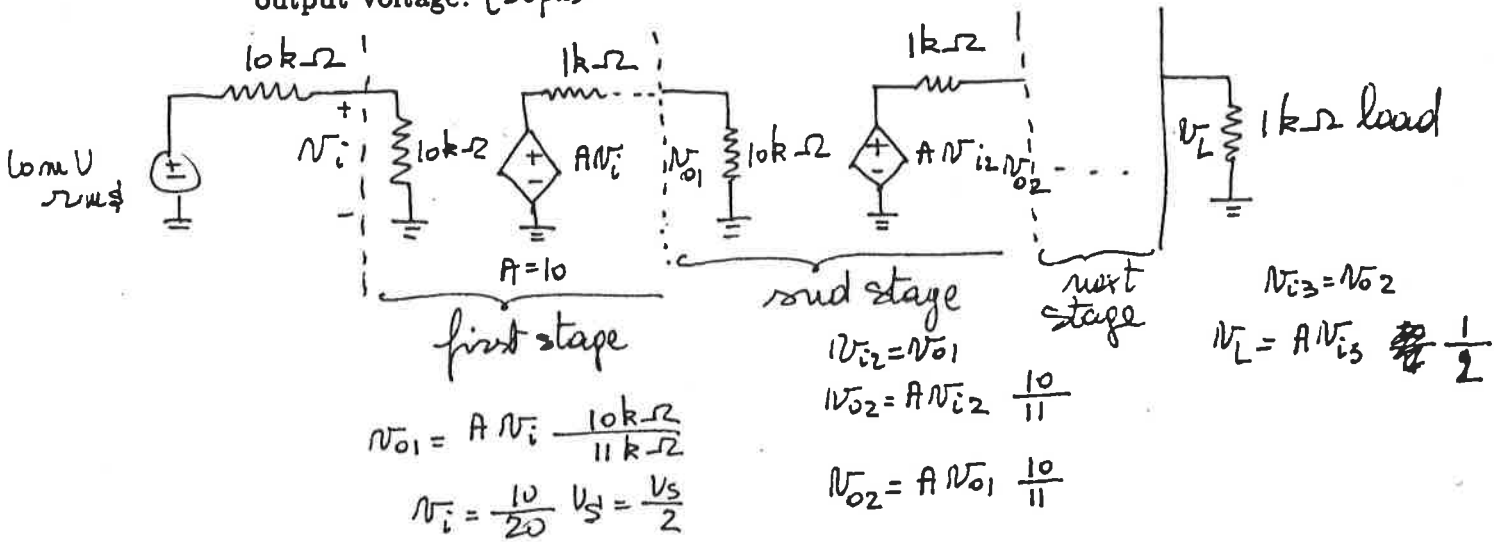III. A designer has available voltage amplifiers having an input resistance of $10k\Omega$, an output resistance of $1k\Omega$, and an open-circuit voltage gain of 10. The signal source has a $10k\Omega$ resistance and provides 10 mV rms signal. If it is required to provide a signal of at least 2 V rms to a $1k\Omega$ load, how many amplifier stages are required? For this number of amplifiers, what is the actual output voltage? (30pts)



$$V_L = \frac{A}{2} V_{i3} = \frac{A}{2} V_{o2} = \frac{A^2}{2} V_{o1} \cdot \frac{10}{11} = \frac{A^3}{2} V_i \left(\frac{10}{11}\right)^2$$

$$V_L = \frac{A^3}{2} \left(\frac{10}{11}\right)^2 \frac{V_s}{2}$$

$$V_L = \frac{1}{2} A^m \left(\frac{10}{11}\right)^{m-1} \frac{V_s}{2} \quad \text{where } m = \# \text{ of stages}$$

we want $\frac{V_L}{V_s} = \frac{2}{10m} = 200 = \frac{1}{2} A^m \left(\frac{10}{11}\right)^{m-1} = \frac{1}{2} \frac{10^m 10^{m-1}}{11^{m-1}} = \frac{11}{20} \frac{10^{2m}}{11^m}$

$$\frac{V_L}{V_s} = 200 = \frac{11}{20} \left(\frac{100}{11}\right)^m \Rightarrow \boxed{\text{solve for minimum } m \text{ needed}}$$

$$\left(\frac{100}{11}\right)^m = \frac{4000}{11} = 363.6$$

$$\Rightarrow \left. \begin{array}{l} \text{for } m=3, \left(\frac{100}{11}\right)^3 = 751 \\ \text{for } m=2, \left(\frac{100}{11}\right)^2 = 83 \end{array} \right\} \rightarrow 3 \text{ stages needed}$$

Test 1 - Fall 1997 (100pts max) - M. Cahay

Name:


ELECTRONICS I

October 14, 1997


I. (25 pts) A voltage amplifier has the transfer function

$$A_v = \frac{100}{(1 + \frac{jf}{10^4})(1 + \frac{10^2}{jf})} \quad (1)$$

Using the Bode plots for low-pass and high-pass filters, sketch the Bode plot for $|A_v|$. Give approximate values for the gain amplitude at $f = 10, 10^2, 10^3, 10^4, 10^5, 10^6,$ and 10^7 Hz. Find the bandwidth of the amplifier (defined as the frequency range over which the gain remains within 3 dB of the maximum value).

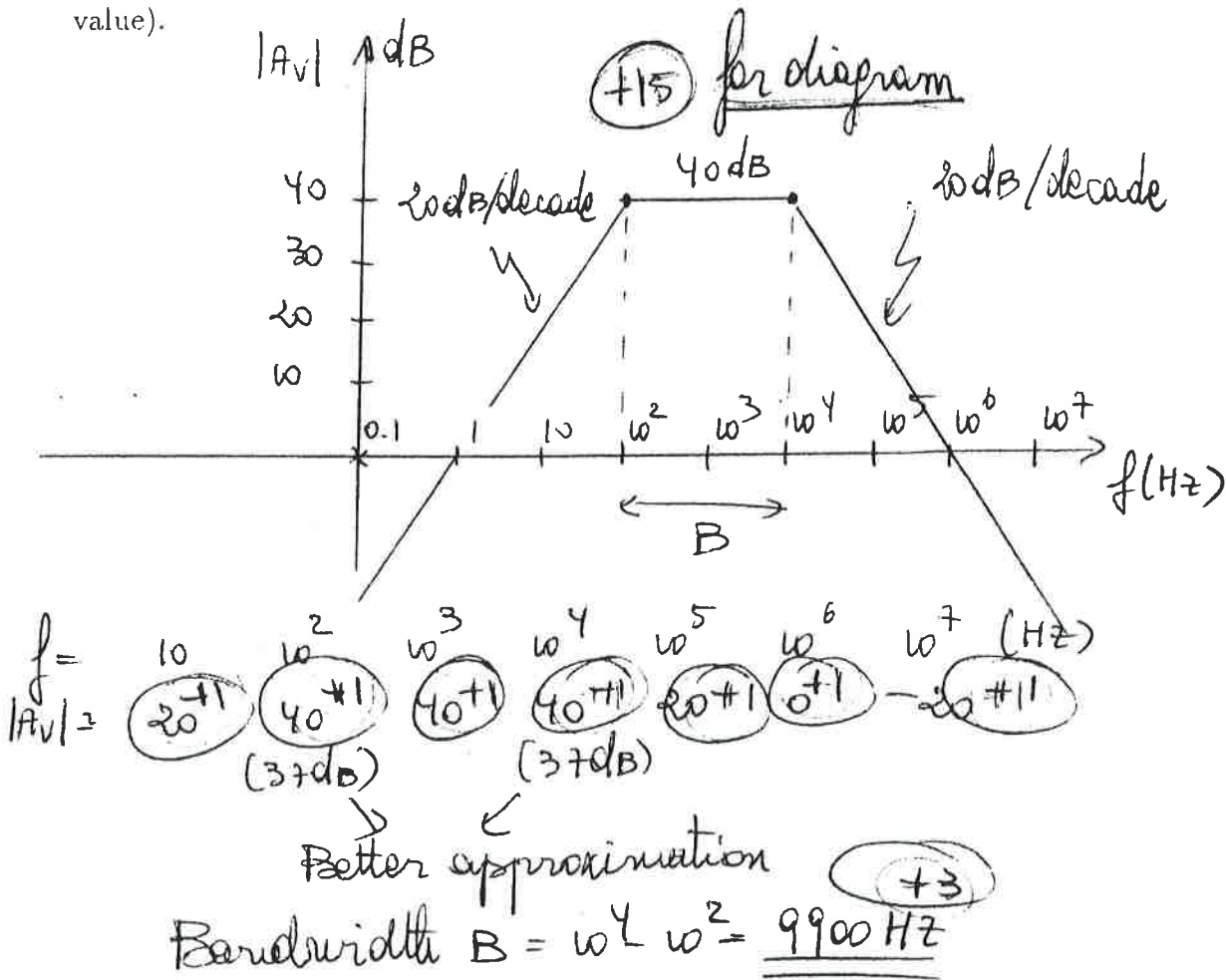

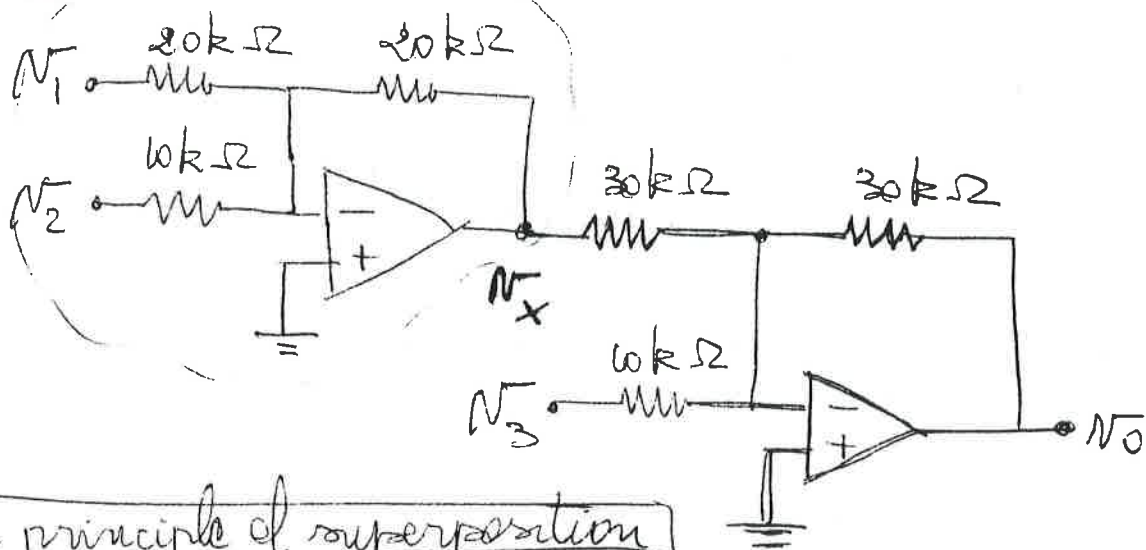Calculate v_0 in terms of v_1, v_2, v_3 for the circuit below. Assume ideal op-amps.




Use principle of superposition

$$v_x = -v_1 - 2v_2$$

$$v_0 = -(-v_1 - 2v_2) - 3v_3$$

$$v_0 = v_1 + 2v_2 - 3v_3$$

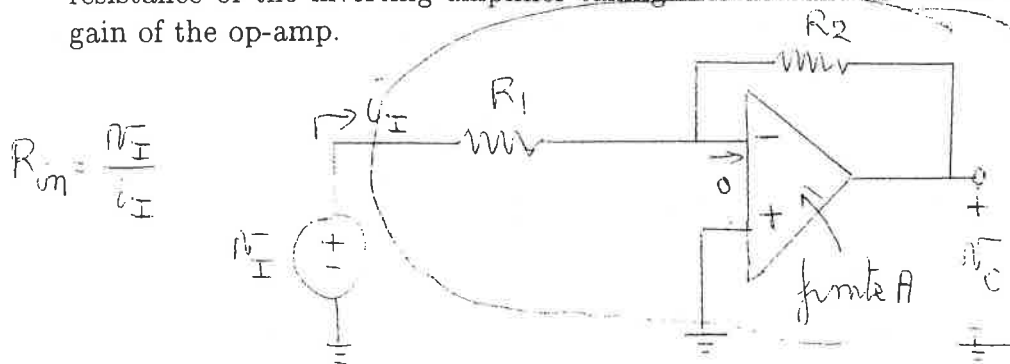IV. (25 pts) For the circuit shown below, derive an expression for the input resistance of the inverting amplifier taking into account the finite open-loop gain of the op-amp.



$$R_{in} = \frac{v_I}{i_I}$$

$$v_O = A(v_+ - v_-); \quad v_+ = 0$$

$$\Rightarrow v_O = -A v_-$$

$$= v_- - i_I R_2$$


$$\Rightarrow i_I R_2 = (A+1)v_-$$

$$\Rightarrow r_- = i_I R_2 / (1+A)$$

$$\begin{aligned} \text{Now } v_I &= i_I R_1 + v_- \\ &= i_I R_1 + \frac{i_I R_2}{A+1} \end{aligned}$$

$$\Rightarrow R_{in} = \frac{v_I}{i_I} = R_1 + \frac{R_2}{A+1}$$

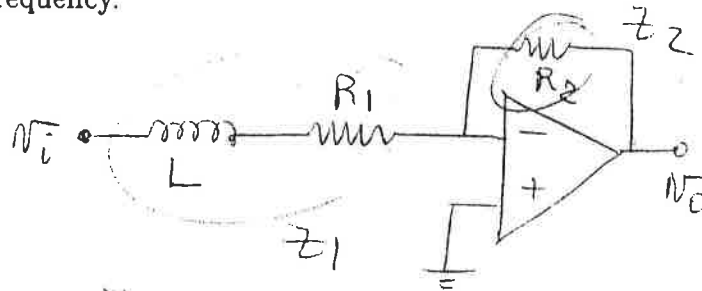IV. (25 pts) For the circuit below, calculate the transfer function $T(s) = v_o(s)/v_i(s)$. Is it of the low-pass or high-pass type? Give an expression for the 3 dB frequency.



$$\frac{v_o}{v_i} = \frac{R_2}{R_1 + j\omega L} = \frac{-R_2/R_1}{1 + j\omega \frac{L}{R_1}} = \frac{-R_2/R_1}{1 + \frac{j\omega L}{R_1}}$$

$$\Rightarrow K = -R_2/R_1$$

$$\omega_{3dB} = R_1/L$$

Low-pass filter

III. (25 pts) For the circuit shown below, find v_o in terms of v_1 and v_2 assuming an ideal op-amp. For


$$v_1 = 10\sin(2\pi \times 60t) - 0.1\sin(2\pi \times 1000t), \text{ volts} \quad (2)$$

and

$$v_2 = 10\sin(2\pi \times 60t) + 0.1\sin(2\pi \times 1000t), \text{ volts} \quad (3)$$

Find v_o .


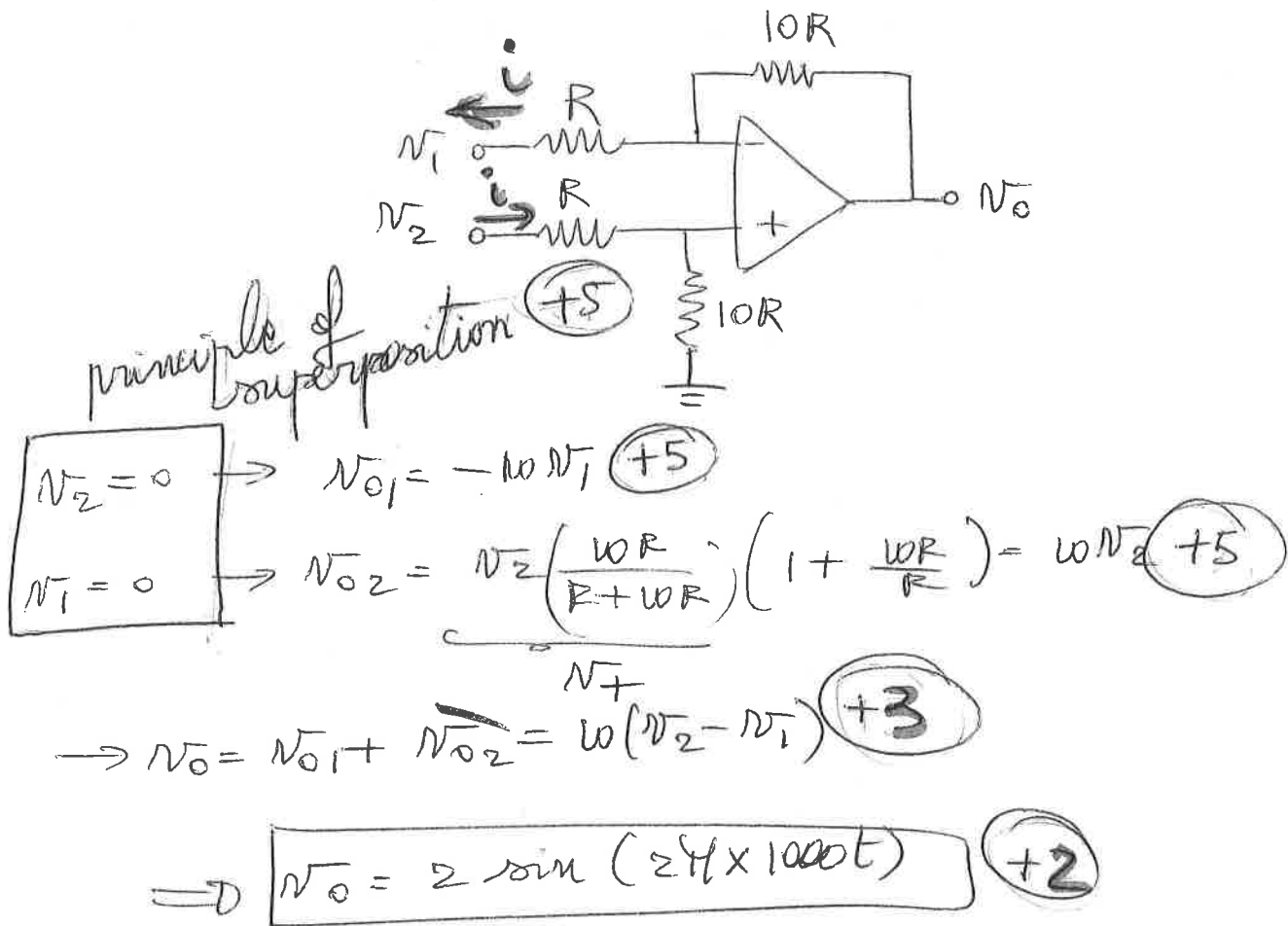
Find the input resistance seen by the differential input signal $v_2 - v_1$.



$$R_{in} = \frac{v_2 - v_1}{i} = 2R \quad (+5)$$



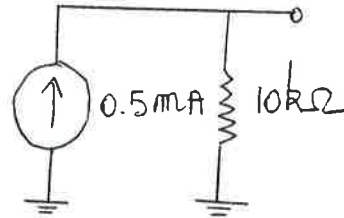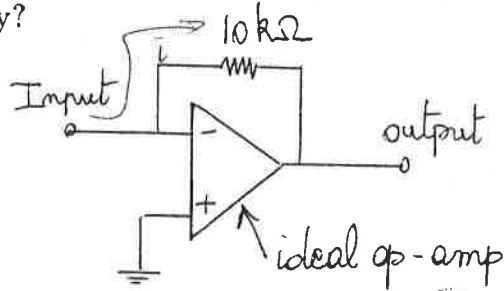II. (25 pts) The circuit shown below (left) can be used to implement a transresistance amplifier. Find the value of the input resistance R_i , the transresistance R_m , and output resistance of the transresistance amplifier R_o . If the signal source shown on the right below is connected to the input of the transresistance amplifier, find its output voltage. Does it depend on the load resistance? Why?




$$R_i = \frac{v_i}{i_i} = 0 \quad (+4)$$

$$R_o = 0 \quad (+4)$$

$$v_o = -10 \text{ k}\Omega i_i \Rightarrow R_m = -10 \text{ k}\Omega \quad (+4)$$

$$R_o = 0$$

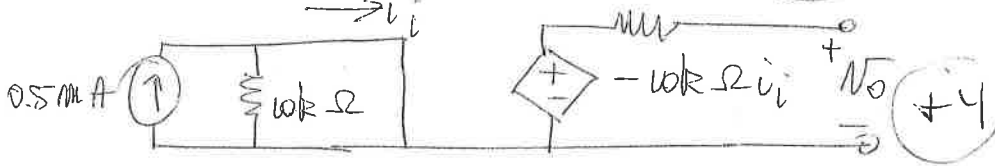


$$i_i = 0.5 \text{ mA}$$

$$\Rightarrow v_o = -10 \text{ k}\Omega \times 0.5 \text{ mA} = -5 \text{ V} \quad (+3)$$

v_o does not depend on R_L because $R_o = 0$. (+2)

EE 351 (Electronics I - Spring 1993 - Final), NAME:

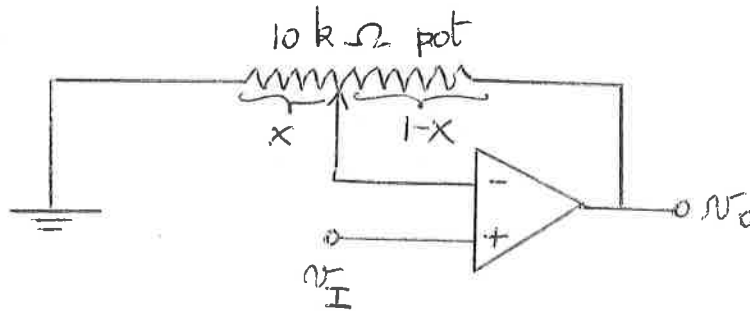- Problem 1: The circuit shown below utilizes a 10 kilohms potentiometer to realize an adjustable-gain amplifier. Derive an expression for the gain as a function of the potentiometer setting x . Assume the op amp to be ideal. What is the range of gains obtained? Show how to add a fixed resistor so that the gain range can vary from 1 V/V to 11 V/V. What should the resistor value be?



35] Refer to Eq. P 2.35


$$V_0 = V_I \left[1 + \frac{(1-x) \times 10}{x \times 10} \right]$$

$$= V_I (1 + \frac{1}{x} - 1) = \underline{V_I/x} \quad (+10)$$

$$\underline{\frac{V_0}{V_I} = \frac{1}{x}}$$

The gain obtained ranges from +1 to ∞ . (+5)
 For gain range of +1 to +11, need to
 add a resistor R to ground end of pot
 so that with $x=0$,
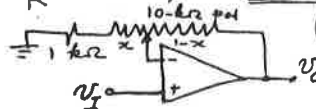
$$\text{gain} = 1 + \frac{10 \text{ k}\Omega}{R} = 11 \Rightarrow R = \underline{1 \text{ k}\Omega} \quad (+10)$$



Final Exam (200 pts: 25 pts each)- Spring 1996 - M. Cahay

Name: KEY

ELECTRONICS I

June 5, 1996


I. In the circuit below, express v_0 in terms of v_1 and v_2 . Assume the op-amps are ideal. Calculate v_0 if

$$v_1 = 3\sin(2\pi \times 60t) + 0.01\sin(2\pi \times 1000t) \text{ Volts,} \quad (1)$$

and

$$v_2 = 3\sin(2\pi \times 60t) - 0.01\sin(2\pi \times 1000t) \text{ Volts.} \quad (2)$$

Show your work.

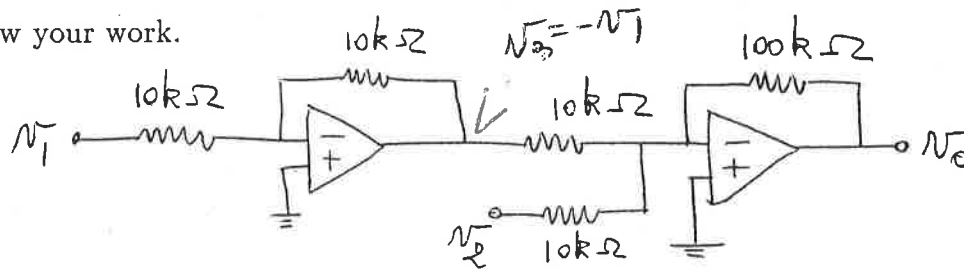

$$v_2 = 0 \quad v_{01} = -10v_3 = 10v_1$$


$$v_1 = 0 = v_3 \quad v_{02} = -10v_2$$

$$v_0 = v_{01} + v_{02} = -10(v_3 + v_2) = 10(v_1 - v_2)$$

$$v_1 - v_2 = \pm 0.02 \sin(2\pi \times 1000t)$$

$$\rightarrow v_0 = \pm 0.2 \text{ V } \sin(2\pi \times 1000t)$$

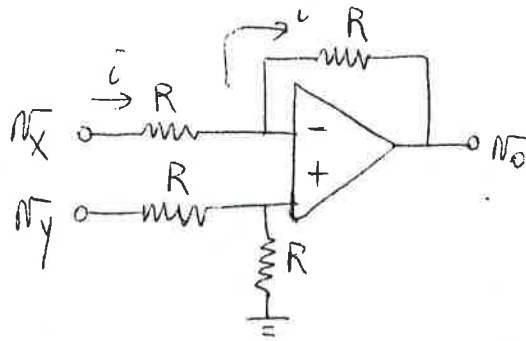III. (25 pts) In the circuit below, the op-amp is ideal except that it has a finite A. Express v_o in terms of v_x , v_y , and the open-loop gain A. If v_y is grounded, What is the input resistance seen by v_x . Express your answer in terms of R and A.



(15 pts)
A

$$v_+ = \frac{v_y}{2}$$

(+3)

$$v_- = ? \quad v_o = A(v_+ - v_-)$$

$$v_+ - v_- = \frac{v_o}{A}$$

$$v_- = v_+ - \frac{v_o}{A}$$

(+3)

$$i = \frac{v_x - v_-}{R} = \frac{v_- - v_o}{R}$$

(+4)

$$\Rightarrow v_o = 2v_- - v_x = 2\left(v_+ - \frac{v_o}{A}\right) - v_x$$

(+2)

$$= 2\frac{v_y}{2} - \frac{2v_o}{A} - v_x$$


$$v_o\left(1 + \frac{2}{A}\right) = v_y - v_x$$

$$v_o = \frac{v_y - v_x}{1 + \frac{2}{A}}$$

(+3)

(15 pts)
B

$$v_y = 0$$

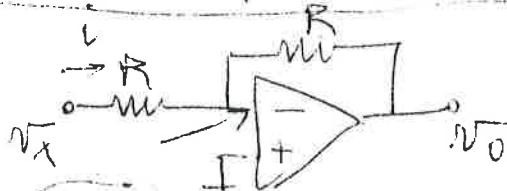

$$\frac{-v_o}{A}$$

$$v_x + \frac{v_o}{A} = v_- - v_o = -\frac{v_o}{A} - v_o$$

(+4)

$$R_{in} = \frac{v_x}{i}$$

$$\Rightarrow v_x = -\left(\frac{2}{A} + 1\right)v_o \Rightarrow R_{in} = \frac{v_x R}{v_x + \frac{v_o}{A}} = R \frac{1}{1 + \frac{2}{A}}$$

(+3)


$$R_{in} \stackrel{V}{=} R \text{ as } A \rightarrow \infty$$

$$R_{in} = R \left(\frac{A+2}{A+1} \right)$$

↑↑

$$R_{in} = R \frac{1}{1 + \frac{2}{A}}$$

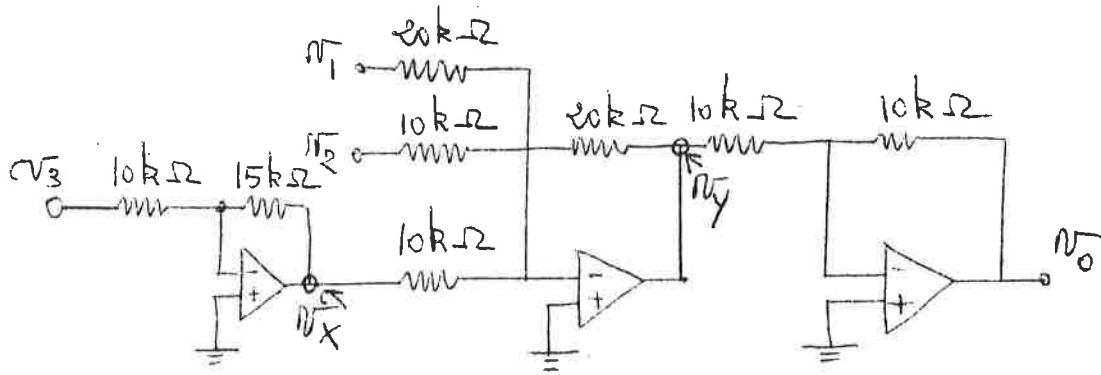II. (25 pts) In the circuit shown below, assume that all op-amps are ideal. Give an expression for v_0 in terms of v_1 , v_2 , and v_3 . Show all intermediate steps for full credit.



$$v_x = -\frac{3}{2}v_3 \quad +4$$

$$v_y = -v_1 - 2v_2 - 2v_x = -v_1 - 2v_2 - 2\left(-\frac{3}{2}v_3\right) \quad +4$$

$$v_y = -v_1 - 2v_2 + 3v_3 \quad +4$$

$$v_0 = -v_y = v_1 + 2v_2 - 3v_3 \quad +4$$

IV: (25 pts) A measurement of the open-loop gain of an internally compensated op-amp at very low frequencies show it to be $4.2 \times 10^4 \text{ V/V}$. At 100 kHz, it is 76 V/V . Estimate the values for A_o , f_b , and f_t . Remember that your answers must be in Hz for f_b and f_t .

$$A_o = 4.2 \times 10^4 \text{ V/V} \quad (+5)$$

$$A = \frac{A_o}{1 + j \frac{f}{f_b}} \quad (+5)$$

$$|A| = \frac{A_o}{\sqrt{1 + \left(\frac{f}{f_b}\right)^2}}$$

$$76 = \frac{4.2 \times 10^4}{\sqrt{1 + \left(\frac{100}{f_b}\right)^2}} \Rightarrow \begin{cases} f_b = 0.181 \text{ kHz} \\ f_b = 181 \text{ Hz} \end{cases}$$

But $f_t = A_o f_b = 4.2 \times 10^4 \times 0.181 \text{ kHz} \quad (+5)$

$$f_t = \underline{\underline{7.6 \text{ MHz}}}$$

(+5)


Test 1 - Fall 1998 (100pts max) - M. Cahay

Name:

ELECTRONICS I


October 16, 1998

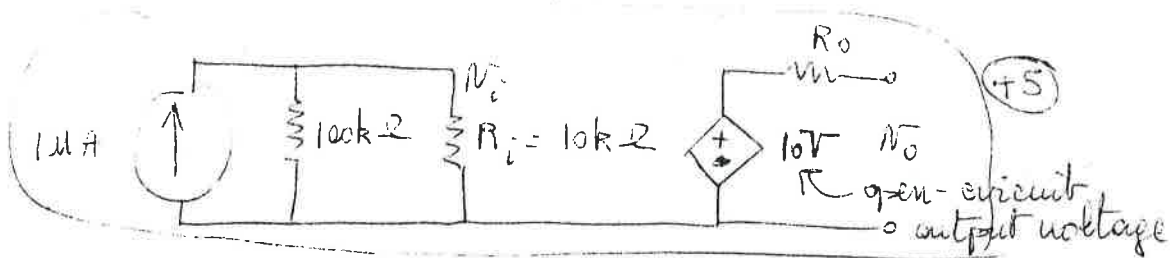(25 pts) A voltage amplifier with an input resistance of $10\text{ k}\Omega$, when driven with a current source of $1\text{ }\mu\text{A}$ and a source resistance of $100\text{ k}\Omega$, has a short-circuit output current of 10 mA and an open-circuit output voltage of 10 V . When driving a $4\text{ k}\Omega$ load, what are the voltage gain, current gain, and power gains expressed in dB?



short circuit output current = 10 mA
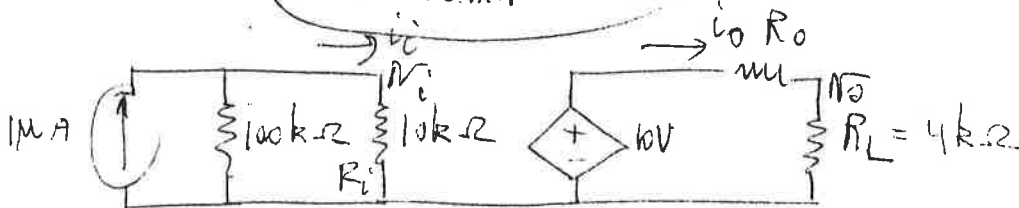
$$R_o = \frac{10\text{ V}}{10\text{ mA}} = 1\text{ k}\Omega$$



$$v_o = 10 \times \frac{4}{4+1} = 8\text{ V}$$

$$A_{vT} = \frac{v_o}{v_i} = \frac{8}{10^{-6} (100/10)} = 888\text{ V/V} \text{ or } 58.9\text{ dB}$$

$$A_{iT} = \frac{i_o}{i_i} = \frac{v_o/R_L}{i_i} = \frac{8/4 \times 10^{-3}}{10^{-6} \frac{100}{100+10}} = 2200\text{ A/A} \text{ or } 66.8\text{ dB}$$

$$A_{PT} = \frac{P_o/R_L}{R_i i_i^2} = 14.36 \times 10^8\text{ W/W} = 62.9\text{ dB} = \frac{1}{2} [A_{vT} + A_{iT}]$$