

# **Introduction to VLSI Testing**

李昆忠

**Kuen-Jong Lee**

**Dept. of Electrical Engineering  
National Cheng-Kung University  
Tainan, Taiwan, R.O.C.**


# Problems to Think

- **A 32 bit adder**
- **A 32 bit counter with RESET function**
- **A 1MB cache memory**
- **A  $10^7$ -transistor CPU**

# OUTLINE

- Introduction
- Fault modeling
- Fault simulation
- Test generation
- Automatic test pattern generation (ATPG)
- Design for testability
- Built-in self test
- Synthesis for testability
- An example
 
# Testing: To tell whether a system is good or bad



## Related fields

**Verification**: To verify the correctness of a design

**Diagnosis**: To tell the faulty site


**Reliability**: To tell whether a good system will work after some time.

# Importance of testing

**N = # transistors in a chip**

**p = prob. (a transistor is faulty)**

**Pf = prob. (the chip is faulty)**

   **$Pf = 1 - (1 - p)^N$**


**If  $p = 10^{-6}$**

**$N = 10^6$**

  **$Pf = 63.2\%$**
 
# Difficulties in Testing

- **Fault may occur anytime**
  - Design
  - Process
  - Package
  - Field
- **Fault may occur at any place**



- **VLSI circuit are large**
  - Most problems encountered in testing are NP-complete
- **I/O access is limited**


# How to do testing from Designer's points of view

- **Circuit modeling**
- **Fault modeling**



 
**Modeling**

- **Logic simulation**
- **Fault simulation**
- **Test generation**



 **ATPG**

- **Design for test**
- **Built-in self test**




**Testable design**

- **Synthesis for testability**

 
# Circuit Modeling

- **Functional model---** logic function
  - $f(x_1, x_2, \dots) = \dots$
  - Truth table
- **Behavioral model---** functional + timing
  - $f(x_1, x_2, \dots) = \dots$  , Delay = 10
- **Structural model---** collection of interconnected components or elements




# Levels of Description


- **Circuit level**

 

- **Gate level**

 


- **Switch level**

 

- **Higher/ System level**
 
# Fault Modeling

- The effects of physical defects
- Most commonly used fault model: **Single stuck-at fault**



A s-a-1 B s-a-1 C s-a-1 D s-a-1  
A s-a-0 B s-a-0 C s-a-0 D s-a-0

E s-a-1 F s-a-1 G s-a-1  
E s-a-0 F s-a-0 G s-a-0


**14 faults**

- **Other fault models:**
  - Break faults, Bridging faults, Transistor stuck-open faults, Transistor stuck-on faults, Delay faults

# Fault Coverage (FC)

$$FC = \frac{\text{\# faults detected}}{\text{\# faults in fault list}}$$


Example:

 

6 stuck-at faults  
(  $a_0, a_1, b_0, b_1, c_0, c_1$  )

Test	faults detected	FC
$\{(0,0)\}$	$c_1$	16.67%
$\{(0,1)\}$	$a_1, c_1$	33.33%
$\{(1,1)\}$	$a_0, b_0, c_0$	50.00%
$\{(0,0), (1,1)\}$	$a_0, b_0, c_0, c_1$	66.67%
$\{(1,0), (0,1), (1,1)\}$	all	100.00%

# Testing and Quality

 

- **Quality of shipped parts is a function of yield  $Y$  and the test (fault) coverage  $T$**
- **Defect level (DL) : fraction of shipped parts that are defective**

# Defect Level, Yield and Fault Coverage

$$DL = 1 - Y(1-T)$$

**DL:** defect level




**Y:** yield

**T:** fault coverage

Yield (Y)	Fault Coverage (T)	DPM (DL)
50%	90%	67,000
75%	90%	28,000
90%	90%	10,000
95%	90%	5,000
99%	90%	1,000
90%	90%	10,000
90%	95%	5,000
90%	99%	1,000
90%	99.9%	100

   
# Logic simulation

- To determine how a good circuit should work
- Given input vectors, determine the normal circuit response



 
# Fault simulation

- To determine the behavior of faulty circuits



- Given a test vector, determine all faults that are detected by this test vector.

**Example:**

 


Test vector (1 1) detects  
 $\{ a_0, b_0, c_1 \}$

# Test generation

- Given a fault, identify a test to detect this fault

Example:

 

To detect D s-a-0, D must be set to 1.


Thus  $A=B=1$ .

To propagate fault effect to the primary output  
E must be 1. Thus C must be 0.

Test vector:  $A=1, B=1, C=0$

 
# Automatic Test Pattern Generation (ATPG)

- Given a circuit, identify a set of test vectors to detect all faults under consideration.




# Difficulties in test generation

## 1. Reconvergent fanout

 

# Difficulties in test generation (cont.)

## 2. Sequential test generation

 


# Testable Design

- **Design for testability (DFT)**
  - *ad hoc* techniques
  - Scan design
  - Boundary Scan
- **Built-In Self Test (BIST)**
  - Random number generator (RNG)
  - Signature Analyzer (SA)
- **Synthesis for Testability**


# Example of *ad hoc* techniques

Insert test point

 


# Scan System






Original design

 


Modified design

 


# Scan Cell Design

     

# Scan Register

 


# Boundary Scan

 


**TRST\***: Test rest (Optional)  
**TDI**: Test data input  
**TDO**: Test data output  
**TCK**: Test clock  
**TMS**: Test mode select

# Boundary Scan (Cont.)

 

 
# Built-In-Self Test (BIST)

- Places the job of device testing inside the device itself
- Generates its own stimulus and analyzes its own response



 
# Built-In-Self Test (BIST) (Cont.)

- **Two major tasks**
  - Test pattern generation
  - Test result compaction
- **Usually implemented by linear feedback shift register**




# Random Number Generator (RNG)

 

0001	0110	1111
1000	1011	0111
0100	0101	0011
0010	1010	0001
1001	1101	(repeat)
1100	1110	

1. Generate “pseudo” random patterns
2. Period is  $2^n - 1$

# Signature Analyzer (SA)

 

$$G(x) = 1 + x^2 + x^4 + x^5 + x^6 + x^7 \quad P(x) = 1 + x^2 + x^4 + x^5$$

Time	Input stream	Register contents	Output stream
0	1 0 1 0 1 1 1 1	0 0 0 0 0	← Initial state
1	1 0 1 0 1 1 1	1 0 0 0 0	
·	·	·	
·	·	·	
5	1 0 1	0 1 1 1 1	
6	1 0	0 0 0 1 0	1
7	1	0 0 0 0 1	0 1
8		0 0 1 0 1	1 0 1
		$\underbrace{\hspace{2cm}}$	$\underbrace{\hspace{2cm}}$
		Remainder	Quotient
		$R(x) = x^2 + x^4$	$1 + x^2$

## Signature Analyzer (SA) (Cont.)

$$P(x) : x^5 + x^4 + x^2 + 1$$

$$\times Q(x) : x^2 + 1$$

---

$$x^7 + x^6 + x^4 + x^2 + x^5 + x^4 + x^2 + 1$$

$$= x^7 + x^6 + x^5 + 1$$


$$P(x)Q(x) + R(x) = x^7 + x^6 + x^5 + x^4 + x^2 + 1 = G(x)$$

**Prob. of aliasing error =  $1/2^n$**


**where n is # of FFs**

# Memory BIST Architecture with a Compressor


Before

 


After

 
 
# Memory BIST Architecture with a Compressor (Cont.)




# Three Memories and One Compressor

 


# Synthesis for Testability

- **Automatic v.s Semi-automatic**
- **Commercial products**
  - Testability analysis tools
  - Full / partial scan insertion
  - BIST insertion
  - Boundary scan insertion
- **Research**
  - RTL synthesis
  - FSM synthesis
  - Gate level synthesis
  - Boolean equation synthesis

# CPU Test Control Architecture

 

# Testable Design Flow

 

# Problems re-thinking

- **A 32-bit adder --- ATPG**
- **A 32-bit counter --- Design for testability + ATPG**
- **A 1MB Cache memory --- BIST**
- **A  $10^7$ -transistor CPU --- All test techniques**

# Conclusions

## Two major fields in testing

- **ATPG**
  - Fault simulation
  - Test generation
- **Testable design**
  - Design for testability
  - Built-in self-test
  - Synthesis for testability